



# Applied Electronics

## Ee – Exercises Part E

- BJT Switches
- Power supplies
- Linear regulators
- Switching regulators



# Ee: Power and supply circuits

- Ee1 Power switches
- Ee2 Rectifier and filter circuits
- Ee3 Voltage regulators with Zener diode
- Ee4 Voltage regulators with Zener diode and transistor
- Ee5 Switching regulators



# Ee1: Power switch


- A BJT is used as ON/OFF switch for a  $100\ \Omega$  load, powered at  $12\ \text{V}$ .
- Transistor parameters
  - ◆  $\beta = 50$
  - ◆  $V_{\text{CEsat}} = 0.2\ \text{V}$
- a. Draw the interface circuit to drive the BJT using a CMOS gate supplied with  $V_{\text{DD}} = 5\ \text{V}$ .
- b. Determine the maximum power dissipated in the transistor.



- a. Draw the interface circuit to drive the BJT switch using a CMOS gate supplied with  $V_{DD} = 5\text{ V}$ .
- b. Determine the maximum power dissipated in the transistor.
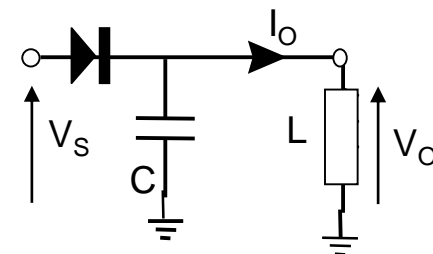
## Ee2: rectifier / filter circuit


- The circuit in the figure is a half-wave rectifier with filter
  - ◆  $V_S = 18 V_{\text{eff}}$  at 60 Hz
  - ◆  $C = 470 \mu\text{F}$
- a. Determine the output ripple voltage,  $V_{\text{OR}}$  for a load current  $I_O = 90 \text{ mA}$ .  
Under these conditions, calculate the output voltage direct component,  $V_{\text{Odc}}$ .
- b. Calculate the output voltage variations ( $\Delta V_{\text{Odc}}$ ) and the max ripple ( $V_{\text{ORmax}}$ ) for load current  $I_O$  varying from 0 mA to 100 mA.
- c. Modify the circuit to use a full-wave rectifier. Calculate the new  $V_{\text{Odc}}$  and  $V_{\text{OR}}$ .





## Ee2-a: rectifier and filter

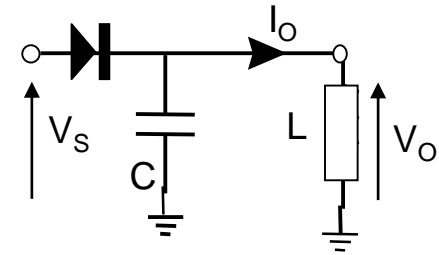
- a. Determine the output ripple voltage,  $V_{OR}$  for a load current  $I_O = 90$  mA. Under these conditions, calculate the output voltage direct component,  $V_{Odc}$ .





## Ee2-b: output ripple

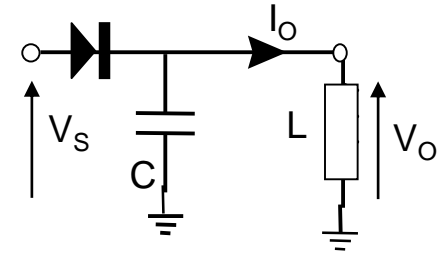- b. Calculate the output voltage variations ( $\Delta V_{Odc}$ ) and the max ripple ( $V_{ORmax}$ ) for load current  $I_O$  from 0 mA to 100 mA.






## Ee2-c: full-wave rectifier

- c. Modify the circuit to use a full-wave rectifier.  
Calculate the new  $V_{Odc}$  and  $V_{OR}$ .
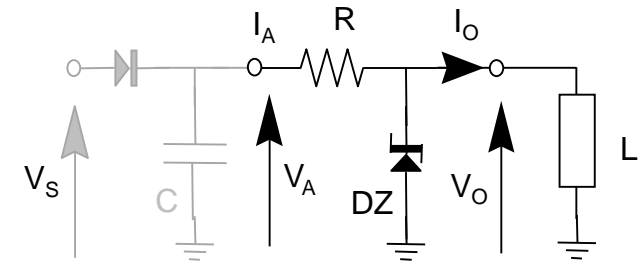
# Ee3: voltage regulator with Zener

- To the previous rectifier-filter group is added a Zener diode

- $V_S = 18 V_{\text{eff}}; C = 470 \mu\text{F};$   
 $R = 120 \Omega; V_{Z0} = 9 V;$   
 $r_Z = 10 \Omega; I_{Z\text{min}} = 7 \text{ mA}$




- For  $V_A = V_{\text{Adc}} + V_{\text{AR}}$ , calculate
  - the continuous component  $V_{\text{Odc}}$
  - the ripple voltage  $V_{\text{OR}}$  for a load current  $I_O = 100 \text{ mA}$
- Determine the power  $P_Z$  dissipated by the Zener diode for  $V_A = V_{\text{Adc}}, I_O = 100 \text{ mA}$ .  
What operating conditions maximize  $P_Z$ ?
- Determine the maximum value of  $R$  that maintains the functionality of the regulator for output currents up to  $200 \text{ mA}$



# Ee3-a regulator with Zener

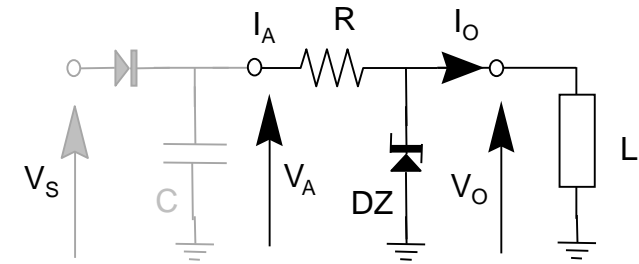
- a. For  $V_A = V_{A_{dc}} + V_{AR}$ , calculate
- the continuous component  $V_{O_{dc}}$
  - the ripple voltage  $V_{OR}$
- for a load current  $I_O = 100 \text{ mA}$





# Ee3-b regulator with Zener

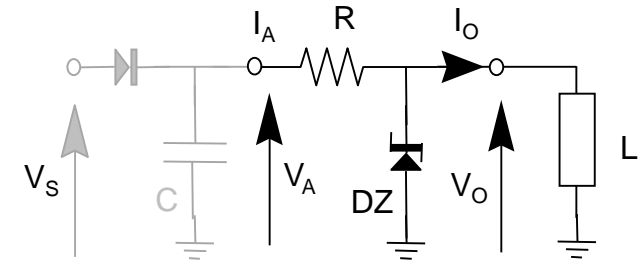
- b. Determine the power  $P_Z$  dissipated by the Zener diode for  $V_A = V_{A_{dc}}$ ,  $I_O = 100$  mA. What operating conditions maximize  $P_Z$ ?





# Ee3-c regulator with Zener

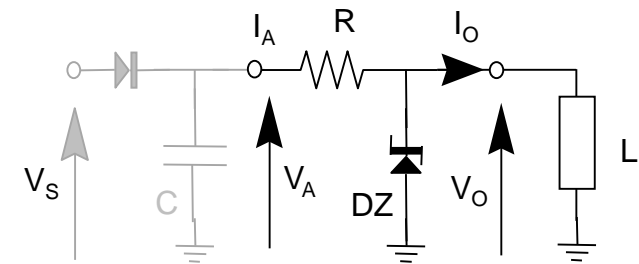- c. Determine the max  $R$  that maintains the functionality of the regulator for output currents up to 200 mA





## Ee4: Zener regulator + transistor

- Add a BJT (npn) to the previous circuit to improve the regulation for various current loads. For the new circuit:
  - a. Determine the power dissipated by the Zener diode and by the transistor for  $V_A = V_{Adc}$ , with  $I_O = 0$  A (no-load).
  - b. How does the regulation change (compared to the circuit with only the Zener diode) for variations in the input voltage and for variations in the load current (qualitative answer).
  - c. Calculate the maximum power dissipated in the Zener diode and in the transistor, for output currents from 0 mA to 100 mA.



## Ee4-a: dissipated power

- a. Determine the power dissipated by the Zener diode and by the transistor for  $V_A = V_{Adc}$ , with  $I_O = 0$  A (no-load).



## Ee4-b: Zener regulator + transistor regulator

- b. How does the regulation change (compared to the circuit with only the Zener diode) for variations in the input voltage and for variations in the load current (qualitative answer).



## Ee4-c: dissipated power

- c. Calculate the max power dissipated in the Zener diode and transistor, for output currents from 0 mA to 100 mA.



# Ee5: switching regulator

- Draw the schematic of a switching regulator with  $V_O < V_I$ 
  - a. Evaluate the duty cycle limits of the command signal required to obtain a 5 V output with input voltages from 8 V to 15 V
  - b. Evaluate the performance considering  $V_{CEsat}$  and  $R_{ON}$