



Applied Electronics

C1 – Interconnections

- Signal integrity, EMI
- Static and dynamic interfacing
- RC models of interconnection
- Definition of parameters



The real bottleneck

- Currently more than 10^9 transistors/chip (Intel i9), but...
 - ◆ How to transfer the **information** – distribution of signals?
 - ◆ How to transfer the **energy** – power supply system?
 - ◆ How to remove the **heat** – thermal circuits?
- The **distribution of signals** and **power** is the main performance **bottleneck** of IC, SoC, PCB
 - ◆ Digital circuits use **0 and 1** (binary symbols), but ...
 - The real quantities are **Voltages** and **Currents** (V and I)
 - ◆ Needed **analog electronics** and **microwaves** knowledge
 - Behaviors related to the physical structure (layout)
 - Consider the effects of propagation (transmission lines)
 - Always useful analysis, necessary for **high-speed** systems



Unit C: interconnections – objectives

- Problems of interconnection systems for:
 - ◆ Signals (transport of information)
 - ◆ Power (transport of energy)
- Main point: the conductors **are not single nodes**
- Problems are known as **SIGNAL INTEGRITY**
- Objective: understand and apply *basic techniques* for
 - ◆ **Transfer of digital signals**
 - Bus and communication protocols
 - ◆ **Energy distribution** for power supply
 - Bypass capacitors, layout criteria, ...



Unit C: organization and contents

- C1: Signal integrity, problems, RC models.
- C2: Transmission line models
- C3: Interconnections with transmission lines
- C4: Basic transfer operations
- C5: Bus protocols
- C6: Serial communications
- C7: Signal integrity, power distribution



Unit C: reference texts

- D. Del Corso: "Interconnections for high-speed digital circuits", 2 parts, MindSigInt1.pdf and MindSigInt2.pdf
 - ◆ PDFs are available in the Applied Electronics → Course materials folder in the “Materials” tab in the course site




Lecture C1: Interconnections


- Signal integrity and interferences (EMI)
- Limits due to interconnections
 - ◆ Problem identification
 - ◆ Static and dynamic interfacing
- Models of the interconnection system
 - ◆ RC model
 - ◆ Definition of parameters
- References
 - ◆ D. Del Corso: Interconnections for High Speed ..: lectures 1, 2

Time-domain noise: Jitter and Skew

 - Difference between delays: **skew** t_K
 - ◆ Skew is defined for **one transition** simultaneous for **two signals**



 - Variation from period to period: **jitter** t_J
 - ◆ Jitter is measured on **two transitions** of a **single signal**



- Skew and Jitter **change temporal relationships**
 - ◆ Change the timing margins, hence the synchronization!
 - ◆ Are **random variables**, usually defined by the **maximum** (min = 0)




-

- $$\blacklozenge T_{CKmin} = T_{CO} + T_L + T_{SU} + T_J$$

◆ $F_{\max} = 1 / T_{\text{CKmin}}$

◆ $F_{\max}(T_{CO}, T_L, T_J, T_{SU})$

 

F_{\max} : effect of interconnections


- The **interconnections** introduce propagation delays T_P
 - The OUT and IN nodes are separated (transmission delays T_{Pn})
 - The delays are partly unknown

- Max operating frequency


$$T_{CKmin} = T_{CO} + T_L + T_{SU} + T_J + f(T_{P1}, T_{P2}, T_{P3})$$

$$F_{\max} = 1 / T_{CKmin}$$


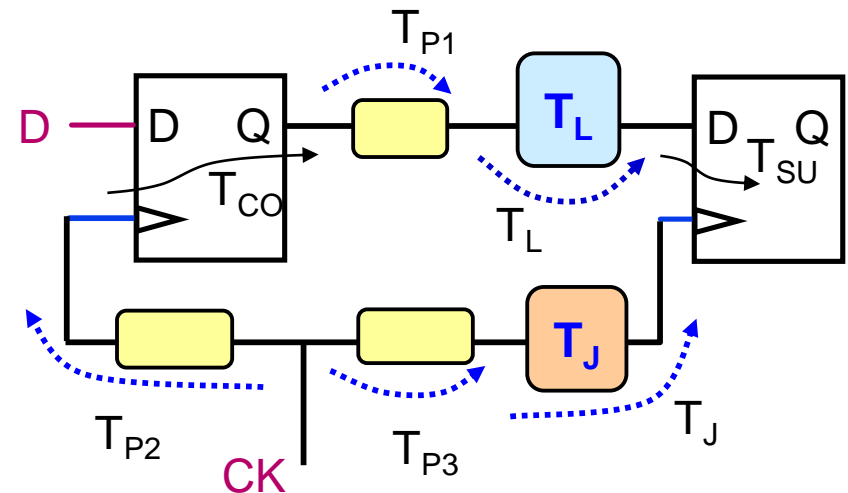
$$F_{\max} (T_{CO}, T_L, T_{P1}, T_{P2}, T_{P3}, T_J, T_{SU})$$



Ideal interconnection

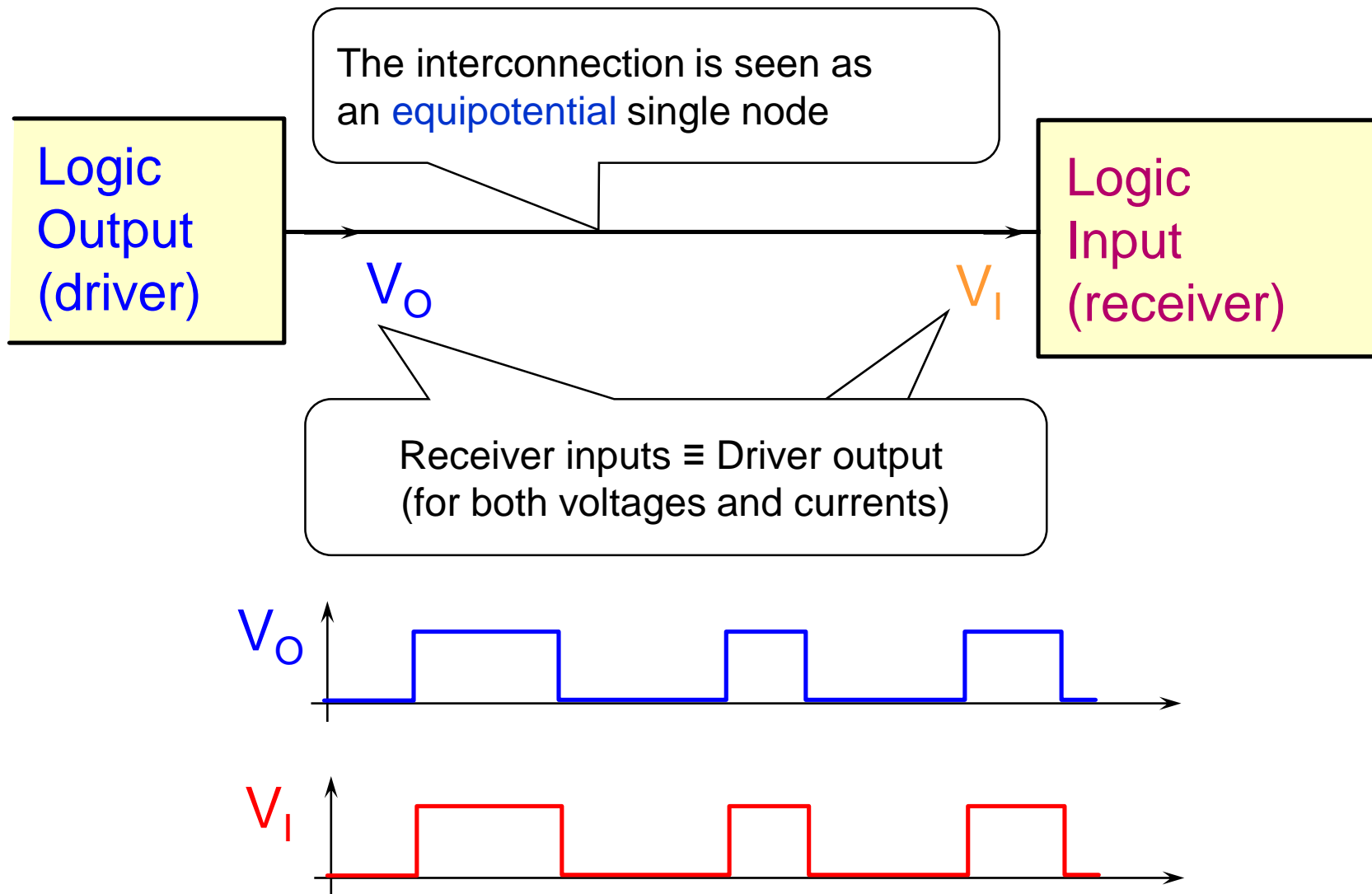

Real interconnection

  



Interconnection models

- How to analyze the exchange of digital information?
 - ◆ Use a **layered pattern** (ISO-OSI type)
 - ◆ Define **services and interfaces** for each layer
 - Highest level: application
 - ...
 - Lowest level: physical variables (V, I, R, ...)
- These lectures cover the **lower levels**
 - ◆ **Physical:** transfer of single bits
 - ◆ **Cycle:** transfer of groups of bits
 - ◆ **Transaction:** reading instructions/data, writing, ...
- Objectives: **correctness, speed, low power**



References to the ISO-OSI Model

- 7 APPLICATION
- 6 PRESENTATION
- 5 SESSION
- 4 TRANSPORT
- 3 NETWORK
- 2 DATA LINK
- 1 PHYSICAL

In lectures
of group C



Signal integrity and protocols

TRANSACTION

Data transfer,
instructions, ...

CYCLE

Transfer of bit groups

CYCLE 1

CYCLE 2

CYCLE 3

CYCLE N

Time margins,
synchronization

Lectures
C3, C4
(protocols)

ELECTRIC level


Single bit transfer

Voltages,
Currents,
R, C, Z, ...

Lectures
C1, C2
(signal
integrity)


Ideal interconnection (IT)

 What happens in a conductor (wire)? → “minimum” model



Same signal at points A and D

Real interconnection (electronics)

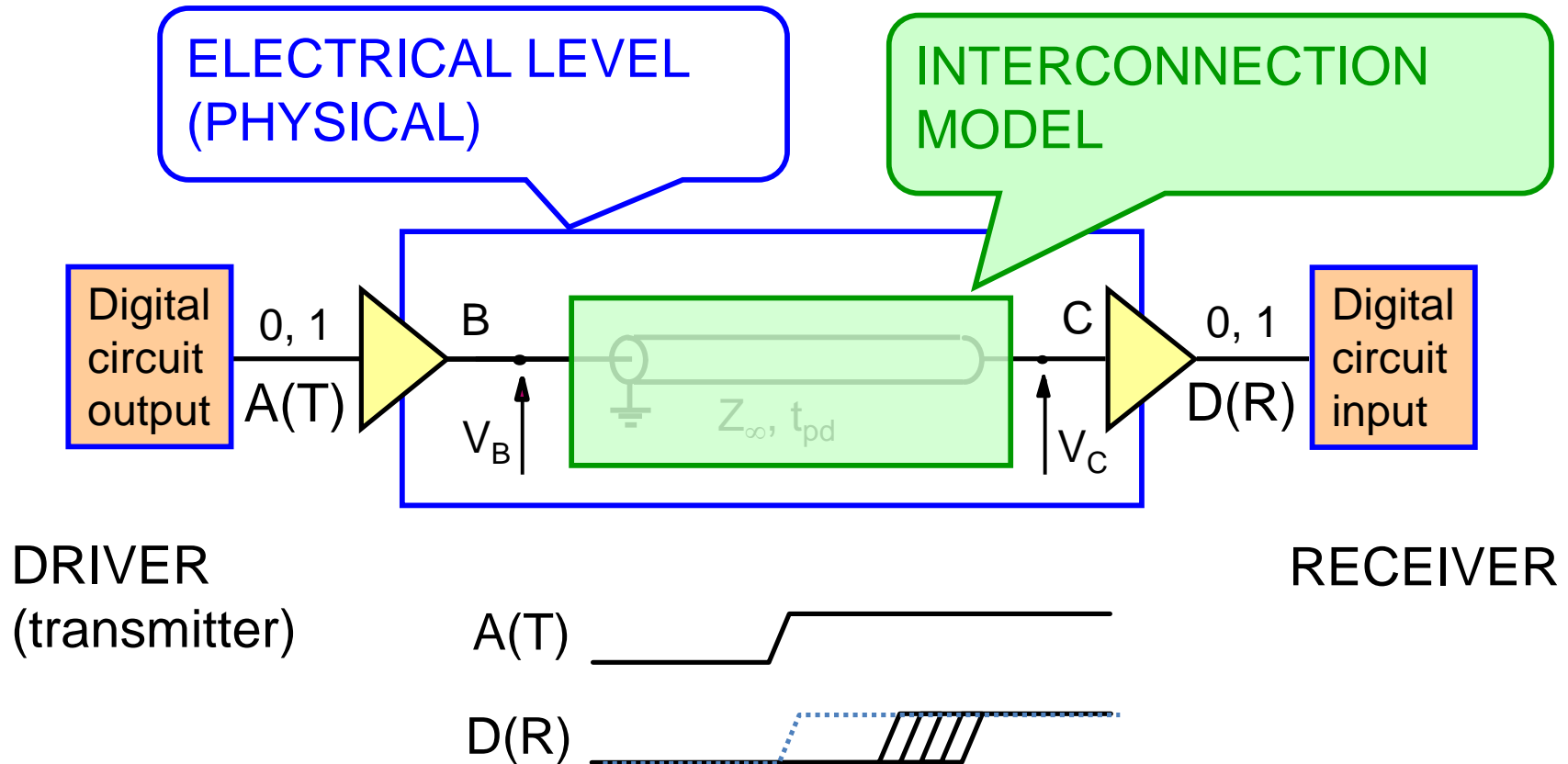

Analog effects from B to C: additive noise, delay, ...

Digital effects from A to D: delay, skew.



Analysis sequence

- OBJECTIVES: maximum speed, no errors
 - ◆ How to distribute energy and signals to maximize clock freq. F_{CK}
 - Limits from structure and physical parameters
 - ◆ How to preserve the information correctness
 - Ensure compliance with static and dynamic specifications
- Models and procedures are needed for
 - ◆ Static and dynamic interfacing of logic circuits
 - ◆ Behavior of interconnections (delays, noise, ...)
 - ◆ → Signal integrity
- Correct distribution of power supply is important
 - ◆ → Power integrity


Models for Driver and Receiver

- Linear model for driver and receiver
 - ◆ A, D input/output Boolean variables (0, 1)
 - ◆ R_O equivalent driver output resistance
 - ◆ R_I equivalent input resistance of the receiver ($\rightarrow \infty$)
 - ◆ C_I equivalent input capacitance of the receiver





Single equipotential node

 - The simplest interconnection model
 - ◆ Interconnection modeled as **single node** ($B \equiv C$) (no loss, no delay)
 - ◆ One can define the parameters
 - Transmission time: T_{TX}
 - Skew (misalignment): T_K



RC model

  - Driver-receiver connection modeled as **low-pass RC** cell
- Voltage step on V_A
- **Exponential** evolution
 - ◆ Time constant (τ)
 $\tau = R C$
 - ◆ Logical state change detected when V_C crosses the threshold V_T
- **Delay t_{TX}** in the reception




Transmit Time and Skew

- Delay with which a change in logic state is detected
 - ◆ TRANSMISSION TIME (t_{TX})
 - ◆ Called also t_p (propagation time)
 - ◆ Called t_{TX} here to emphasize the interconnection
- t_{TX} mainly depends on
 - ◆ Initial and final levels at the driver output (V_H , V_L)
 - ◆ Threshold of the receiver (V_T)
 - ◆ Driver output resistance (R_O)
 - ◆ Receiver input capacitance (C_I)
- These parameters can have wide variations
 - ◆ t_{TX} depends on interconnection, even with identical components



Variations of t_{TX} and Skew t_K

- The difference $t_{TXmax} - t_{TXmin}$ is the **SKEW t_K**
 - ◆ The skew (misalignment) to a receiver depends on the dispersion of the parameters that determine t_{TX}

 - ◆ ΔR_O
- ◆ ΔC_I
- ◆ $\Delta V_{H/L}$
- ◆ ΔV_T
- ◆ ...



Parameters of an interconnection

  

t_{TX} → transmission time
 t_{TXmax} → transmission time max
 t_{TXmin} → transmission time min
 $t_K = t_{TXmax} - t_{TXmin}$ → SKEW

Exercise C1.1: RC model delays

- A CMOS driver and receiver are connected using an equipotential conductor with the parameters
 - ◆ Driver: $V_{DD} = 5 \text{ V}$, $R_O = 120 \Omega$
 - ◆ Receiver: $R_I \rightarrow \infty$, $V_{IH} = 3 \text{ V}$, $V_{IL} = 1 \text{ V}$
 - ◆ Total equivalent capacitance: $C = 80 \text{ pF}$
- For a transition $L \rightarrow H$ plot the signals on
 - ◆ Driver input
 - ◆ Driver output – conductor – receiver input
 - ◆ Receiver output
- Calculate the transmission time t_{TX} and the skew t_K

Effects of skew – single signal

- The skew is the indetermination of the **time position** of the signal at the receiver – example only for **signal A**

◆ $t_{1\min} = t_{TX\min}$


◆ $t_{1\max} = t_{TX\max} = t_{TX\min} + t_K$

Signals
at the driver

A(D)

Signals
at the receiver

A(R)

 

Effects of skew – pair of signals

- Skew **changes temporal relationships between signals**

◆ The set-up time t_{SU} is **reduced** by t_K

$$t_1 = t_0 + t_{TXm} + t_K$$

$$t_2 = t_0 + t_{SU(D)} + t_{TXm}$$

$$t_{SU(R)} = t_2 - t_1 = t_{SU(D)} - t_K$$

Signals
at the driver


Signals
at the receiver

A(D)


B(D)

A(R)

B(R)

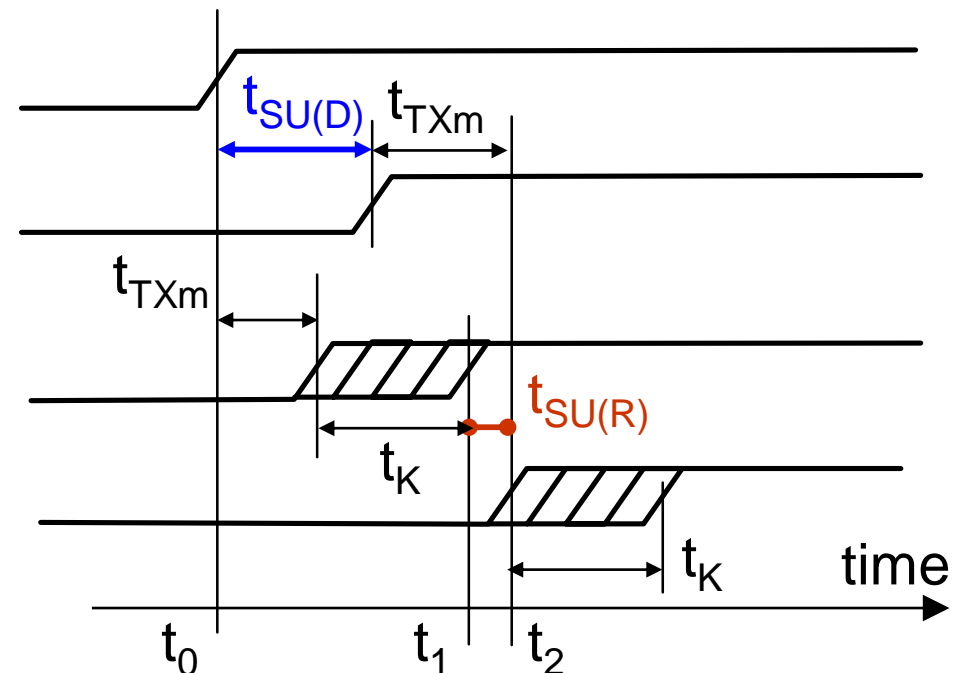

Model of the lower layers

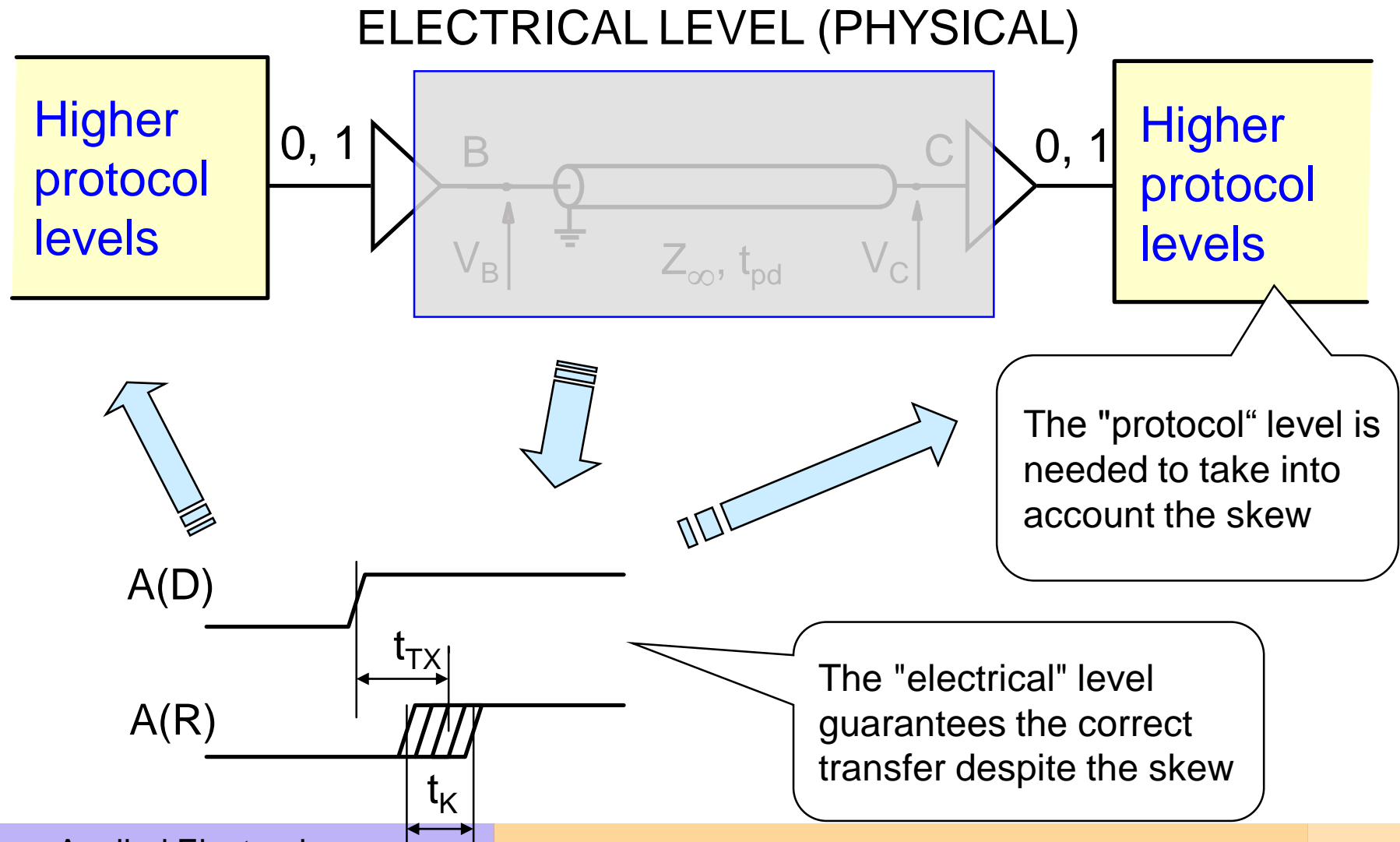



Lecture C1 – final test

- Why is the analysis of interconnections important?
- Describe the structure and advantages of a layered model.
- Explain the meaning of “signal integrity”.
- What is the logic state at the output of an inverter with input voltage V_I , where $V_{IL} < V_I < V_{IH}$?
- Define the propagation time and skew.
- For a CMOS driver-receiver pair, does a change in the supply voltage change the transmission time (as a first approximation)?