

# Applied Electronics


## D/A Converters



# D/A Converters


- Parameters of D/A converters
  - ◆ Linear: gain and offset error
  - ◆ Integral and differential nonlinearity
  - ◆ Dynamic parameters
- DAC structures
  - ◆ Uniform and weighted architectures
  - ◆ Ladder networks
  - ◆ Example of circuits
- References
  - ◆ F. Maloberti: Understanding Microelectronics..., Ch. 7.4

# D/A Converters

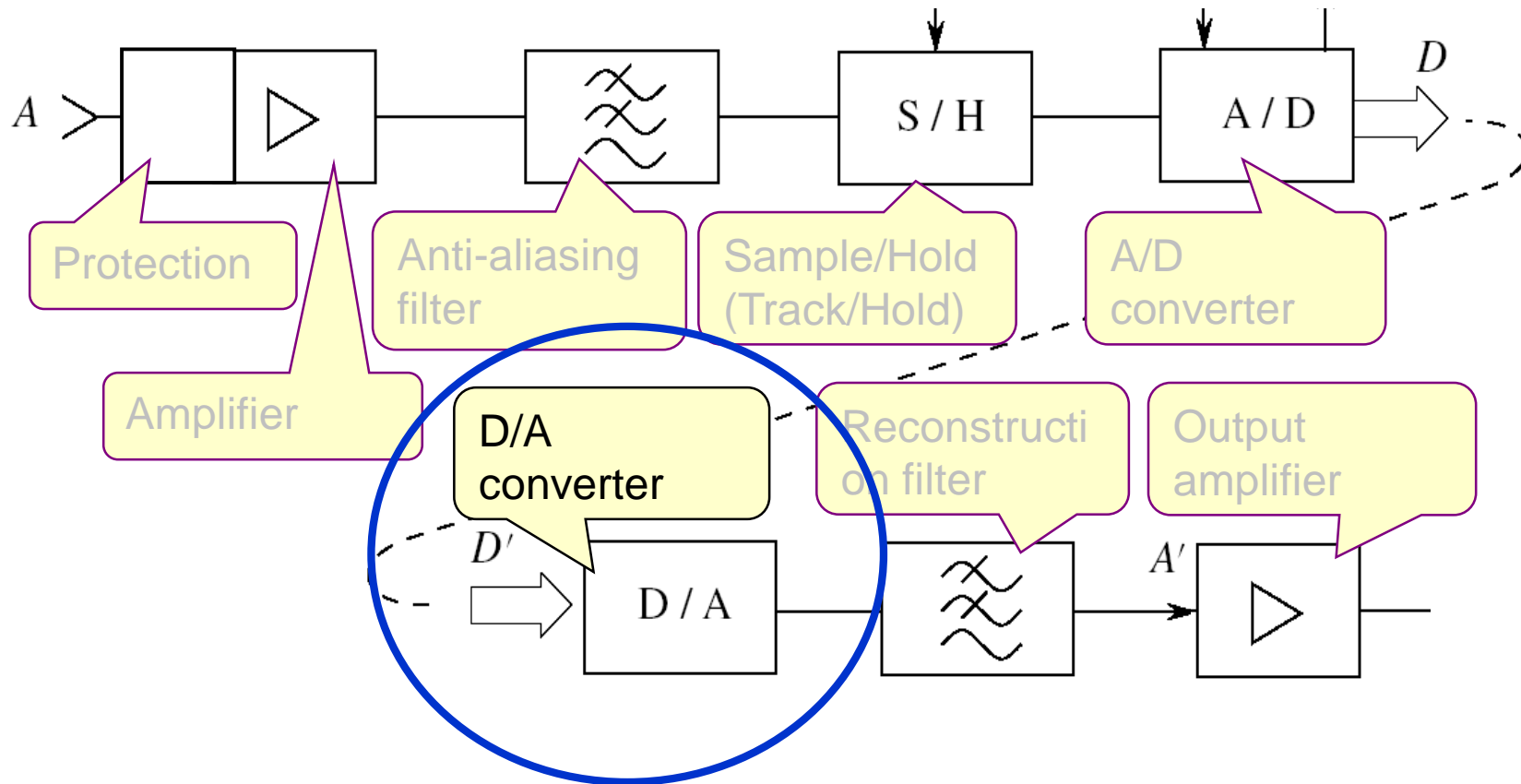
 
# D/A Transfer Function


- Input variable ( $D$ ) is discrete
  - ◆ The  $A(D)$  plot is a **sequence of dots**
  - ◆ For a constant  $A_d$ , the dots are **lined up**




 
# Conversion Characteristic

- $M = 2^N$ 
  - ◆ Many dots for high  $N$
  - ◆ Dot sequence becomes almost a continuous line





# Errors in D/A Converters

- **Static** errors
  - ◆ Constant input
  - ◆ Steady state behavior
  - ◆ Can be seen in the  $A(D)$  plot
- **Dynamic** errors
  - ◆ Variable input signal
  - ◆ Transient behavior
  - ◆ Can be seen in the  $A(t)$  plot




# Static Errors: Two Step Analysis

- Which parameters define “how good” is a DAC?
- The actual transfer function is not a straight line
- Plot the best approximating straight line
- Compare actual/ideal transfer functions in two steps
- 1: From real characteristic to best approximating line
  - ◆ Nonlinearity errors
- 2: From best approximating line → ideal transfer function
  - ◆ Linear errors: offset and gain




# Ideal and Actual D/A Characteristic

 






# Approximation With Straight Line

 



# Ideal vs Best Linear Approximation

 



# Linear Errors: Offset and Gain

- Best approximating line may miss  $(0,0)$  and  $(M,S)$
- Offset  $\varepsilon_o$ 
  - ◆ Best approximating line intercept of the A axis
  - ◆ Can be compensated by **adding a constant**
- Gain error  $\varepsilon_g$ 
  - ◆ Difference between slopes of ideal and best approximating line
  - ◆ Can be compensated by **gain correction**
- This methodology applies for any device with a linear transfer function

# Offset Error

- **Ideal** transfer function

- ◆  $D = 0 \Rightarrow A = 0$


- **Actual** best approximating transfer function

- ◆ Not through (0,0)

- ◆  $D = 0 \Rightarrow A = V_{\text{off}}$

- **Offset** error

- ◆  $\varepsilon_o = V_{\text{off}}$

 

# Gain Error

- **Ideal** transfer function

- ◆  $A = KD$

- **Actual** best approximating transfer function


- ◆ Different slope

- ◆  $A = K'D$

- ◆  $K' = K + \Delta K$

- **Gain** error

- ◆  $\epsilon_g = \frac{\Delta K}{K}$

 



# Nonlinearity Errors


- Compare the real characteristic and the best approximating line
- Real characteristic has nonlinearity errors that change from point to point
  - ◆ Thus, they *cannot be compensated*
- Nonlinearity defined by two parameters
  - ◆ *Differential* nonlinearity (local behavior)
  - ◆ *Integral* nonlinearity (overall behavior)
- Maximum difference between the real characteristic and the best approximation line is a nonlinearity band
  - ◆  $\varepsilon_{inl}$  is called integral nonlinearity error



# Differential Nonlinearity Error


- Ideal transfer function
  - ◆ Dots spaced by  $A_D$  ( $A$  axis) mapped on 1 LSB ( $D$  axis)
- Actual transfer function
  - ◆ Dots spaced by  $A'_D \neq A_D$
- The difference  $A_D - A'_D = \varepsilon_{\text{dnl}}$ 
  - ◆ Differential nonlinearity
- If  $\varepsilon_{\text{dnl}} > 1 \text{ LSB} = A_D$  (slope inversion)
  - ◆  $A_D - A'_D > A_D \rightarrow A'_D < 0$
  - ◆ *Non-monotonicity error*

# Nonlinearity Errors: Differential

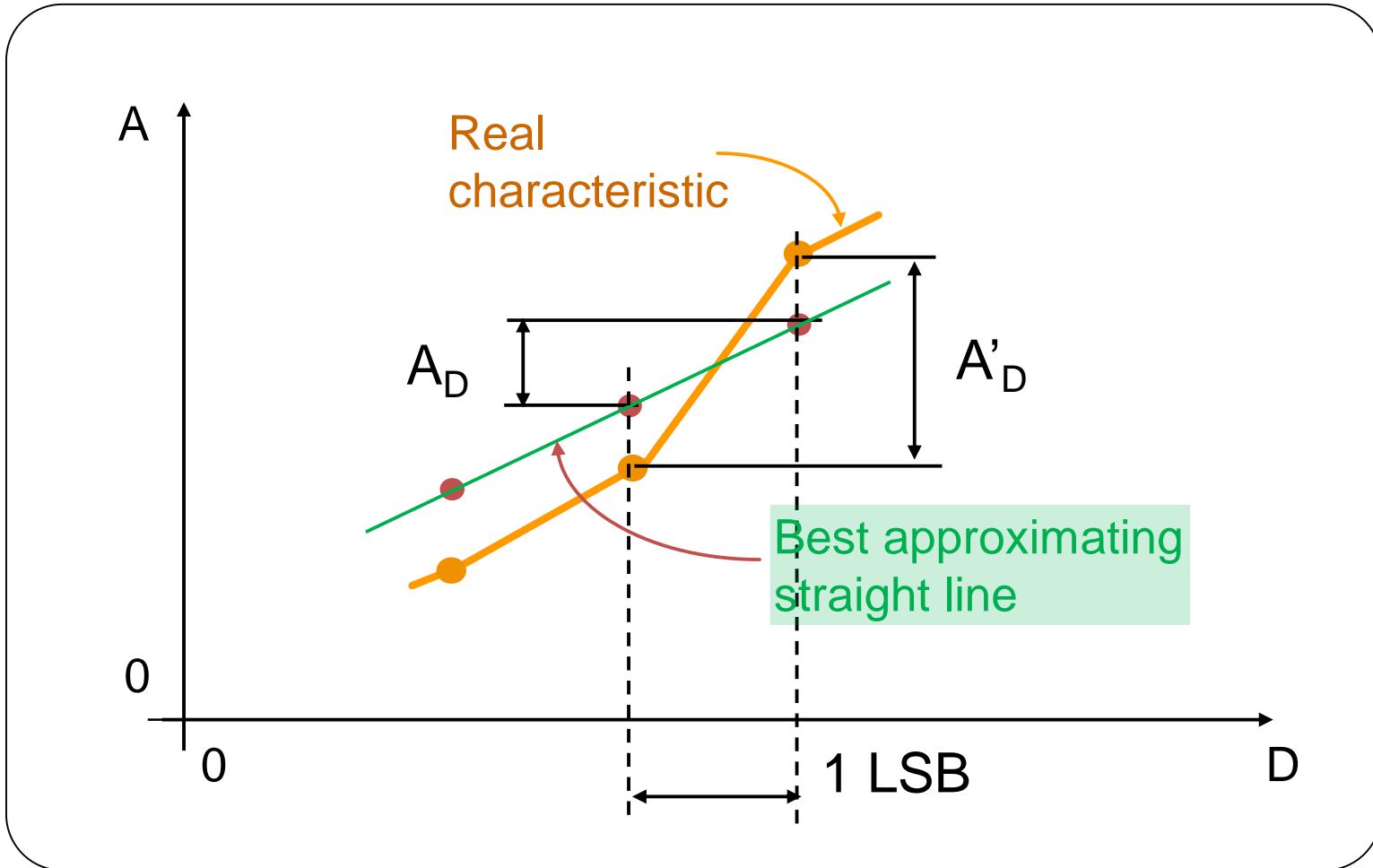




# Non-Monotonicity Error

 

# Nonlinearity Errors: Integral

 




# Differential vs. Integral Nonlinearity


- Draw the characteristic for a 3-bit DAC with
  - ◆  $\mathcal{E}_{\text{dnl}} = +1/4 \text{ LSB}$  from 000 to 011 ( $\text{MSB} = 0$ )
  - ◆  $\mathcal{E}_{\text{dnl}} = -1/4 \text{ LSB}$  from 100 to 111 ( $\text{MSB} = 1$ )
- Draw the characteristic for a 3-bit DAC with
  - ◆  $\mathcal{E}_{\text{dnl}} = +1/4 \text{ LSB}$  when  $\text{LSB} = 0$
  - ◆  $\mathcal{E}_{\text{dnl}} = -1/4 \text{ LSB}$  when  $\text{LSB} = 1$
- Compare the two cases
  - ◆ Evaluate integral nonlinearity error  $\mathcal{E}_{\text{inl}}$
  - ◆ Evaluate differential nonlinearity error  $\mathcal{E}_{\text{dnl}}$
  - ◆ Evaluate offset and gain errors

# Overall View

 

 
# Settling Time

- The D/A output takes a **settling time  $T_s$**  to reach the new value (within a given error)



 
# Glitch

- During transients, the output can temporarily reach a widely wrong value (typically 0 V or full-scale  $S$ )
- The spike is called **glitch**


 
# Where Do Glitches Come From?

- Glitches come from different switching delays of bits
  - ◆ These delays cause wrong transient states (e.g., 1111 and 0000 while changing state from 0111 to 1000)
  - ◆ These states drive the output towards 0 V or full-scale  $S$
- Glitches occur when several bits flip, e.g.,  $0111 \rightarrow 1000$ 
  - ◆ The real change is just 1 *LSB*
  - ◆ But temporary state during the transient can be 0000 or 1111
- Avoid glitches by using Gray encoding
  - ◆ Changes only one bit between adjacent states






# DAC Error Summary

- Static parameters
  - ◆ Bit number  $N$  Full scale  $S$
- Linear errors
  - ◆ Gain  $\mathcal{E}_G$  Offset  $\mathcal{E}_O$
- Nonlinearity errors
  - ◆ Integral nonlinearity  $\mathcal{E}_{inl}$  Differential nonlinearity  $\mathcal{E}_{dnl}$
- Dynamic parameters
  - ◆ Settling time  $t_S$  Glitch
- Measured as
  - ◆ % of full-scale  $S$ , absolute (mV, ...), *LSB* fraction (1,  $\frac{1}{2}$ , ...)


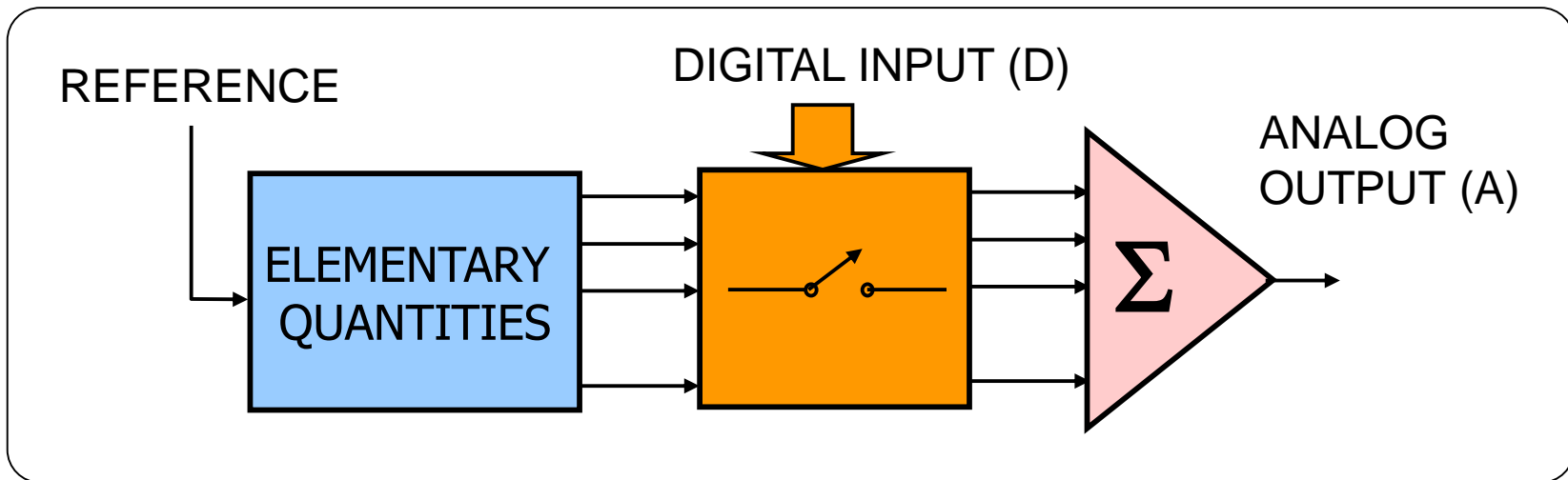
# D/A Conversion Basic Circuits

- Sum of elementary quantities controlled by  $D$



- ◆ **Uniform** elementary quantities (1, 1, 1, ...)
- ◆ **Weighted** elementary quantities (1, 2, 4, 8, ...)



# Uniform Quantities

- Sum of elementary units with the same weight (1)
- The number of units is controlled by the digital value
  - ♦  $Output = D \cdot LS$
  - ♦ Example
$$13_{10} = 1 + 1 + 1 + 1 + 1 + 1 + 1 + 1 + 1 + 1 + 1 + 1 + 1$$
- This is called **uniform element** conversion

# Weighted Quantities

- Called **weighted element** conversion
- Sum of elementary units with weights powers of 2
- Each unit controlled by the corresponding bit value (1/0)

◆  $Output = \sum_{i=0}^{N-1} 2^i \cdot D_i$

◆ Example:

◆ Weight

◆ Binary representation

◆  $9_{10} =$

$$9_{10} = 1001_2$$


$$2^3 \quad 2^2 \quad 2^1 \quad 2^0$$

$$1 \quad 0 \quad 0 \quad 1$$

$$2^3 \cdot 1 + 2^2 \cdot 0 + 2^1 \cdot 0 + 2^0 \cdot 1$$




# Uniform Currents D/A Converter

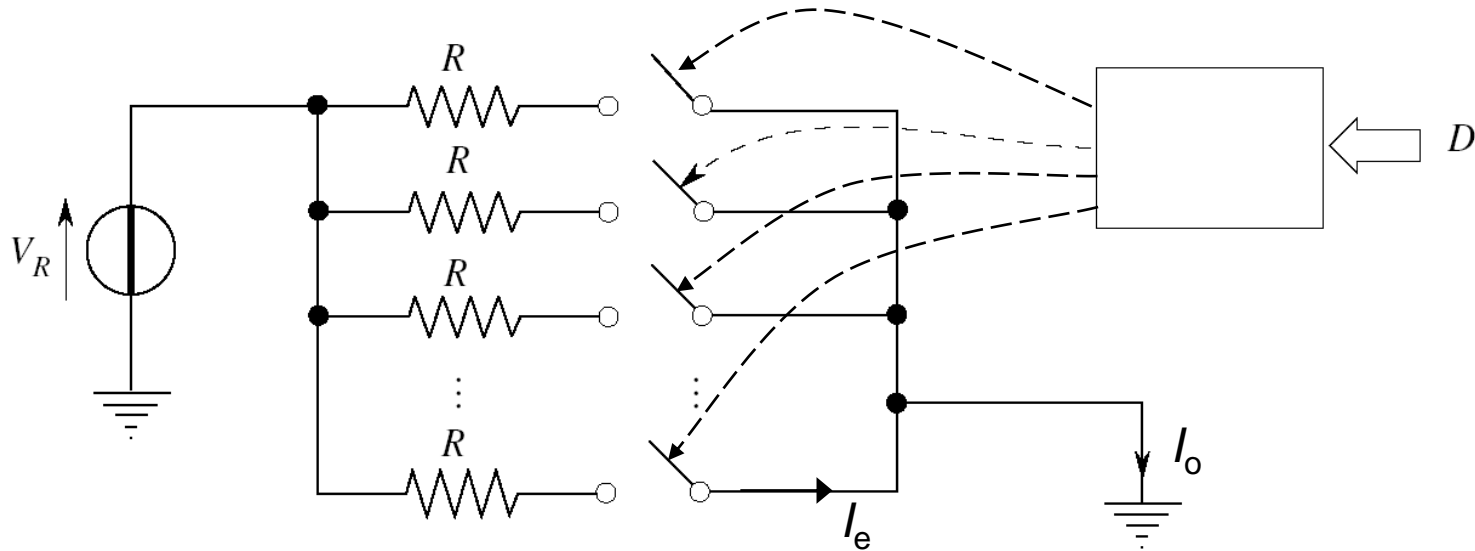

- The output current  $I_o$  is the sum of a variable number of identical elementary currents  $I_e$ , controlled by the  $N$  bits of  $D \rightarrow M = 2^N$  identical branches

 
# Uniform Voltages D/A Converters

- Output voltage  $V_O$  is the sum of elementary voltage drops on the resistor chain made of identical resistors  
→ equal voltage drops
- The tap is set by the digital value  $D$
- Also called *potentiometric DAC*



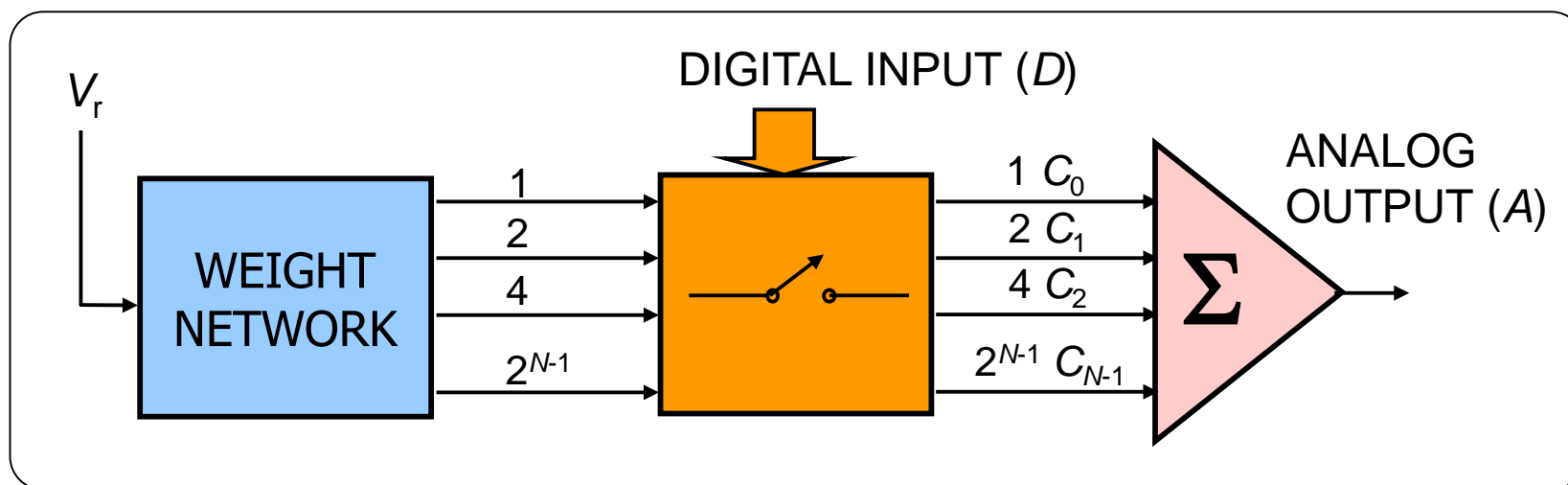
# Weighted Elements Converters

- Weighted elements (usually currents)
  - ◆ Generated from a reference (usually a voltage  $V_r$ )
  - ◆ Using a **weight network**
  - ◆ Connected to adder through switches controlled by the bits  $C_i$  of  $D$


 
# Weighted Currents D/A Converters


- Output current  $I_o$  is the sum of weighted elementary currents  $I_i$  (weight ratio 2) controlled by  $D$
- $N$  bits  $\rightarrow N$  weighted branches



# Weighted Resistor D/A Converter

- Same circuit, with switches steering the currents towards nodes at the same potential (GND)

- ◆ Current switches

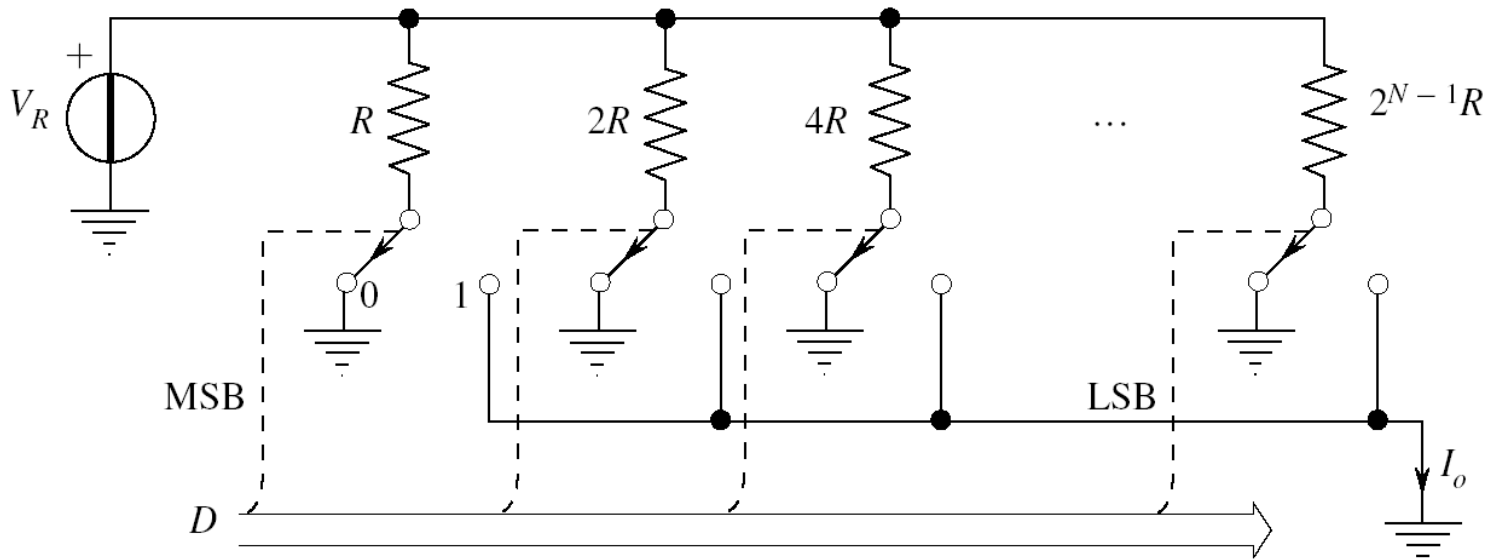


- ◆ High dynamic range for resistors ( $2^{N-1}$ )




# Voltage and Current Switches

- Linear passive networks: **reciprocity**
  - ◆ If input and output are exchanged, same  $I(V)$  relation

$$I_1 = D(V_1)$$

 


$$I_2 = D(V_2)$$

 


# Voltage/Current Switch Comparison

Current switches  
(both nodes 0 V)

 


 Voltage switches  
(nodes at  $V_R$  or 0 V)



# Ladder Network (1)

- Splitting a current in two equal parts

 


$$I = V_R / 2R$$



# Ladder Network (2)


- Repeat the splitting

 

$$I = V_R / 2R$$

# Ladder Network (3)

- Continue splitting (4 currents)

 

$$I = V_R / 2R$$


$$I_i = I / 2^i$$



# Benefits of Ladder Networks


- The ladder network is fully modular
  - ◆ Any number of bits
- Uses only resistors of value  $R$  and  $2R$ 
  - ◆ Same technology, same behavior (temp, aging, ...)
  - ◆ Precise current ratio
- D/A converter with ladder network
  - ◆ Branch currents can be sent to ground/output summing node using current switches
  - ◆ Convert output to voltage with Norton/Thevenin conversion
  - ◆ Reciprocal network with V-switches feasible

# Ladder Network With I-Out and I-SW

 

I-switches drive the current  
between equipotential nodes


# Ladder Network with V-Out and V-SW

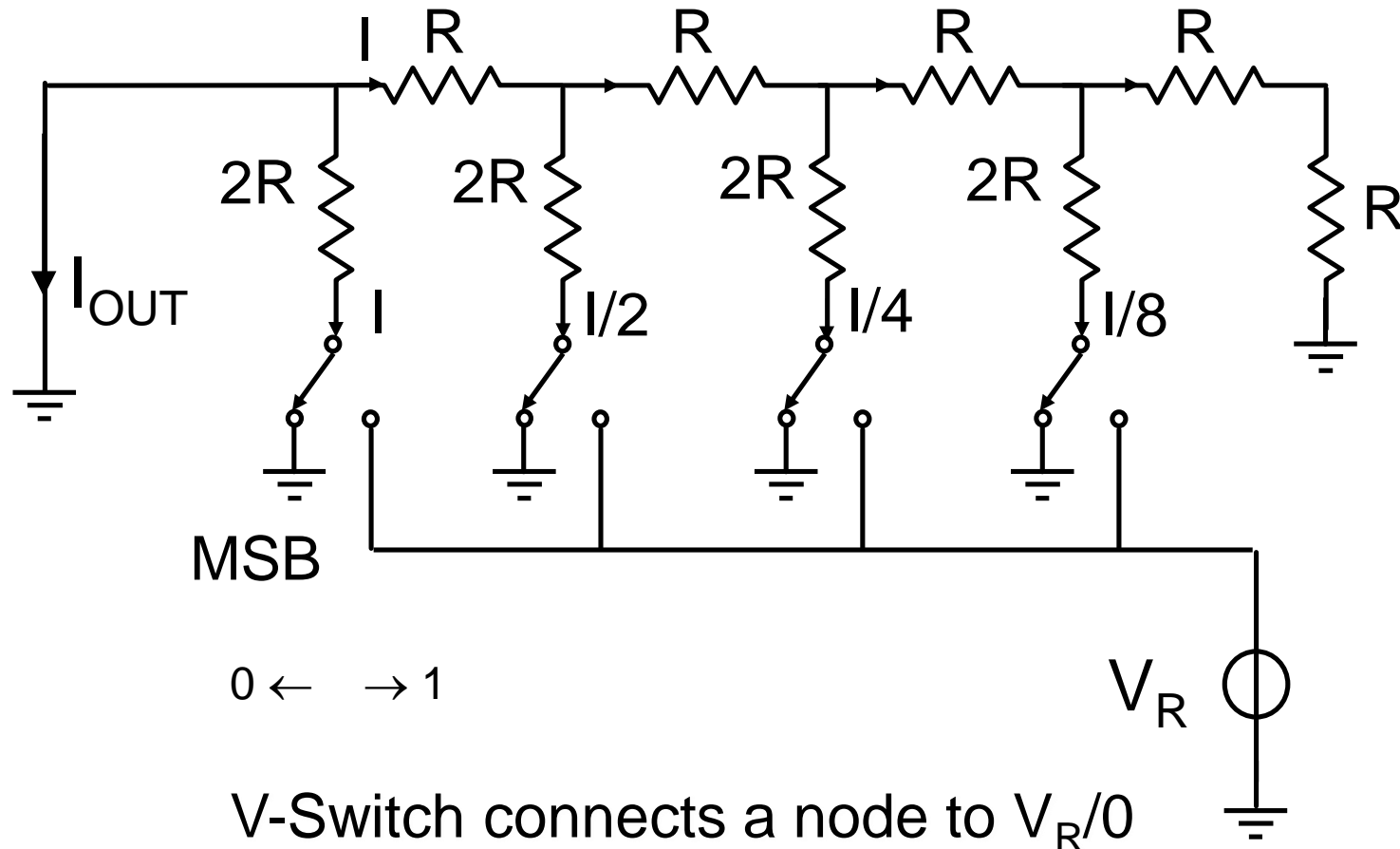





# Ladder Network – Example

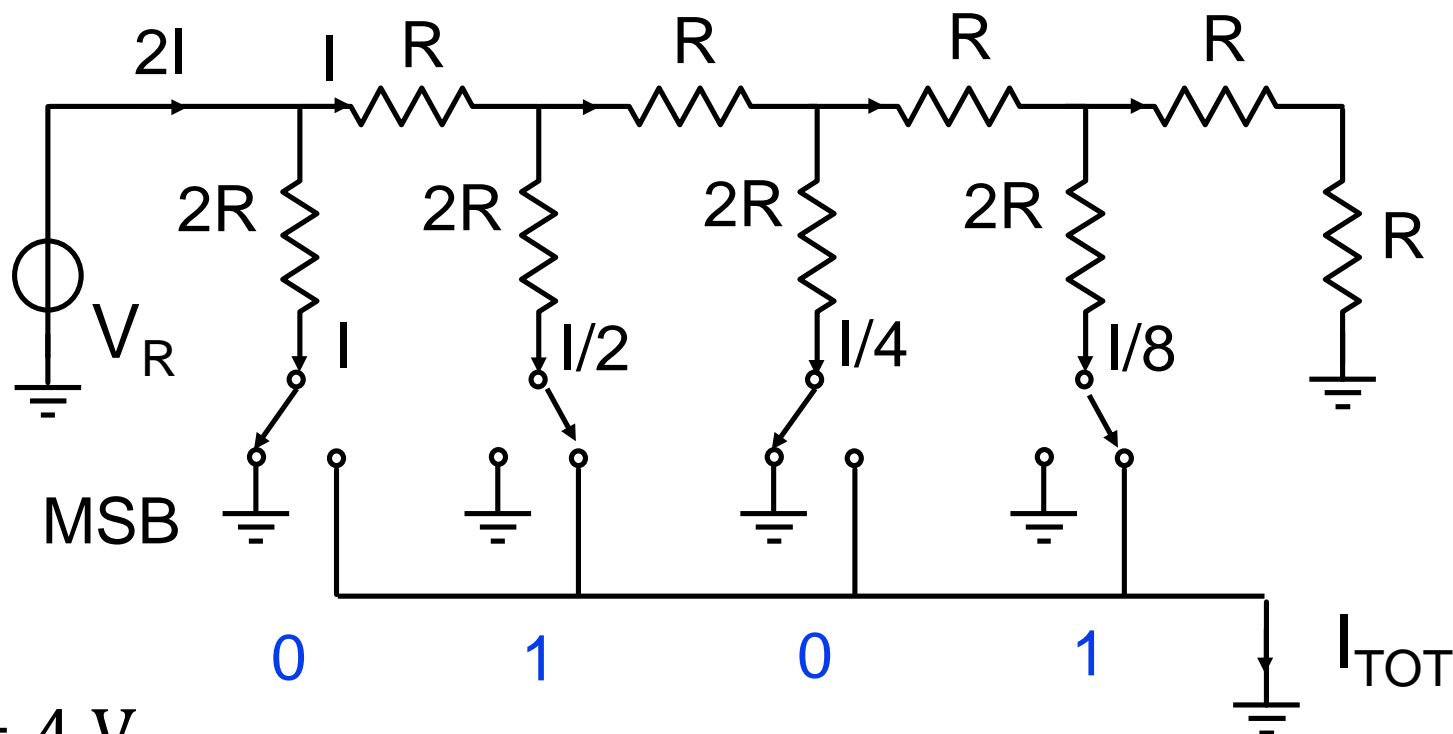

$$V_R = 4 \text{ V}$$


$$R = 10 \text{ k}\Omega$$

$$I = \frac{V_R}{2R} = 0.2 \text{ mA} \quad 0101 \rightarrow I_{TOT} = \frac{I}{2} + \frac{I}{8} = \dots$$

$$0111 \rightarrow I_{TOT} = \dots$$
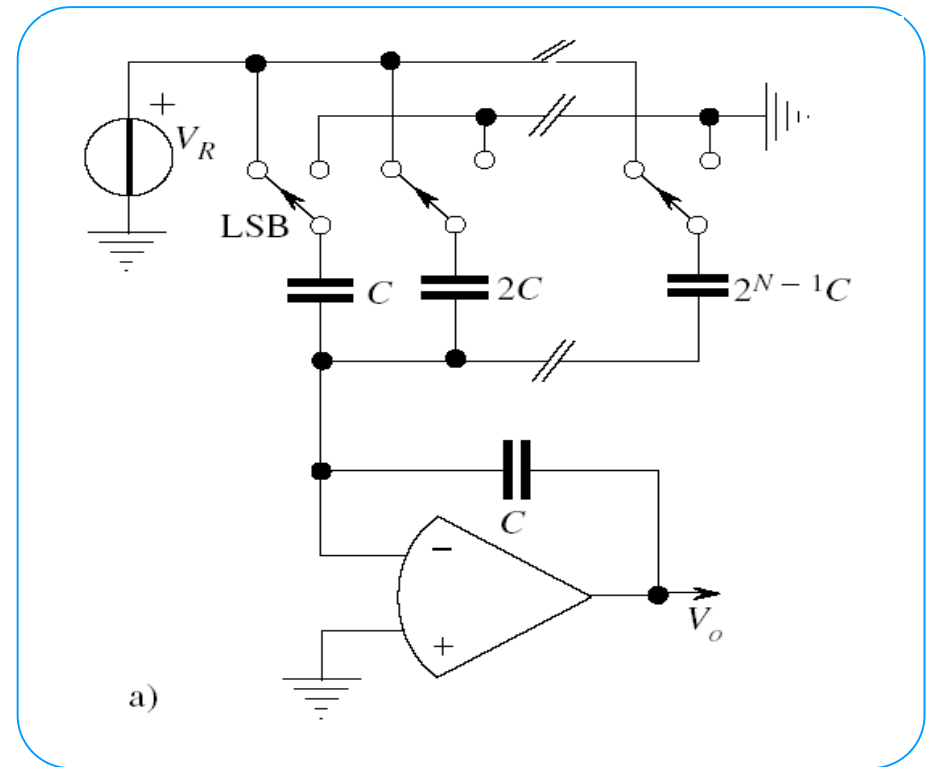
# Capacitive Weighted Networks

- Can add electrical charges (instead of electrical currents)
- Weighted network with electrical capacitances (instead of resistors)
- Conversion accuracy depends on accuracy of capacitance ratios
  - ◆ There are also C-2C ladder networks
- Low power consumption





# Sources of Linear Errors

- *Gain error*
  - ◆ Changes in  $V_r$
  - ◆ Systematic error in the weight network
- *Offset error*
  - ◆ Leakage current of switches
  - ◆ Offset of operational amplifier
- These errors do not depend on the value  $D$ 
  - ◆ A unique correction value works for the whole dynamic range
  - ◆ Can be corrected



# Branch Errors

- Equivalent resistance of switches ( $R_{ON}$ )
  - ◆ Modifies the total branch resistance
  - ◆ Same effects as weight resistor error (tolerance)
  - ◆ Modifies the branch current
  - ◆ If  $\Delta R/R$  is constant across branches  $\rightarrow$  *gain* error
- Leakage current of switches ( $I_{off}$ )
  - ◆ Some output current even for  $D = 0$
  - ◆ If it is constant: offset error
  - ◆ Depends on temperature



# Errors in Weighted D/A Networks


- Each branch contributes to output when the corresponding bit is 1
  - ◆ *MSB* contributes over  $S/2$ ,  $MSB - 1$  over  $S/4$ , ...
- Branches have different weights
  - ◆ *MSB* weight is  $1/2$ ,  $MSB - 1$  weight is  $1/4$ , ...
- $Out_{\text{error}} = branch_{\text{error}} \times branch_{\text{weight}}$ 
  - ◆ Same % error in different branches  $\rightarrow$  *different* output errors
  - ◆ Higher effects on *MSBs*
- *MSB* branches must be more accurate
- Affected parameter: **differential nonlinearity**



# Errors in Weighted D/A – Example

- Error on MSB branch
  - ◆ Shifted upper half of characteristic
  - ◆ Branch error 10% → output error 5%
- Error on MSB–1 branch
  - ◆ Shifted odd quarters (1, 3) of characteristic
  - ◆ Branch error 10% → output error 2.5%
- Error on MSB–2 branch
  - ◆ Branch error 10% → output error 1.25%
- ...
 
# Errors in Weight Network: $MSB$ , $MSB - 1$






# Errors in Uniform D/A Networks

- $Out_{error} = branch_{error} \times branch_{weight}$ 
  - ◆ Each branch has the same weight (1 *LSB*)
  - ◆ The *same* % error in any branch causes the *same* output error
  - ◆ Intrinsically *monotonic output*
    - Sum of elements with the same sign
- All branches can have the same precision
- Errors of all branches sum at the output
- Critical parameter: **integral nonlinearity**


 
# Uniform Elements D/A: Example

- Potentiometric converter with systematic errors in resistor chain
  - ◆  $-\Delta R$  in the upper half,  $+\Delta R$  in the lower half
  - ◆ High **integral nonlinearity**



The voltage divider is unbalanced. Mid node voltage lower than  $S/2$

Intermediate nodes have proportional errors.




# Error Summary

- Gain error
  - ◆ Changes of reference voltage  $V_r$
  - ◆ Systematic errors in the weight network
- Offset error
  - ◆ Offsets of the operational amplifier
  - ◆ Leakage current of switches
- Nonlinear errors
  - ◆ Random errors in the weight network ( $N_{LD}$ )
  - ◆ Systematic error in the uniform network ( $N_{LI}$ )
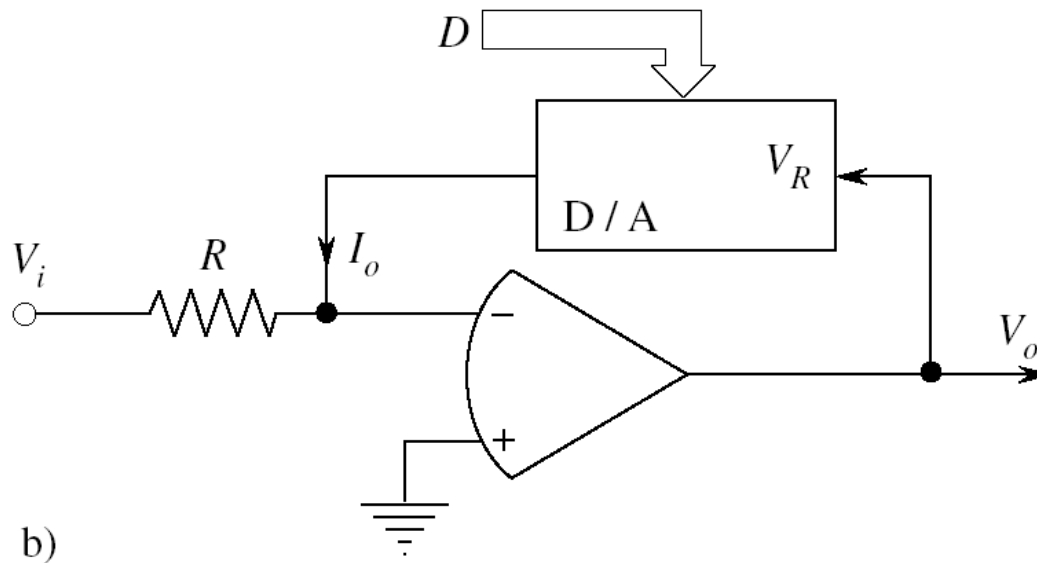
# Gain Control With a DAC

- The DAC is used as feedback (or input) transconductance
- The D/A must allow  $V_R$  sign inversion:  $I_O = KDV_R$



b)

$$\frac{V_i}{R} = KDV_o \Rightarrow V_o = \frac{V_i}{RKD}$$



# Lecture D2: Review Questions

- How can be corrected a D/A offset and gain errors?
- Can nonlinearity errors be corrected?
- What is a non-monotonicity error?
- Describe the transient behavior of a D/A converter.
- How can we modify the circuit to avoid glitches?
- What are the disadvantages of weighted networks?
- What are the advantages of the ladder networks?
- What weighted network error may lead to a high differential error?



# Exercise 1

- Draw the schematic of a 6-bit D/A converter with weighted resistances and voltage output.
- Defined the  $R$  values for  $V_r = 5\text{ V}$  and full scale  $-10\text{ V}$  (assume feedback resistor of the amplifier  $R_F = 10\text{ k}\Omega$ ).
- Determine the two max absolute output errors (in V) for 5% tolerance resistors in the MSB and in LSB branches.
- Define the required tolerance for the resistors for a max total error of  $\frac{1}{2}$  LSB, if each branch has the same absolute error.




# Exercise 1

- Draw the schematic of a 6-bit D/A converter with weighted resistances and voltage output.
 
# Exercise 1: Schematic

- Draw the schematic of a 6-bit D/A converter with weighted resistances and voltage output.





# Exercise 1

- Defined the  $R$  values for  $V_r = 5\text{ V}$  and full scale  $-10\text{ V}$  (assume feedback resistor of the amplifier  $R_F = 10\text{ k}\Omega$ ).




# Exercise 1

- Defined the  $R$  values for  $V_R = 5\text{ V}$  and full scale  $-10\text{ V}$  (assume feedback resistor of the amplifier  $R_F = 10\text{ k}\Omega$ ).
- Full scale (max  $V_O$  magnitude) when all bits are 1

$$\diamond R_{eq} = R \parallel 2R \parallel \dots \parallel 32R = \frac{32}{63} R$$

$$\diamond V_O = -V_R \frac{R_F}{R_{eq}} \Rightarrow R_{eq} = -R_F \frac{V_R}{V_O}$$
 
$$\diamond \frac{32}{63} R = -10\text{ k}\Omega \cdot \frac{5\text{ V}}{-10\text{ V}} \Rightarrow R = \mathbf{9.84\text{ k}\Omega}$$






# Exercise 1

- Determine the two max absolute output errors (in V) for 5% tolerance resistors in the MSB and in LSB branches.
 
# Exercise 1

- Determine the two max absolute output errors (in V) for 5% tolerance resistors in the MSB and in LSB branches.
- Branches with errors are activated

$$\begin{aligned}
 \blacklozenge V_{O_{\text{nom}}}^{\text{MSB}} &= -V_R \frac{R_F}{R} = -5 \text{ V} \cdot \frac{10 \text{ k}\Omega}{9.84 \text{ k}\Omega} = -5.08 \text{ V} \\
 \blacklozenge V_{O_{\text{min}}}^{\text{MSB}} &= -V_R \frac{R_F}{R(1+5\%)} = -4.84 \text{ V} \\
 \blacklozenge V_{O_{\text{max}}}^{\text{MSB}} &= -V_R \frac{R_F}{R(1-5\%)} = -5.35 \text{ V} \\
 \blacklozenge V_{O_{\text{nom}}}^{\text{LSB}} &= -V_R \frac{R_F}{32R} = -5 \text{ V} \cdot \frac{10 \text{ k}\Omega}{32 \cdot 9.84 \text{ k}\Omega} = -0.159 \text{ V} \\
 \blacklozenge V_{O_{\text{min}}}^{\text{LSB}} &= -V_R \frac{R_F}{32R(1+5\%)} = -0.151 \text{ V} \\
 \blacklozenge V_{O_{\text{max}}}^{\text{LSB}} &= -V_R \frac{R_F}{32R(1-5\%)} = -0.167 \text{ V}
 \end{aligned}$$





# Exercise 1

- Define the required tolerance for the resistors for a max total error of  $\frac{1}{2}$  LSB, if each branch has the same absolute error.

# Exercise 1

- Define the required tolerance for the resistors for a max total error of  $\frac{1}{2}$  LSB, if each branch has the same absolute error.

- Each branch contributes

$$\frac{1/2 \text{ LSB}}{6} = \frac{1}{12} \text{ LSB} = \frac{1}{12} V_R \frac{R_F}{32 R}$$

- MSB branch contribution

$$\diamond \frac{1}{12} V_R \frac{R_F}{32 R} = V_R \frac{R_F}{R} - V_R \frac{R_F}{R + \Delta R}$$

$$\diamond R + \Delta R = R \frac{12 \cdot 32}{12 \cdot 32 - 1} \Rightarrow \frac{\Delta R}{R} = \frac{1}{12 \cdot 32 - 1} = 0.26 \%$$

- MSB-1 branch contribution

$$\diamond \frac{1}{12} V_R \frac{R_F}{32 R} = V_R \frac{R_F}{2R} - V_R \frac{R_F}{2R + \Delta R}$$

$$\diamond 2R + \Delta R = 2R \frac{6 \cdot 32}{6 \cdot 32 - 1} \Rightarrow \frac{\Delta R}{2R} = \frac{1}{6 \cdot 32 - 1} = 0.52 \%$$

- MSB-2 branch contribution...

