



Applied Electronics

C3 – Interconnections with transmission lines

- Incident wave switching
- Reflected wave switching
- Delays and skew
- Terminations




Lecture C3: Interconnections With Transmission Lines

- Incident Wave and Reflected Wave Switching
- Delays and skew
- Terminations
- References:
 - ◆ D. Del Corso: Interconnections for high-speed...: lectures 1, 2

Transmission time and skew

- **Transmission time t_{TX}** is the **delay** until the signal crosses receiver threshold (V_T). Depends on:
 - ◆ Interconnection parameters
 - ◆ Driver and Receiver parameters
 - ◆ Operating conditions (V_{DD} , temperature, ...)
 - ◆ Receiver position on the line
- **Skew t_K** (misalignment) comes from t_{TX} variations
- Objectives
 - ◆ **Minimize delay** and variations (low skew)
 - ◆ Avoid **multiple crossings**
 - ◆ Reduce **power consumption**

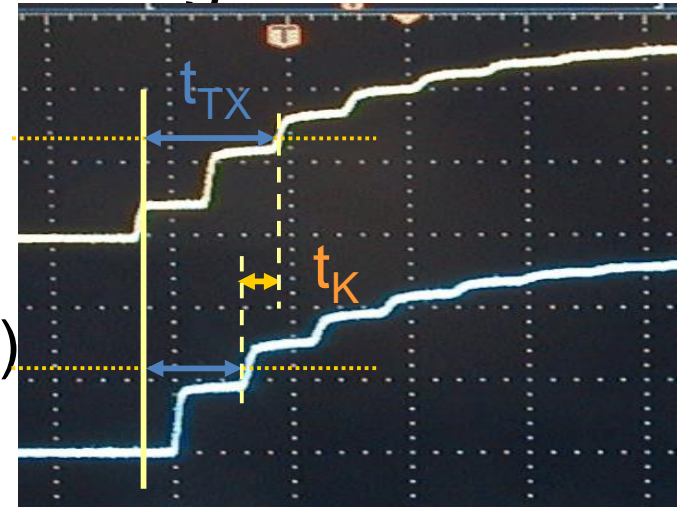

Effects of skew


- Skew **changes the temporal relationships** between signals

◆ Set-up time, t_{SU} , is reduced by t_K

$$t_1 = t_0 + t_{TXmin} + t_K$$

$$t_2 = t_0 + t_{SU(D)} + t_{TXmin}$$
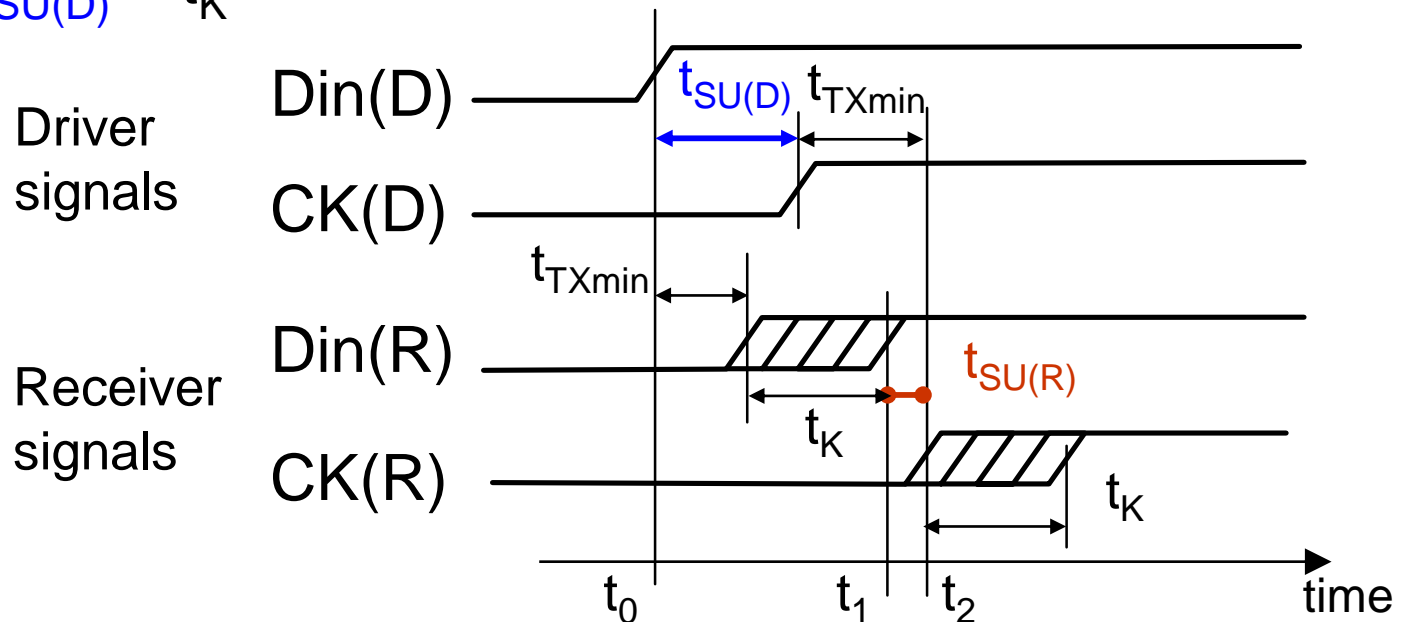
$$t_{SU(R)} = t_2 - t_1 = t_{SU(D)} - t_K$$





What are the causes of skew?

- Basic problem: timing misalignment due to **skew**, t_K , from variations in the transmission time: $t_K = t_{TXmax} - t_{TXmin}$
- Evaluate and check skew, $t_K \rightarrow$ **signal integrity** problem
 - ◆ Analysis of timing constraints of logic circuits \rightarrow **this course**
 - ◆ Signal propagation mechanisms \rightarrow electromagnetic fields
- **Parameters** that affect **transmission** t_{TX} and **skew** t_K times
 - ◆ TX and RX parameters
 - V_H , V_L , V_T , ...
 - ◆ Propagation
 - Reflections, terminations, discontinuities, crosstalk
 - ◆ Load, especially capacitive loads
 - ◆ Ground bounce and switching noise



Connection topologies

- **Point-to-point** connections
 - ◆ Driver at one end (left) → near side, near-end
 - ◆ Receiver at the other end (right) → remote side, far-end
 - ◆ Propagation conditions are **well defined**
- **Bus** connections
 - ◆ **Multi-point** communication structures
 - ◆ Driver at **one end** or at an **intermediate** point
 - ◆ **Several** receivers, in **various** positions
 - Variable load, discontinuity
 - Variable propagation parameters


Reference structure

- **Driver** circuit at far left (near-end)
- Transmission **line** with parameters Z_{∞} , t_p
- A **termination** at far right (far-end)
- Receivers in any position
 - ◆ At the driver, at the termination (near/far end), intermediate, ...



Skew overall (or global)

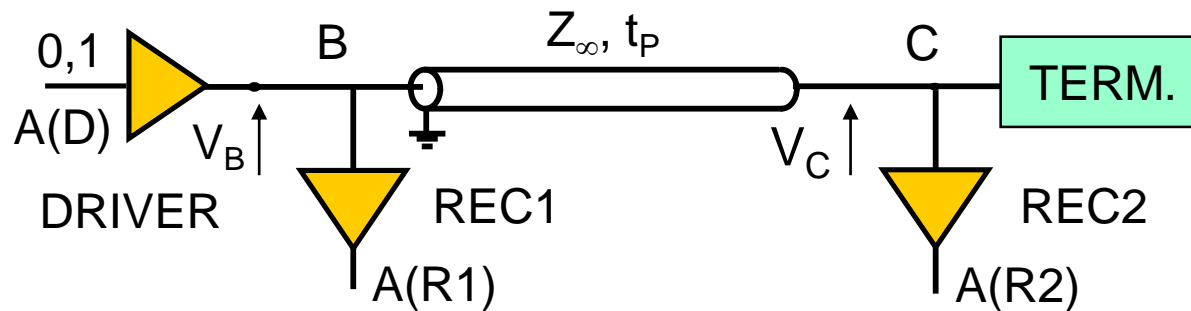- The overall skew t_{KC} includes variations of t_{TX} due to
 - ◆ Parameter dispersion (V_T , C_P , ...)
 - ◆ Different receiver positions (near, far, intermediate)
- Typically, it is not relevant to the protocols (next lecture)
- Overall skew between all receivers
 - ◆ $t_{KC} = \max(t_{TXmaxi}) - \min(t_{TXminj})$




Local skew

- Local skew, t_K , includes variations of t_{TX} caused *only* by parameter dispersion (V_T , C_P , ...)
 - It is the skew between different ports of a single receiver (card)
- Local skew for receiver i:
 - $t_K = \max(t_{TXmaxi}) - \min(t_{TXmini})$



Local skew

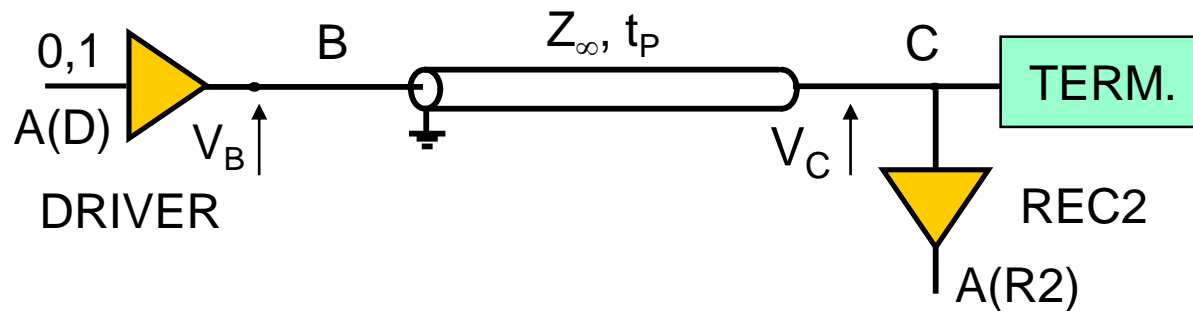- Local skew, t_K , includes variations of t_{TX} caused *only* by parameter dispersion (V_T , C_P , ...)
 - It is the skew between different ports of a single receiver (card)
- Local skew for receiver i:
 - $t_K = \max(t_{TXmaxi}) - \min(t_{TXmini})$





First voltage step

- Driver transition: **first voltage step**
 - ◆ Causes an incident wave that propagates along the line
- On transition, the driver is loaded with Z_∞
 - ◆ The amplitude of the first step depends on the ratio R_O / Z_∞
- The termination can **reflect** the signal
 - ◆ The signal on the line is the sum of the incident wave and the reflections
- Analysis for three cases
 - ◆ **Low** R_O / Z_∞ : ($R_O < Z_\infty$) → fast buses
 - ◆ **High** R_O / Z_∞ : ($R_O > Z_\infty$) → slow buses
 - ◆ Driver **adapted**: $R_O = Z_\infty$ → good compromise


High Current Driver: Low $R_O / Z_\infty \rightarrow$ IWS

- Low $R_O / Z_\infty \rightarrow R_O < Z_\infty \rightarrow$ **high** first step
 - ◆ Receiver threshold is crossed by the first step
 - ◆ Incident Wave Switching (IWS), low t_{TX} , **fast**
 - Used in **high-speed** buses
 - ◆ $\Gamma_D < 0 \rightarrow$ negative reflection at the driver
 - Oscillations \rightarrow possible multiple crossings of the threshold
 - **Requires termination** to the far end (suitable for buses)
 - The termination dissipates energy

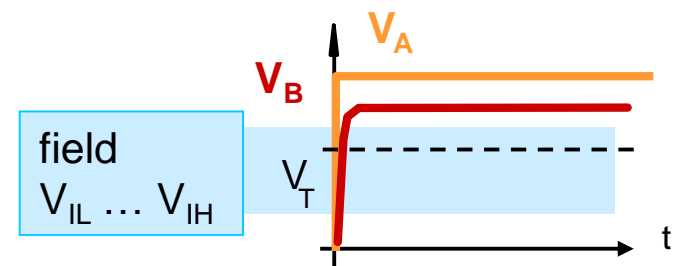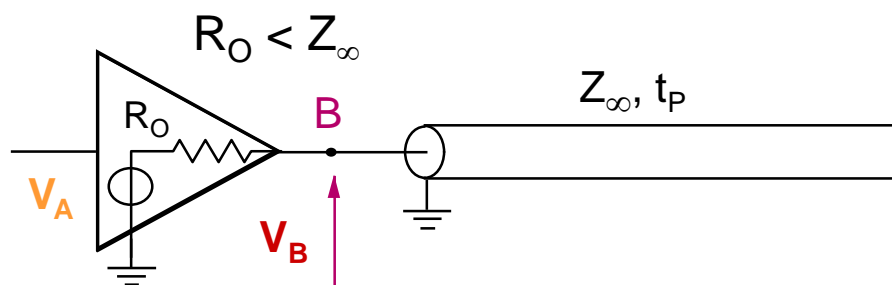


Adapted driver: $R_O = Z_\infty$

- $R_O = Z_\infty \rightarrow$ driver-side adaptation
 - ◆ Adaptation at the Near End (possible series termination)
 - ◆ First step amplitude equal to half of the steady state voltage
 - ◆ The threshold V_T is crossed by the first reflection
 - Reflected Wave Switching (RWS)
- $\Gamma_D = 0 \rightarrow$ no reflection at the driver end
 - ◆ Suitable for point-to-point connections
- Compared to IWS
 - ◆ Slower
 - ◆ Lower consumption

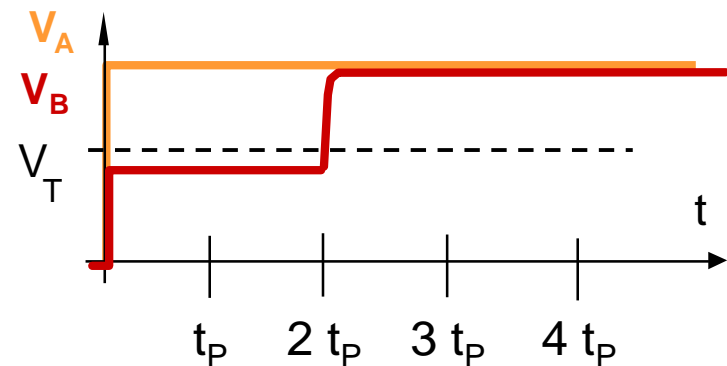


Switching on the reflected wave

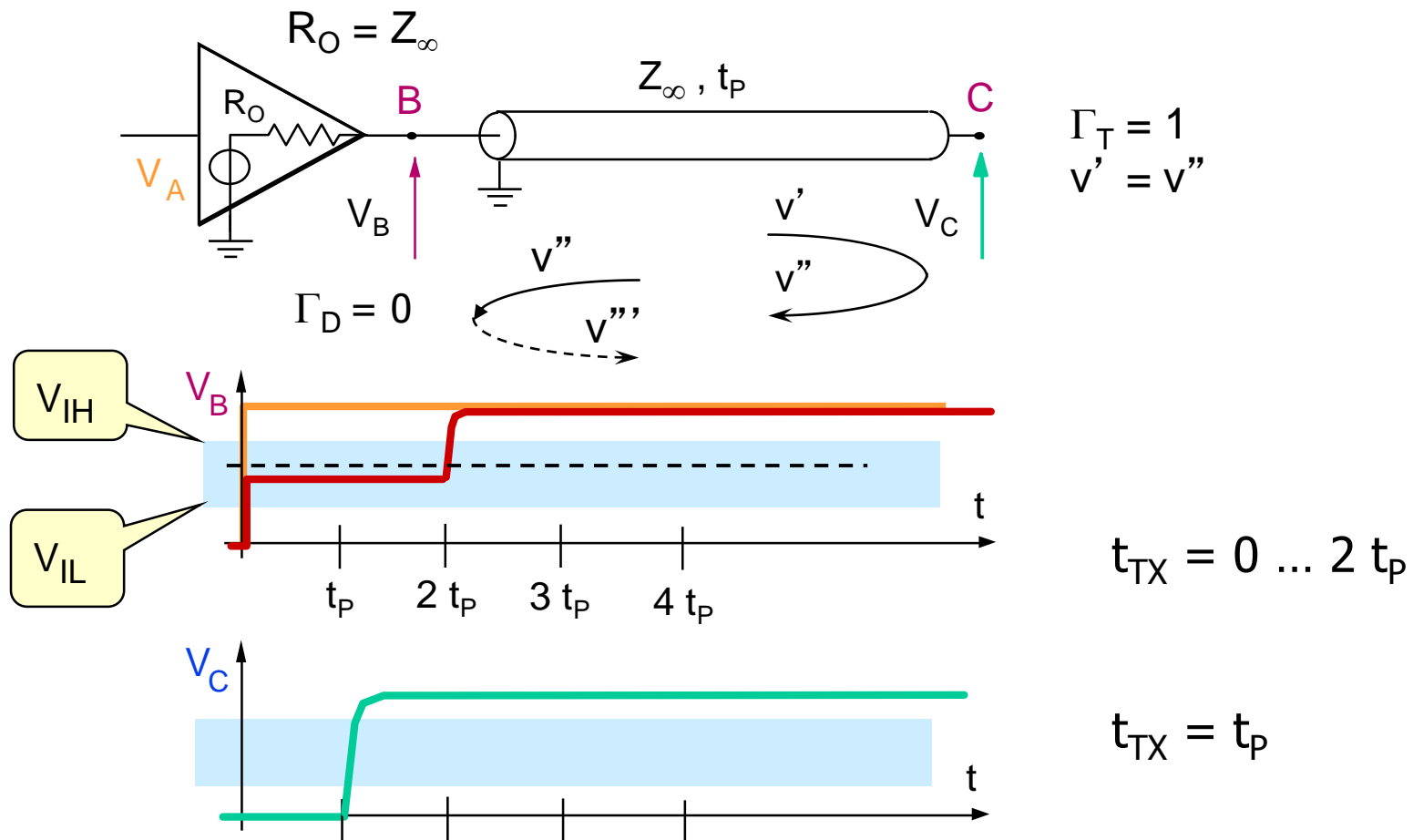

Low current driver: high R_O / Z_∞

- High R_O / Z_∞ ratio ($R_O > Z_\infty$)
 - ◆ Lower first voltage step
 - ◆ The first step cannot cross the threshold
- $\Gamma_T > 0 \rightarrow$ positive reflection on termination
- $\Gamma_D > 0 \rightarrow$ positive reflection on the driver
 - ◆ All reflected waves have the **same polarity**
 - ◆ Slow and **monotonous** change, no oscillations
 - ◆ Thresholds crossed after multiple reflections
- High t_{TX} , **slow** operation

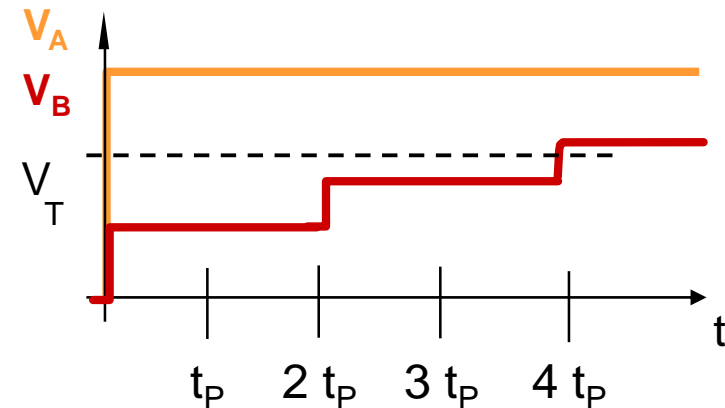



Effects of capacitive load

- A capacitive load on the line
 - ◆ Reduces the characteristic impedance Z_{∞}
 - ◆ Reduces the propagation speed P
 - ◆ Reduces the first step amplitude
 - ◆ Increases dynamic power consumption P_D
- Must **limit capacitive loads**
 - ◆ Separation buffers
 - ◆ Surface Mount Devices (SMD)
 - ◆ Reduce length of PCB traces
 - ◆ Careful layout


$$Z_{\infty} = \sqrt{\frac{L}{C}}$$

$$P = \sqrt{\frac{1}{LC}}$$


$$P_D = F V^2 C$$

Multi-point connection (bus)

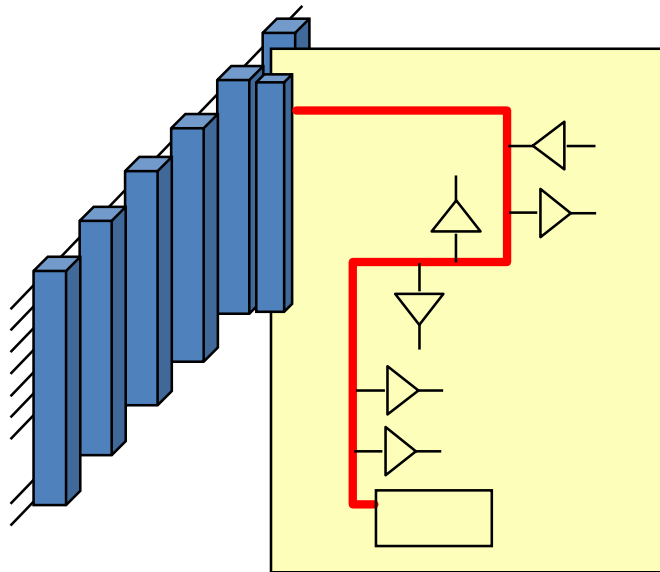- Limit the stubs and capacitive loads
 - ◆ **Do not** connect **directly** the bus to the circuit boards
 - ◆ Use **buffers** or **transceivers** (close to the connector)



Wrong – high C

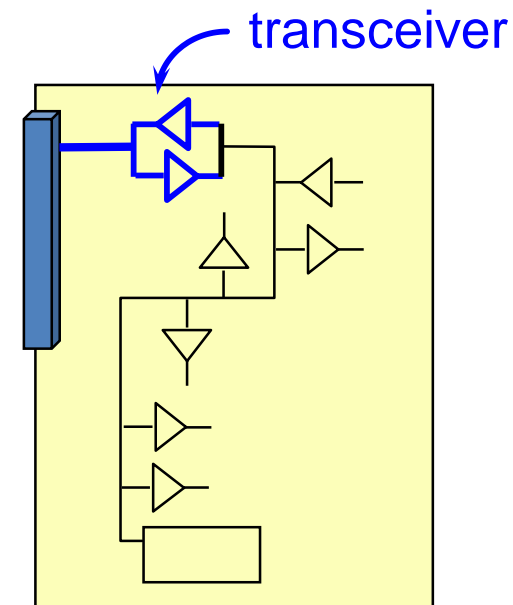

Correct – low C



Summary

- Incident Wave Switching

- ◆ $t_{TXmin} = 0$, $t_{TXmax} = t_P$, $t_K = t_P$ (between RXs at line ends)
- ◆ Fast
- ◆ Static energy (dissipation in the terminations)

- Reflected Wave Switch (first reflection)

- ◆ $t_{TXmin} = t_P$, $t_{TXmax} = 2 t_P$, $t_K = t_P$ (between RXs at line ends)
- ◆ Average speed, low power
- ◆ Best for point-to-point connections

- Multiple Reflections Switching

- ◆ $t_{TXmax} = N \cdot 2 t_P$, N depends on voltage division at driver
- ◆ Slow



Objectives of protocols at cycle level

- Registers have timing specifications (setup and hold)
- Electrical parameter propagation and spread change the temporal relationships (→ skew)
 - ◆ The skew modifies the set-up and hold times
 - ◆ It can cause metastability in flip-flops and registers
- To achieve high speeds
 - ◆ Minimize skew → [this lecture](#)
 - ◆ Ensure timing specifications: [cycle level protocols](#)
- [Cycle-level](#) protocols must guarantee correct information transfer despite [skew-induced variations of temporal relations](#)



Exercise C3.1: transmission delay evaluation

- A point-to-point interconnection has:

- ◆ $Z_{\infty} = 70 \, \Omega$, $t_p = 10 \, \text{ns}$
- ◆ Supply: $V_{AL} = 5 \, \text{V}$
- ◆ Receiver: $V_{IHmin} = 3 \, \text{V}$, $V_{IHmax} = 4 \, \text{V}$

- Combinations for the other parameters

	a	b	c	d	e	f
$R_O \, [\Omega]$	100	100	50	50	10	10
$R_T \, [\Omega]$	∞	200	200	100	100	10

- For a low-to-high transition in the different cases

- ◆ Draw the qualitative evolution of the driver and receiver signals
- ◆ Calculate and compare the transmission time, t_{TX} , and skew, t_K

Exercise C3.1: transmission delay evaluation

- Driver-end (near-end) reflection coefficient

$$\diamond \Gamma_D = \frac{R_O - Z_\infty}{R_O + Z_\infty}$$

- Receiver-end (far-end) reflection coefficient

$$\diamond \Gamma_T = \frac{R_T - Z_\infty}{R_T + Z_\infty}$$

- Steady state line voltage


$$V_{\text{steady}} = \frac{R_T}{R_O + R_T} V_A$$

- Incident wave


$$v_1 = V_B(0) = \frac{Z_\infty}{R_O + Z_\infty} V_A$$

- First reflected wave
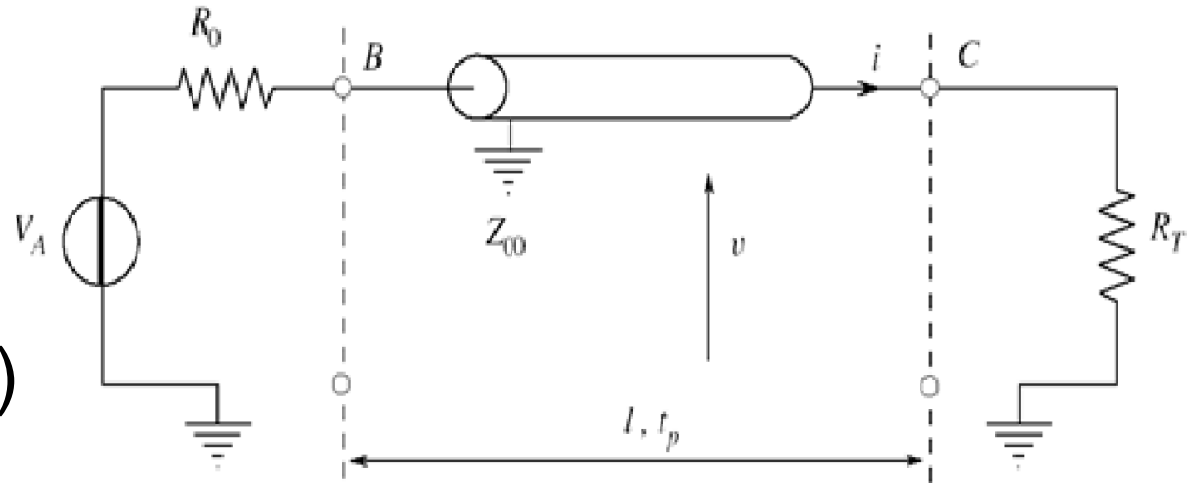
$$v_2 = \Gamma_T v_1 = \frac{R_T - Z_\infty}{R_T + Z_\infty} v_1$$



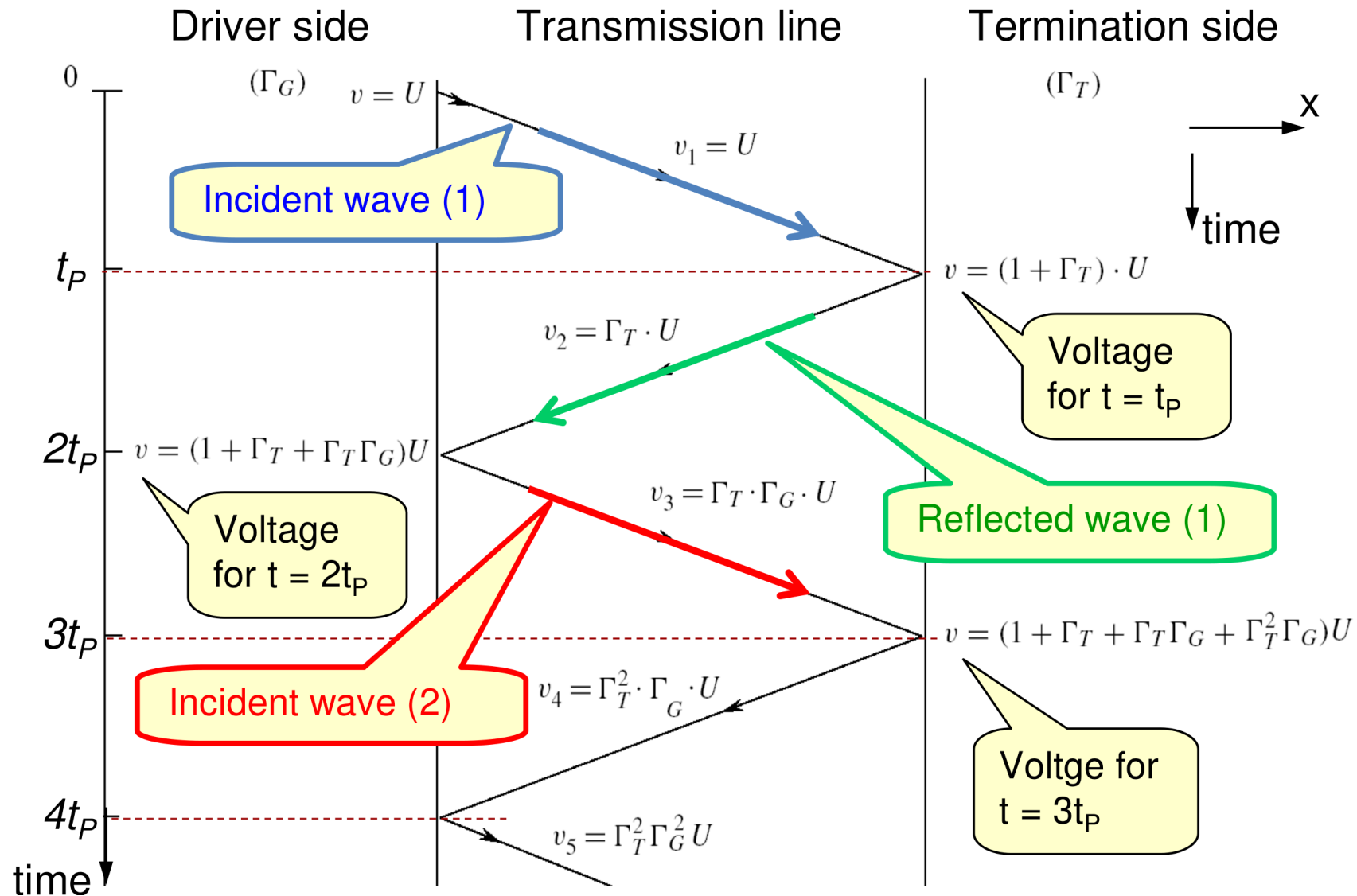Exercise C3.1: transmission delay evaluation: waves on the lattice diagram






Exercise C3.1: transmission delay evaluation: (a) – calculations

- $\Gamma_D = \frac{R_O - Z_\infty}{R_O + Z_\infty} = \frac{100 \, \Omega - 70 \, \Omega}{100 \, \Omega + 70 \, \Omega} = \frac{30 \, \Omega}{170 \, \Omega} = 0.18 > 0$
- $\Gamma_T = \frac{R_T - Z_\infty}{R_T + Z_\infty} = \frac{(R_{T \rightarrow \infty}) - 70 \, \Omega}{(R_{T \rightarrow \infty}) + 70 \, \Omega} = 1 > 0$
- $V_{\text{steady}} = \frac{R_T}{R_O + R_T} V_A = \frac{(R_{T \rightarrow \infty})}{100 \, \Omega + (R_{T \rightarrow \infty})} \cdot 5 \, \text{V} = 5 \, \text{V}$
- $v_1 = V_B(0) = \frac{Z_\infty}{R_O + Z_\infty} V_A = \frac{70 \, \Omega}{100 \, \Omega + 70 \, \Omega} \cdot 5 \, \text{V} = 2.06 \, \text{V}$
- $v_2 = \Gamma_T v_1 = 1 \cdot 2.06 \, \text{V} = 2.06 \, \text{V}$
- $v_3 = \Gamma_D \Gamma_T v_1 = 0.18 \cdot 1 \cdot 2.06 \, \text{V} = 0.37 \, \text{V}$
- $v_4 = \dots$



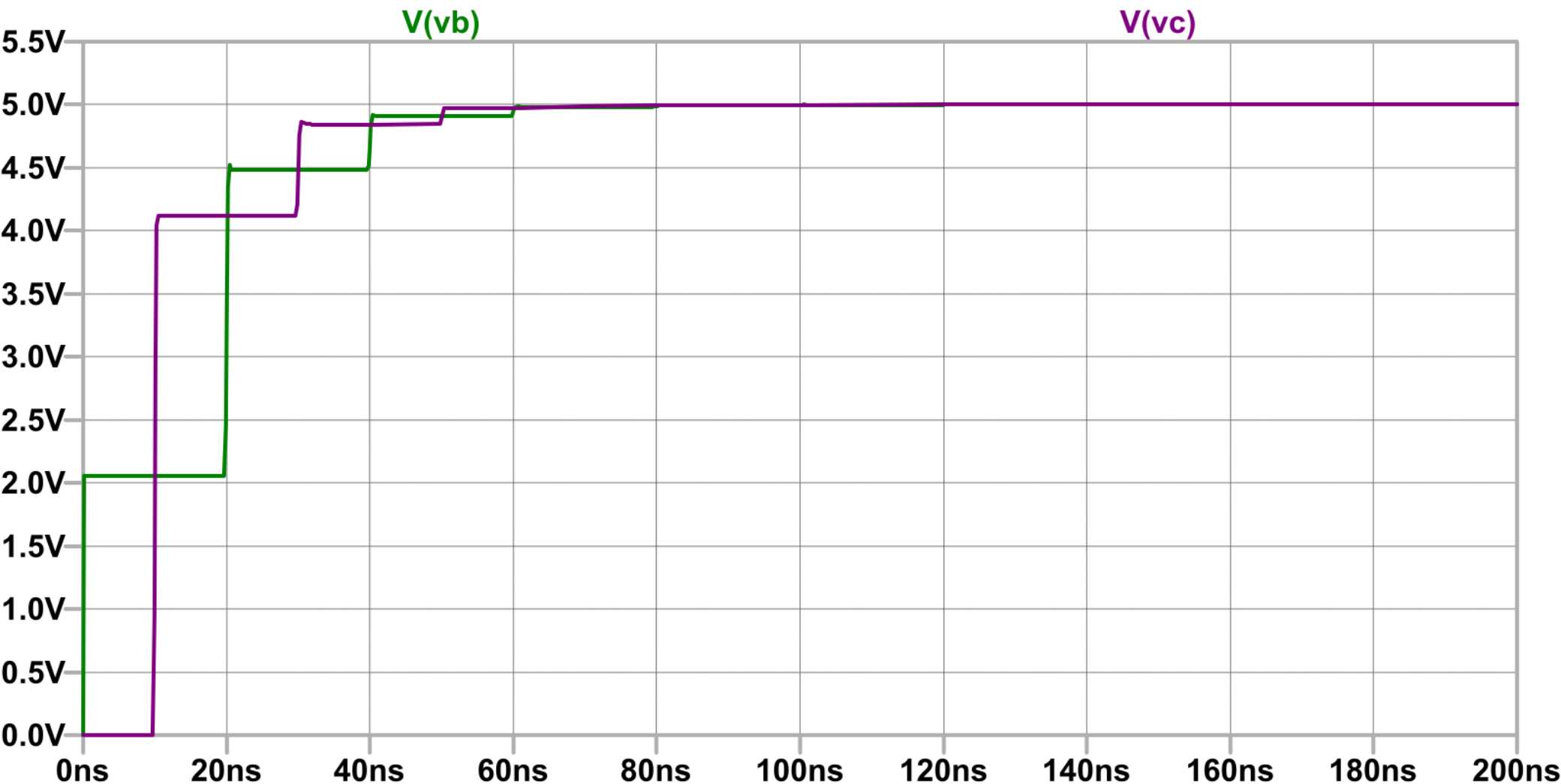Exercise C3.1: transmission delay evaluation: (a) – waveforms






Exercise C3.1: transmission delay evaluation: (b) – calculations

- $\Gamma_D = \frac{R_O - Z_\infty}{R_O + Z_\infty} = \frac{100 \, \Omega - 70 \, \Omega}{100 \, \Omega + 70 \, \Omega} = \frac{30 \, \Omega}{170 \, \Omega} = 0.18 > 0$
- $\Gamma_T = \frac{R_T - Z_\infty}{R_T + Z_\infty} = \frac{200 \, \Omega - 70 \, \Omega}{200 \, \Omega + 70 \, \Omega} = 0.48 > 0$
- $V_{\text{steady}} = \frac{R_T}{R_O + R_T} V_A = \frac{200 \, \Omega}{100 \, \Omega + 200 \, \Omega} \cdot 5 \, \text{V} = 3.33 \, \text{V}$
- $v_1 = V_B(0) = \frac{Z_\infty}{R_O + Z_\infty} V_A = \frac{70 \, \Omega}{100 \, \Omega + 70 \, \Omega} \cdot 5 \, \text{V} = 2.06 \, \text{V}$
- $v_2 = \Gamma_T v_1 = 0.48 \cdot 2.06 \, \text{V} = 0.99 \, \text{V}$
- $v_3 = \Gamma_D \Gamma_T v_1 = 0.18 \cdot 0.48 \cdot 2.06 \, \text{V} = 0.18 \, \text{V}$
- $v_4 = \dots$



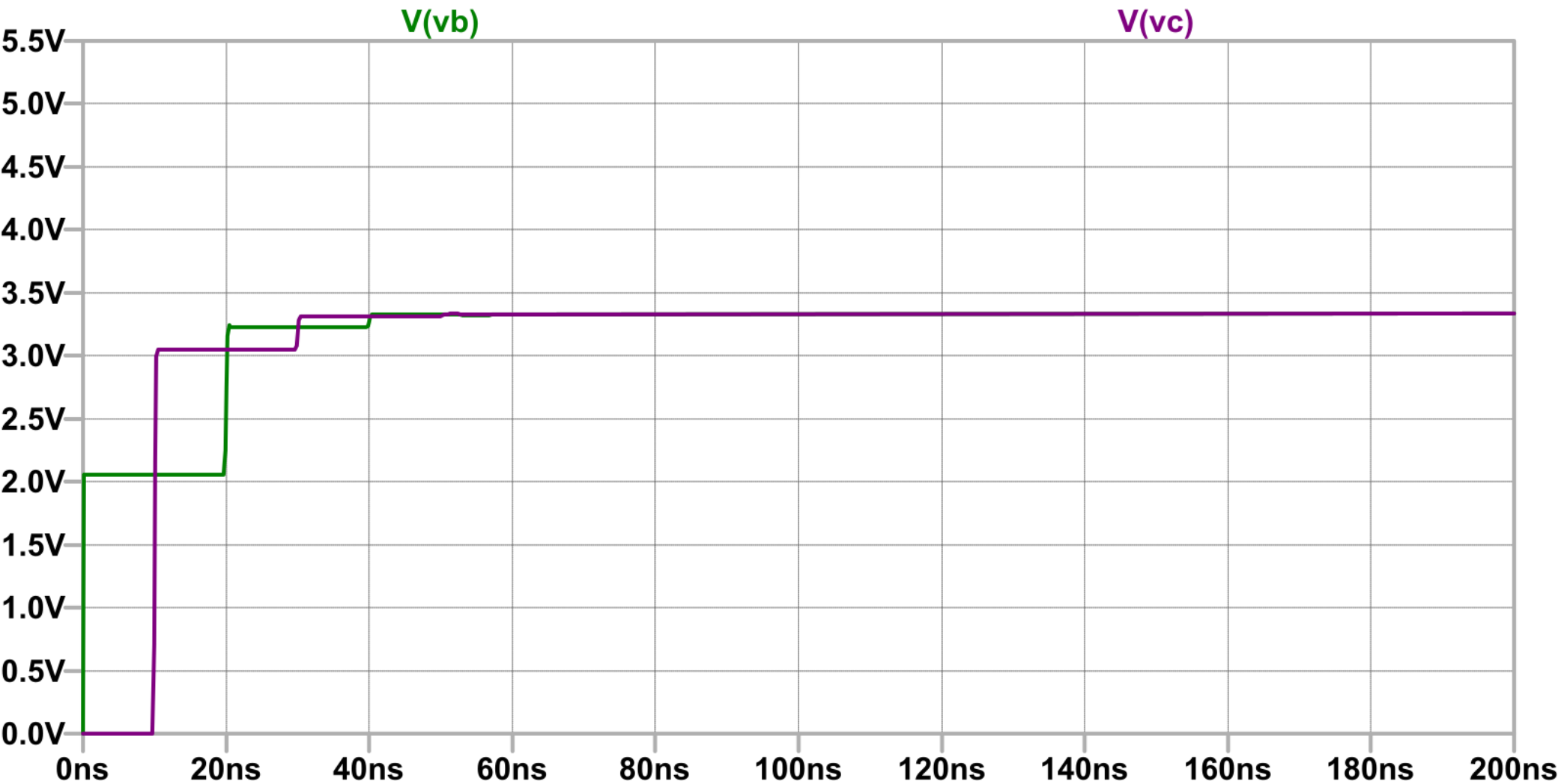Exercise C3.1: transmission delay evaluation: waveforms (b)






Exercise C3.1: transmission delay evaluation: (c) – calculations

- $\Gamma_D = \frac{R_O - Z_\infty}{R_O + Z_\infty} = \frac{50 \, \Omega - 70 \, \Omega}{50 \, \Omega + 70 \, \Omega} = \frac{-20 \, \Omega}{120 \, \Omega} = -0.17 < 0$
- $\Gamma_T = \frac{R_T - Z_\infty}{R_T + Z_\infty} = \frac{200 \, \Omega - 70 \, \Omega}{200 \, \Omega + 70 \, \Omega} = 0.48 > 0$
- $V_{\text{steady}} = \frac{R_T}{R_O + R_T} V_A = \frac{200 \, \Omega}{50 \, \Omega + 200 \, \Omega} \cdot 5 \, \text{V} = 4 \, \text{V}$
- $v_1 = V_B(0) = \frac{Z_\infty}{R_O + Z_\infty} V_A = \frac{70 \, \Omega}{50 \, \Omega + 70 \, \Omega} \cdot 5 \, \text{V} = 2.92 \, \text{V}$
- $v_2 = \Gamma_T v_1 = 0.48 \cdot 2.92 \, \text{V} = 1.40 \, \text{V}$
- $v_3 = \Gamma_D \Gamma_T v_1 = -0.17 \cdot 0.48 \cdot 2.92 \, \text{V} = -0.24 \, \text{V}$
- $v_4 = \dots$



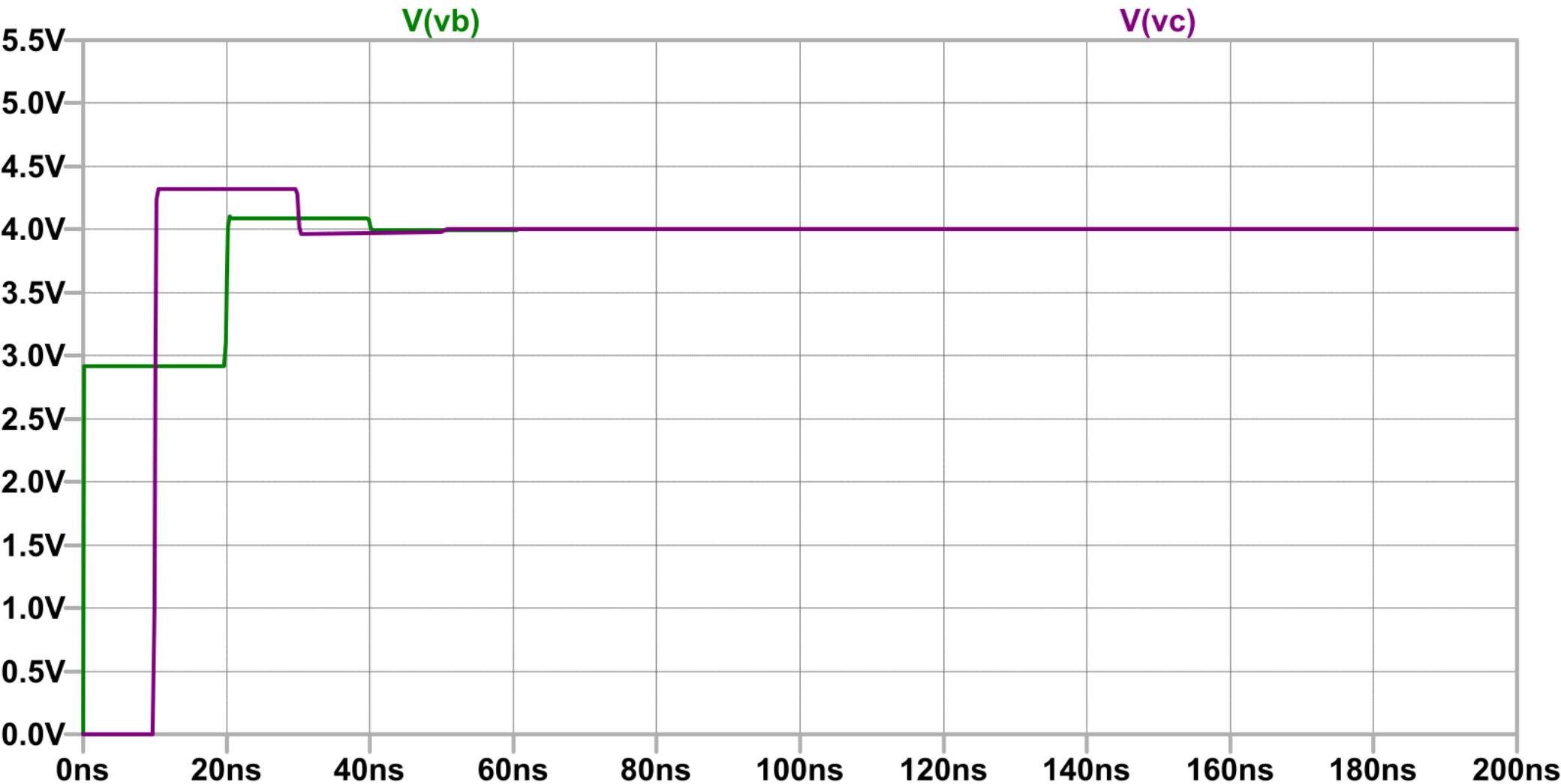Exercise C3.1: transmission delay evaluation: waveforms (c)






Exercise C3.1: transmission delay evaluation: (d) – calculations

- $\Gamma_D = \frac{R_O - Z_\infty}{R_O + Z_\infty} = \frac{50 \, \Omega - 70 \, \Omega}{50 \, \Omega + 70 \, \Omega} = \frac{-20 \, \Omega}{120 \, \Omega} = -0.17 < 0$
- $\Gamma_T = \frac{R_T - Z_\infty}{R_T + Z_\infty} = \frac{100 \, \Omega - 70 \, \Omega}{100 \, \Omega + 70 \, \Omega} = 0.18 > 0$
- $V_{\text{steady}} = \frac{R_T}{R_O + R_T} V_A = \frac{100 \, \Omega}{50 \, \Omega + 100 \, \Omega} \cdot 5 \, \text{V} = 3.33 \, \text{V}$
- $v_1 = V_B(0) = \frac{Z_\infty}{R_O + Z_\infty} V_A = \frac{70 \, \Omega}{50 \, \Omega + 70 \, \Omega} \cdot 5 \, \text{V} = 2.92 \, \text{V}$
- $v_2 = \Gamma_T v_1 = 0.18 \cdot 2.92 \, \text{V} = 0.53 \, \text{V}$
- $v_3 = \Gamma_D \Gamma_T v_1 = -0.17 \cdot 0.18 \cdot 2.92 \, \text{V} = -0.09 \, \text{V}$
- $v_4 = \dots$



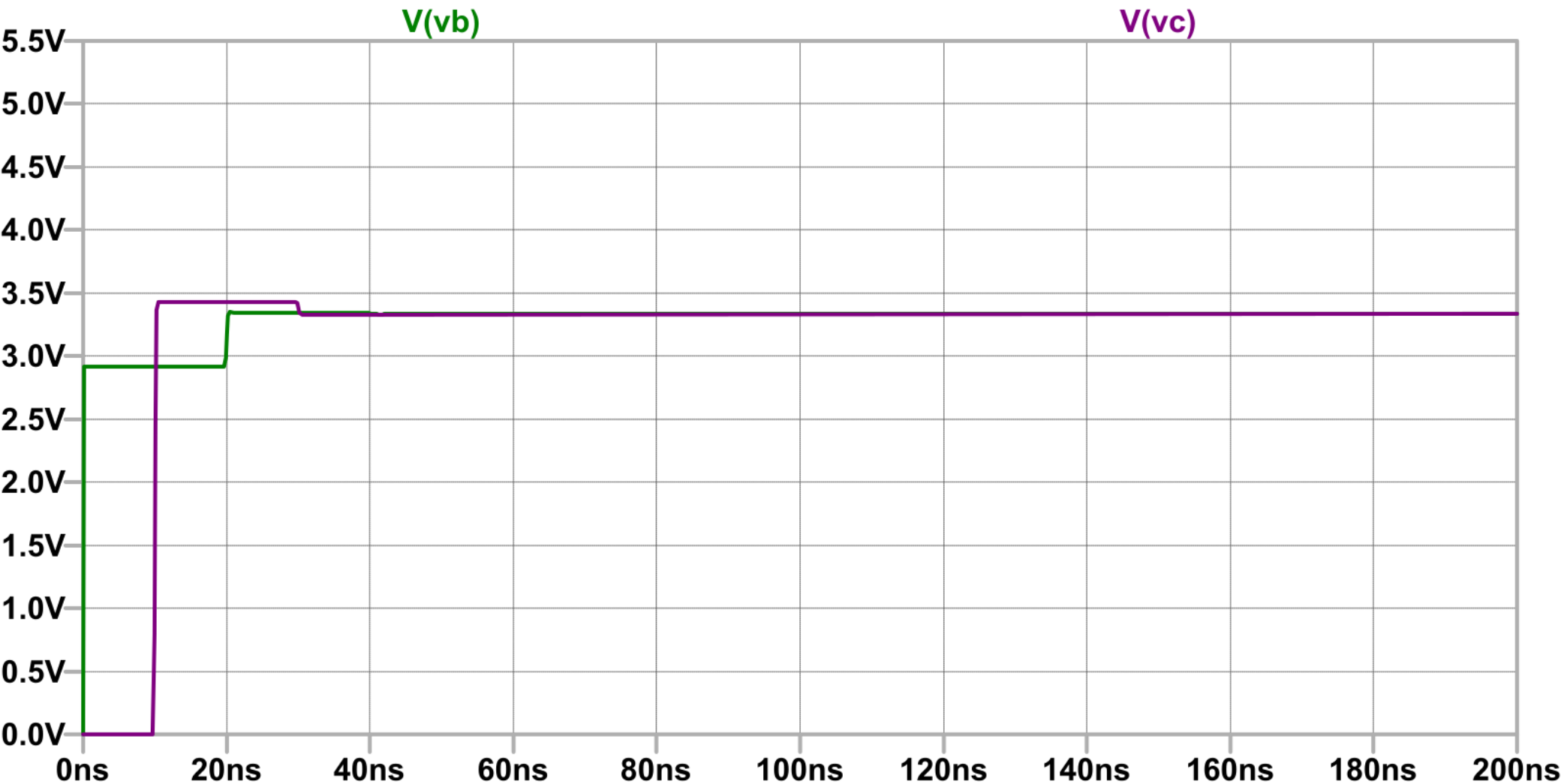Exercise C3.1: transmission delay evaluation: waveforms (d)






Exercise C3.1: transmission delay evaluation: (e) – calculations

- $\Gamma_D = \frac{R_O - Z_\infty}{R_O + Z_\infty} = \frac{10 \, \Omega - 70 \, \Omega}{10 \, \Omega + 70 \, \Omega} = \frac{-60 \, \Omega}{80 \, \Omega} = -0.75 < 0$
- $\Gamma_T = \frac{R_T - Z_\infty}{R_T + Z_\infty} = \frac{100 \, \Omega - 70 \, \Omega}{100 \, \Omega + 70 \, \Omega} = 0.18 > 0$
- $V_{\text{steady}} = \frac{R_T}{R_O + R_T} V_A = \frac{100 \, \Omega}{10 \, \Omega + 100 \, \Omega} \cdot 5 \, \text{V} = 4.55 \, \text{V}$
- $v_1 = V_B(0) = \frac{Z_\infty}{R_O + Z_\infty} V_A = \frac{70 \, \Omega}{10 \, \Omega + 70 \, \Omega} \cdot 5 \, \text{V} = 4.38 \, \text{V}$
- $v_2 = \Gamma_T v_1 = 0.18 \cdot 4.38 \, \text{V} = 0.79 \, \text{V}$
- $v_3 = \Gamma_D \Gamma_T v_1 = -0.75 \cdot 0.18 \cdot 4.38 \, \text{V} = -0.59 \, \text{V}$
- $v_4 = \dots$



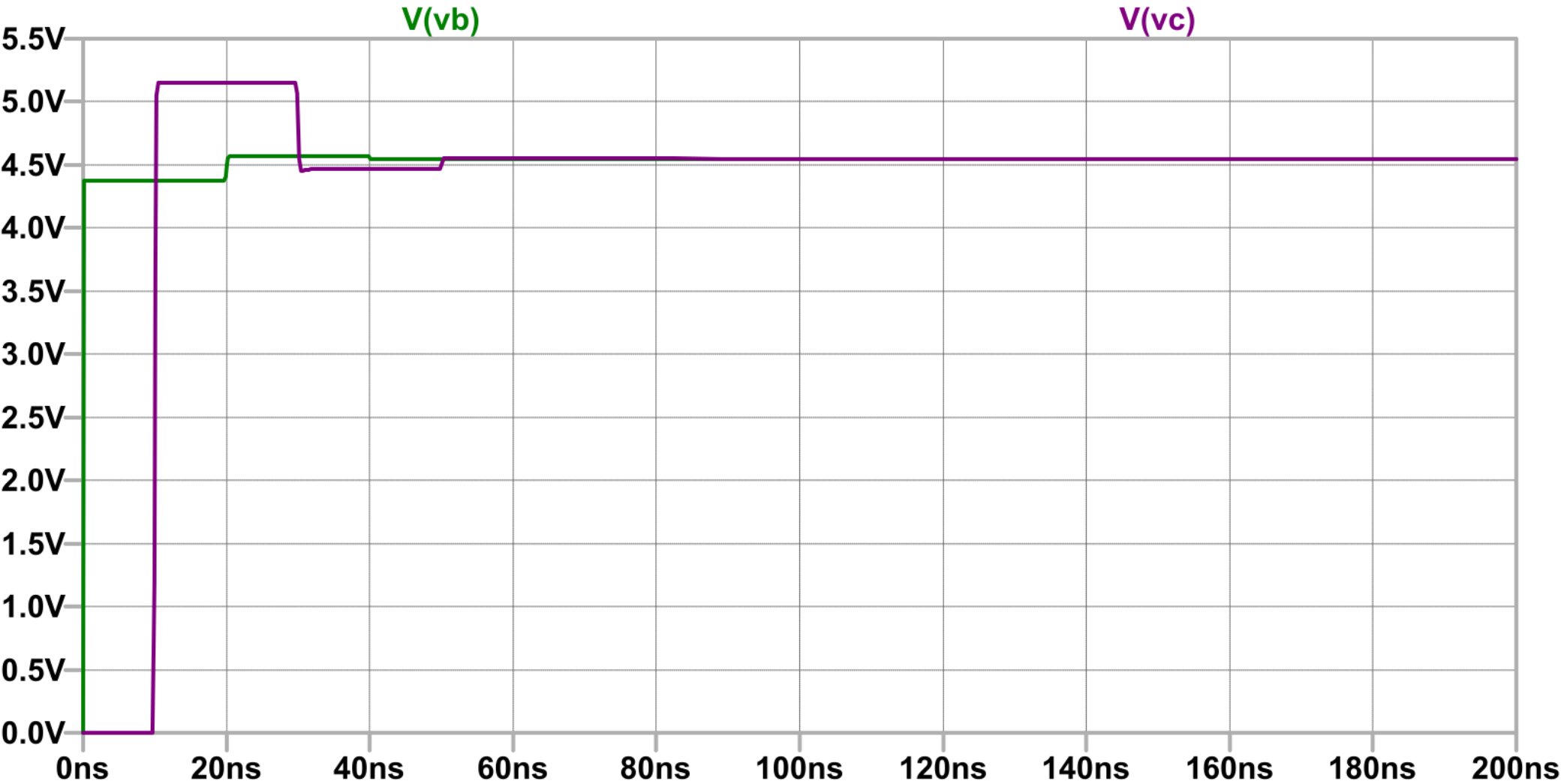Exercise C3.1: transmission delay evaluation: waveforms (e)






Exercise C3.1: transmission delay evaluation: (f) – calculations

- $\Gamma_D = \frac{R_O - Z_\infty}{R_O + Z_\infty} = \frac{10 \, \Omega - 70 \, \Omega}{10 \, \Omega + 70 \, \Omega} = \frac{-60 \, \Omega}{80 \, \Omega} = -0.75 < 0$
- $\Gamma_T = \frac{R_T - Z_\infty}{R_T + Z_\infty} = \frac{10 \, \Omega - 70 \, \Omega}{10 \, \Omega + 70 \, \Omega} = -0.75 < 0$
- $V_{\text{steady}} = \frac{R_T}{R_O + R_T} V_A = \frac{10 \, \Omega}{10 \, \Omega + 10 \, \Omega} \cdot 5 \, \text{V} = 2.50 \, \text{V}$
- $v_1 = V_B(0) = \frac{Z_\infty}{R_O + Z_\infty} V_A = \frac{70 \, \Omega}{10 \, \Omega + 70 \, \Omega} \cdot 5 \, \text{V} = 4.38 \, \text{V}$
- $v_2 = \Gamma_T v_1 = -0.75 \cdot 4.38 \, \text{V} = -3.29 \, \text{V}$
- $v_3 = \Gamma_D \Gamma_T v_1 = -0.75 \cdot (-0.75) \cdot 4.38 \, \text{V} = 2.46 \, \text{V}$
- $v_4 = \dots$



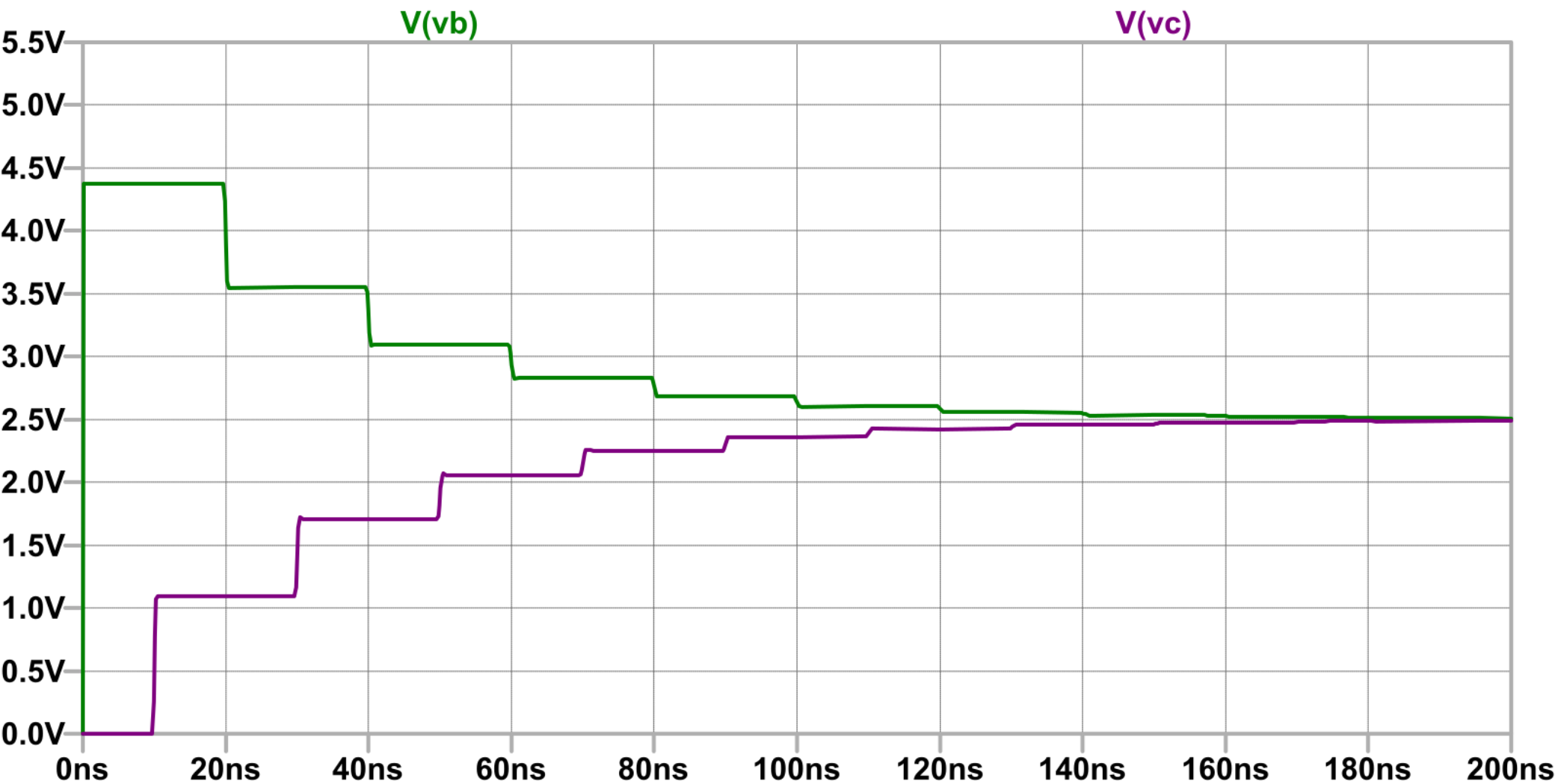Exercise C3.1: transmission delay evaluation: waveforms (f)



Exercise C3.2: parameter selection

- For the interconnection of exercise C3.1
 - ◆ $Z_{\infty} = 70 \, \Omega$, $t_p = 10 \, \text{ns}$
 - ◆ Supply: $V_{AL} = 5 \, \text{V}$
 - ◆ Receiver: $V_{IH} = 3 \, \text{V}$
 - ◆ Cases:


	a	b	c	d
Values of $R_O \, [\Omega]$	100	70	50	10
- Choose the R_O values and determine the corresponding termination resistor R_T values (connected to 2.5 V) which guarantee:
 - ◆ Minimum static power consumption
 - ◆ Maximum speed

Exercise C3.2: parameter selection: calculations

- For fast transmission time, t_{TX} , we must have
 - ◆ $v_1 \geq V_{IH} > \frac{1}{2}V_A$; $v_1 = \frac{Z_\infty}{R_O + Z_\infty} V_A \geq V_{IH} \rightarrow R_O < Z_\infty$; $R_O = \begin{cases} 50 \Omega & \text{(c)} \\ 10 \Omega & \text{(d)} \end{cases}$
- Receiver steady state condition to decode the high level
 - ◆ $V_{\text{steady}} \geq V_{IH} \rightarrow \frac{R_T}{R_O + R_T} V_A \geq V_{IH} \rightarrow R_T \geq R_O \frac{V_{IH}}{V_A - V_{IH}}$
 - c) $R_O = 50 \Omega \rightarrow R_T \geq 75 \Omega$; d) $R_O = 10 \Omega \rightarrow R_T \geq 15 \Omega$
- For minimum static power consumption, we must have
 - ◆ $I_{\text{steady}} = \min \left(\frac{V_{\text{steady}} - 2.5 \text{ V}}{R_O + R_T} \right) = \min \left(\frac{V_{IH} - 2.5 \text{ V}}{R_O + R_T} \right)$
 - c) $R_O = 50 \Omega \rightarrow I_{\text{steady}} = 4 \text{ mA}$; d) $R_O = 10 \Omega \rightarrow I_{\text{steady}} = 20 \text{ mA}$
- Thus, the best combination is
 - ◆ c) $R_O = 50 \Omega$ and $R_T = 75 \Omega$



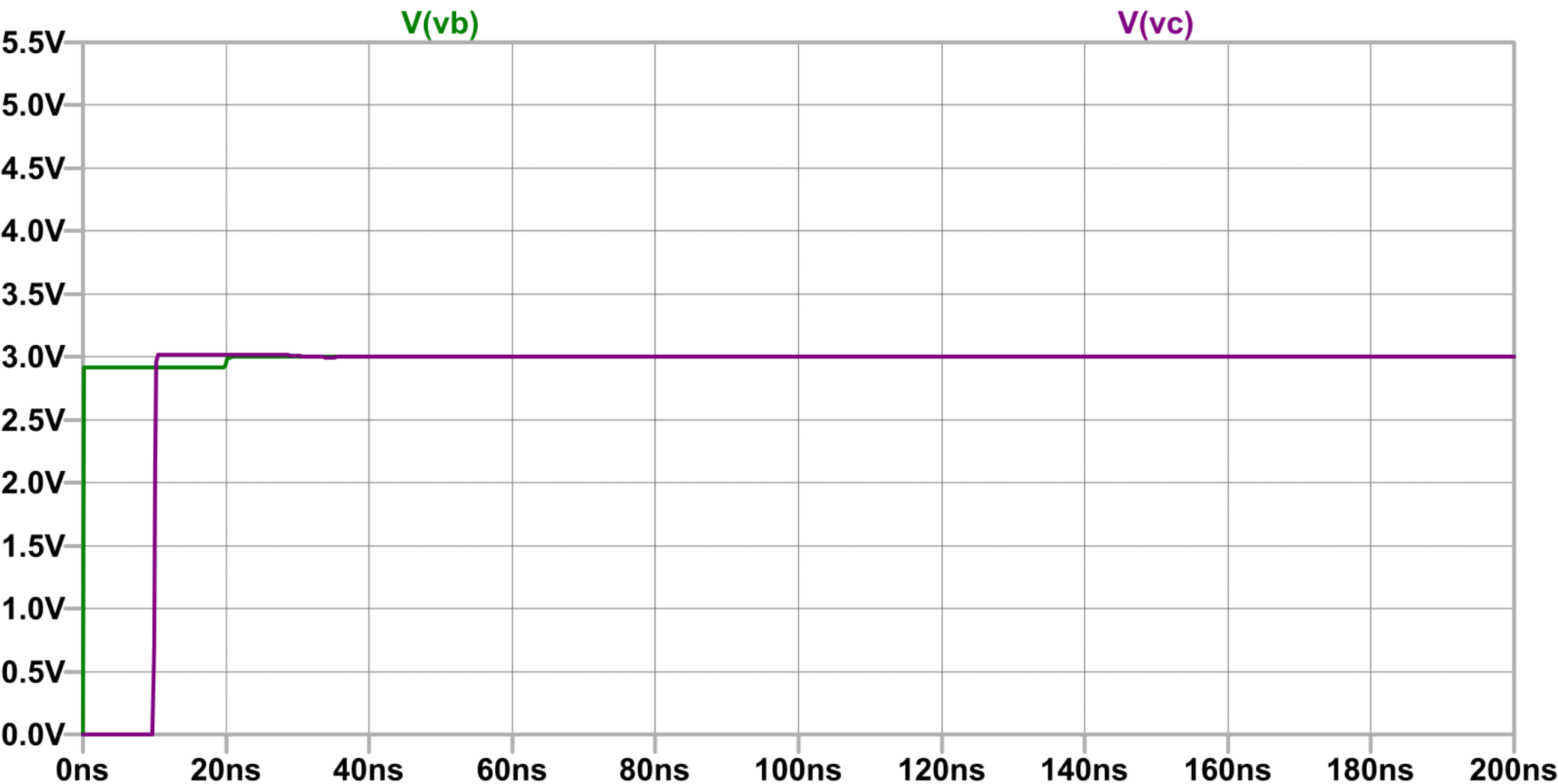Exercise C3.2: parameter selection: waveforms





Lecture C3 – final check

- Define transmission time and skew and discuss on which parameters they depend on.
- How propagation time and the transmission time differ for a transmission line interconnection?
- What is the reflection coefficient Γ at termination for
 - ◆ Open circuit
 - ◆ Short circuit
- Lossless line steady state voltage depends on Z_∞ ?
- Define IWS and RWS.
- What is the effect of a capacitive load on the transmission time of an interconnection?