




# Digital Multi Meter

1


# Digital Multi Meter (DMM)

# Digital Multi Meter


## DMM – Block scheme

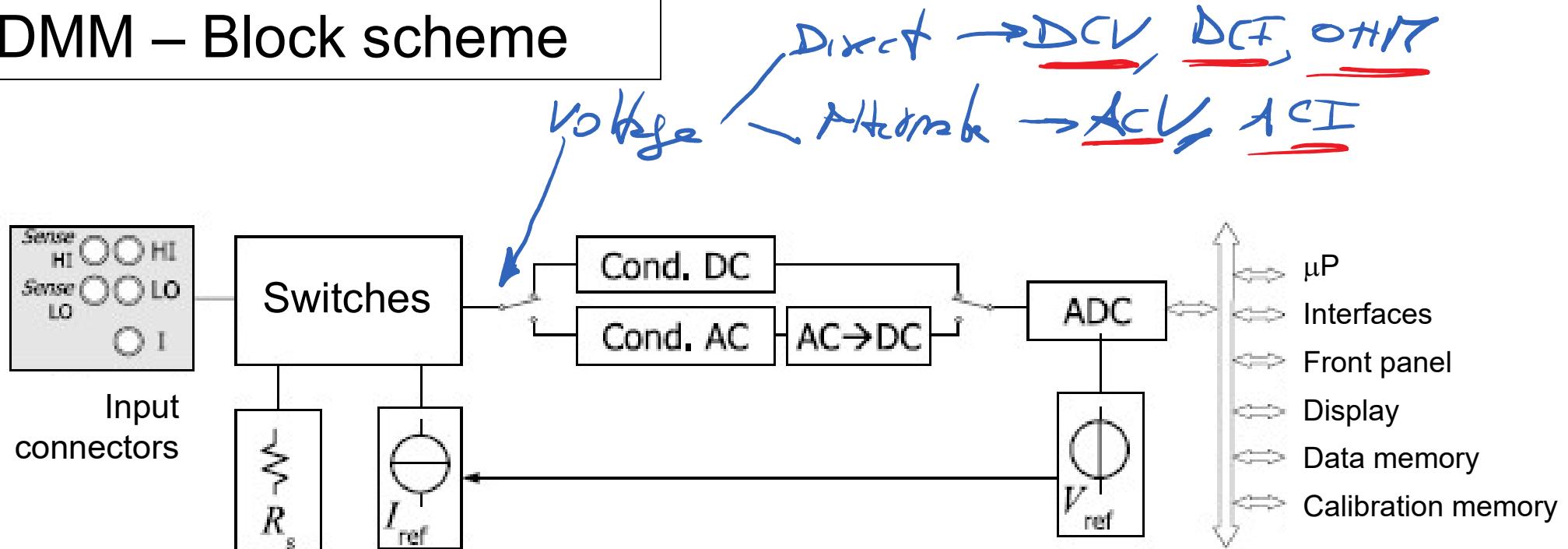

## DMM – DCV section

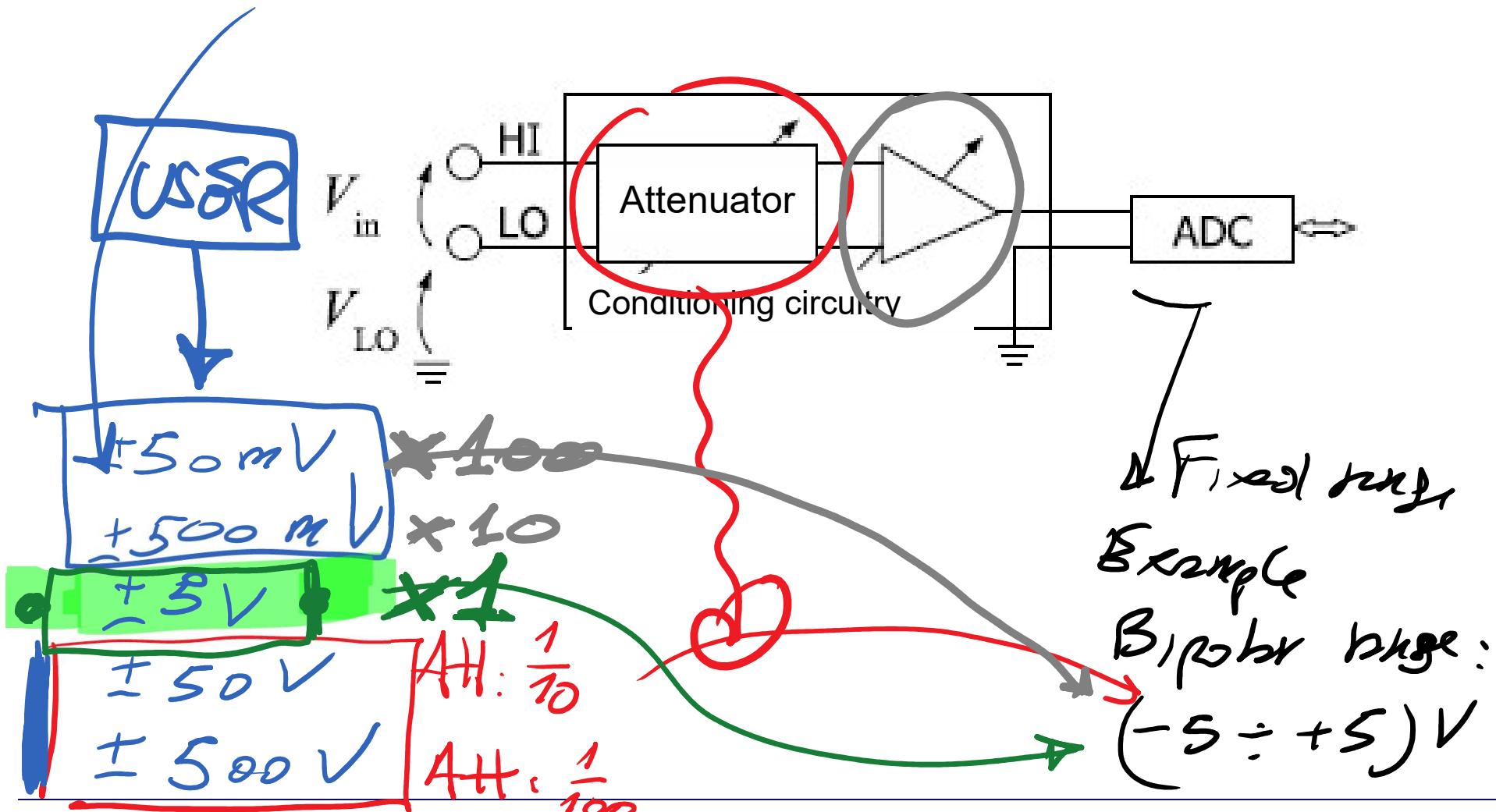

## DMM – DCV section

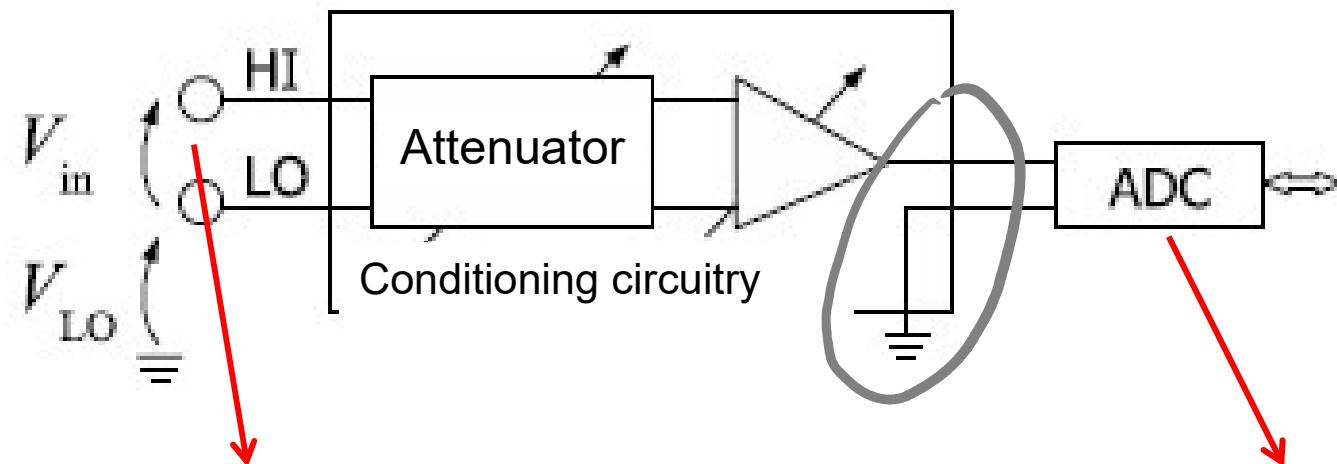

Measurement range up to 1 kV

Multi-range capability





Example:

$\pm 50 \text{ mV}$ ,  $\pm 500 \text{ mV}$ ,  $\pm 5 \text{ V}$ ,  $\pm 50 \text{ V}$ ,  
 $\pm 500 \text{ V}$ ,  $\pm 1000 \text{ V}$

Bipolar measurement range  
not greater than 10 V

Example:  $\pm 5 \text{ V}$


## DMM – DCV section

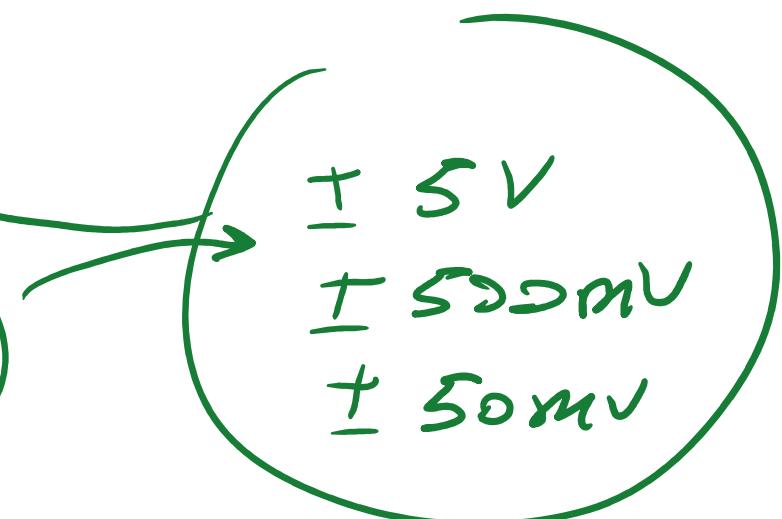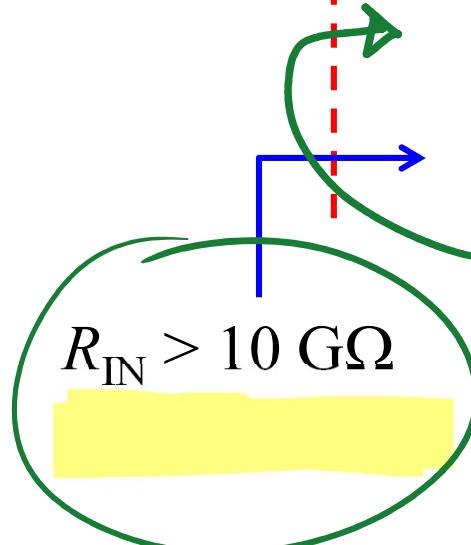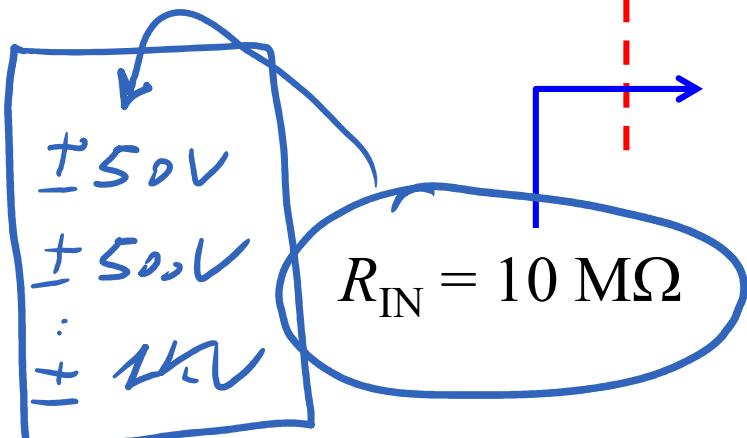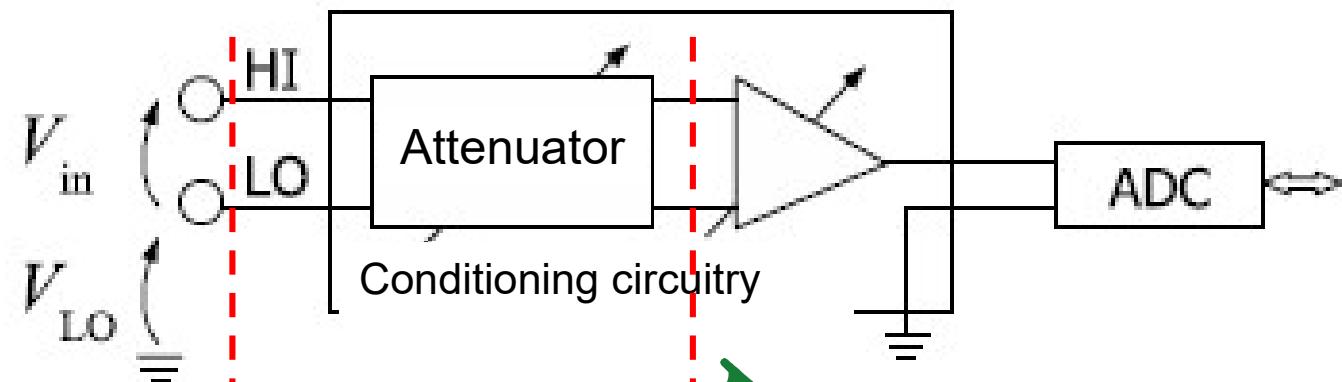

# Digital Multi Meter

## DMM – DCV section

$$V_s = V_A - V_B = V_{HI} - V_{LO}$$

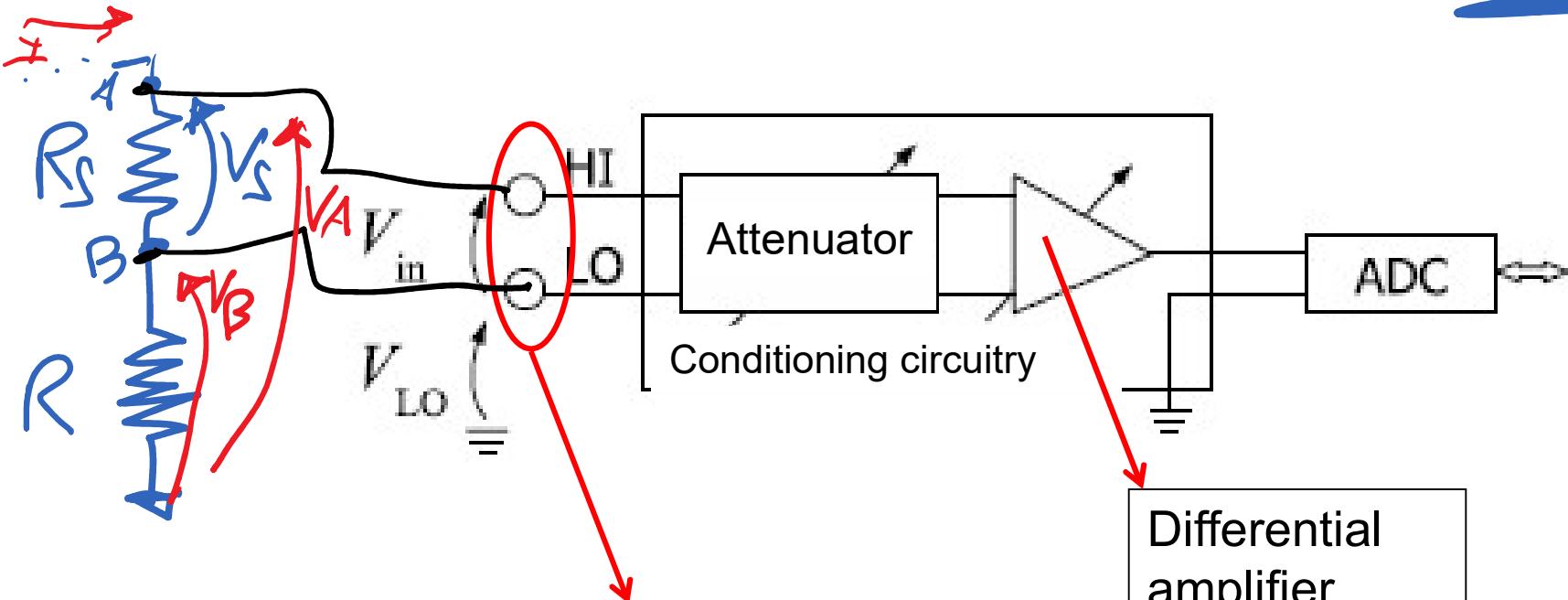


Measurement of voltages not referred to ground (low sensitivity to the voltage  $V_{LO}$ )

# Digital Multi Meter

DMM – DCV section

IDBAL DIFF. AFL.  $\rightarrow A_{CM} = 0$

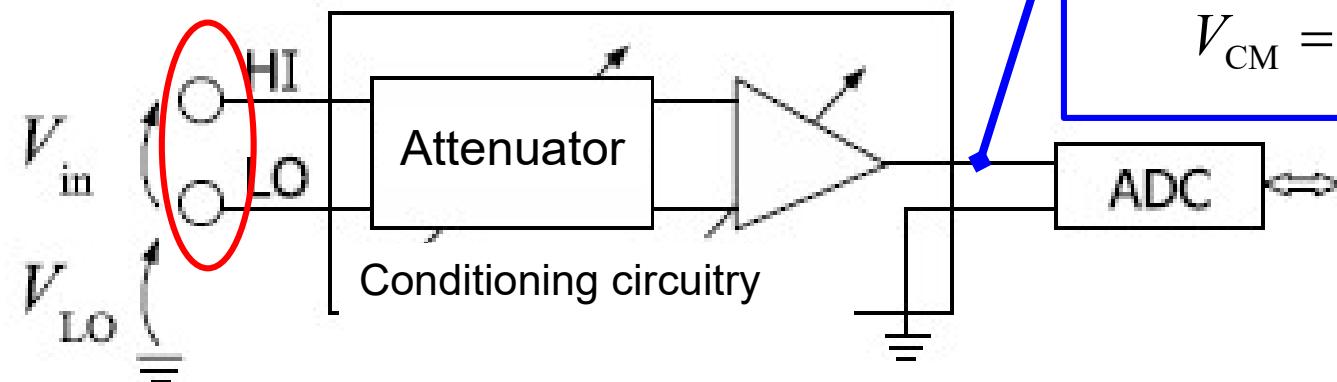$R_{SAL}$   
DIFF.  
AFL.  
 $A_{CM} \neq 0$



Common-Mode  
Rejection  
Ratio

$$CMRR = 20 \cdot \log_{10} \left( \frac{A_D}{A_{CM}} \right)$$

$A_D$ : Differential gain  
 $A_{CM}$ : Common-mode gain


Ideal amplifier  $A_{CM} = 0 \Rightarrow CMRR = \infty$

# Digital Multi Meter

DMM – DCV section

$$V_{HI} = V_{LO} \rightarrow V_{in} = 0$$
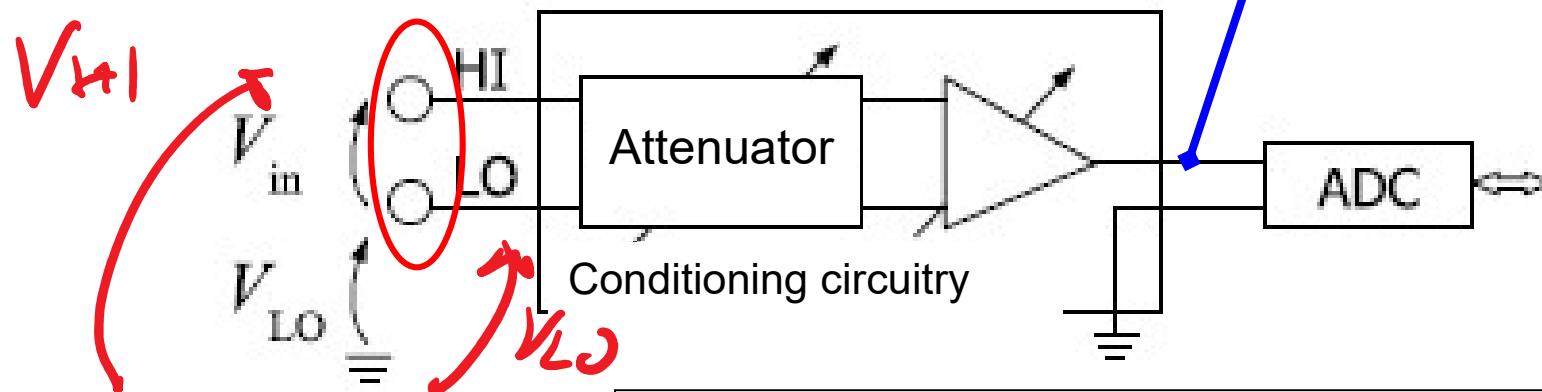
$$V_{out} = A_D \cdot V_{in} + A_{CM} \cdot V_{CM}$$



$$CMRR = 20 \cdot \log_{10} \left( \frac{A_D}{A_{CM}} \right)$$

For a real amplifier  $A_{CM} > 0$ , then the DMM provides an indication  $L_{CM} \neq 0$  even though  $V_{IN} = 0$

Example:  $CMRR = 100 \text{ dB}$ ;  $V_{HI} = 100 \text{ V}$ ;  $V_{LO} = 99 \text{ V}$ ;  $A_d = 1$

$$\Rightarrow V_{out, V_{in}} = 1 \text{ V}; \quad V_{out, V_{CM}} = V_{CM} \cdot 10^{\left( \frac{-CMRR}{20} \right)} = 0.995 \text{ mV}$$

$$10^2 \cdot 10^{-5} \approx 1 \mu\text{V}$$

# Digital Multi Meter


$$CMRR = 20 \log_{10} \left( \frac{A_d}{A_{cm}} \right) ; A_d = 1$$

$$CMRR = 100 \text{ dB}$$


$$\frac{CMRR}{20} = \log_{10} \left( \frac{A_d}{A_{cm}} \right) \Rightarrow \frac{A_d}{A_{cm}} = 10^{\frac{CMRR}{20}}$$

$$A_{cm} = A_d \cdot 10^{-\frac{CMRR}{20}} = 1 \cdot 10^{-\frac{100}{20}} = 10^{-5}$$

$A_{cm}$

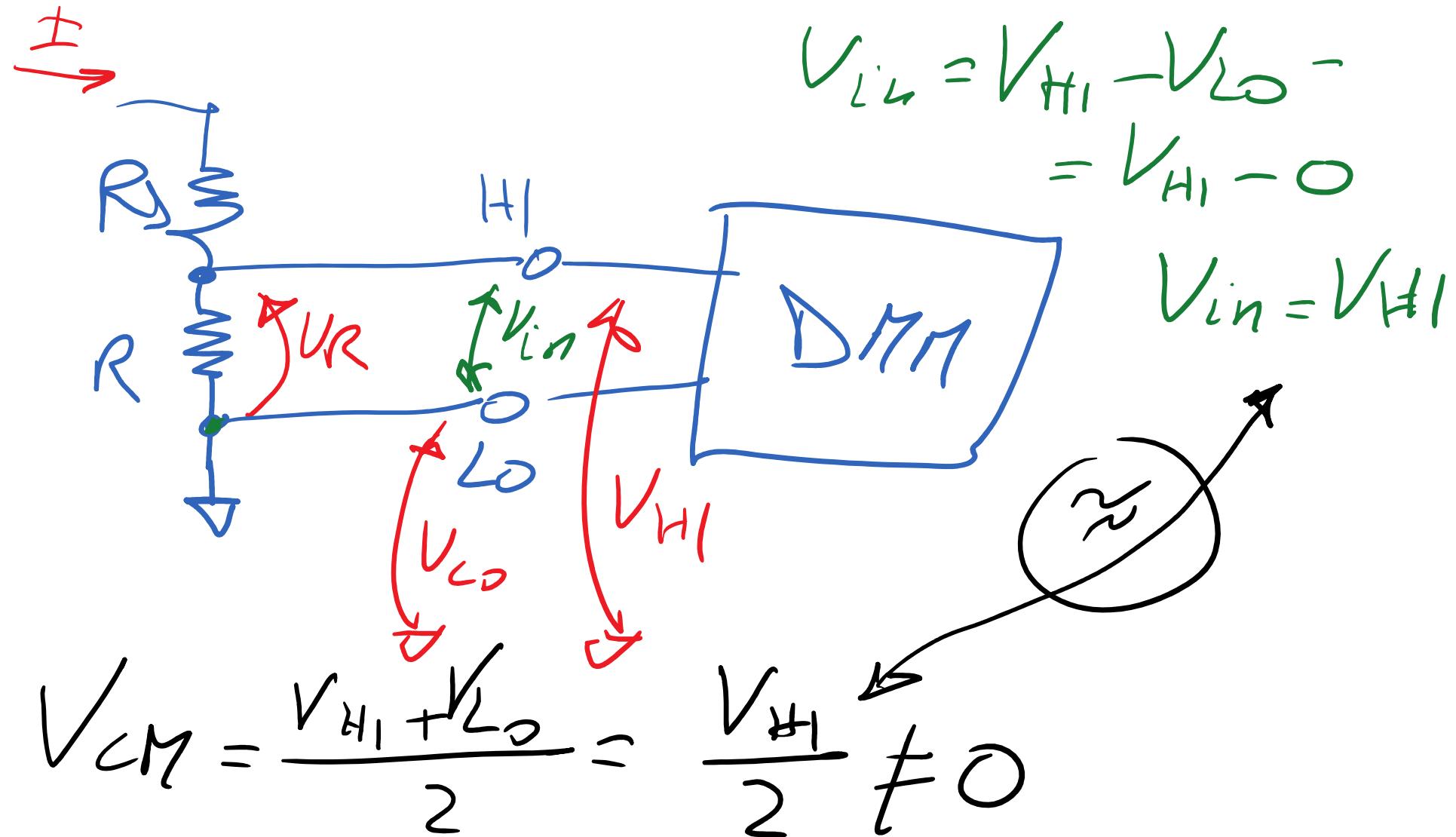


## DMM – ACV section

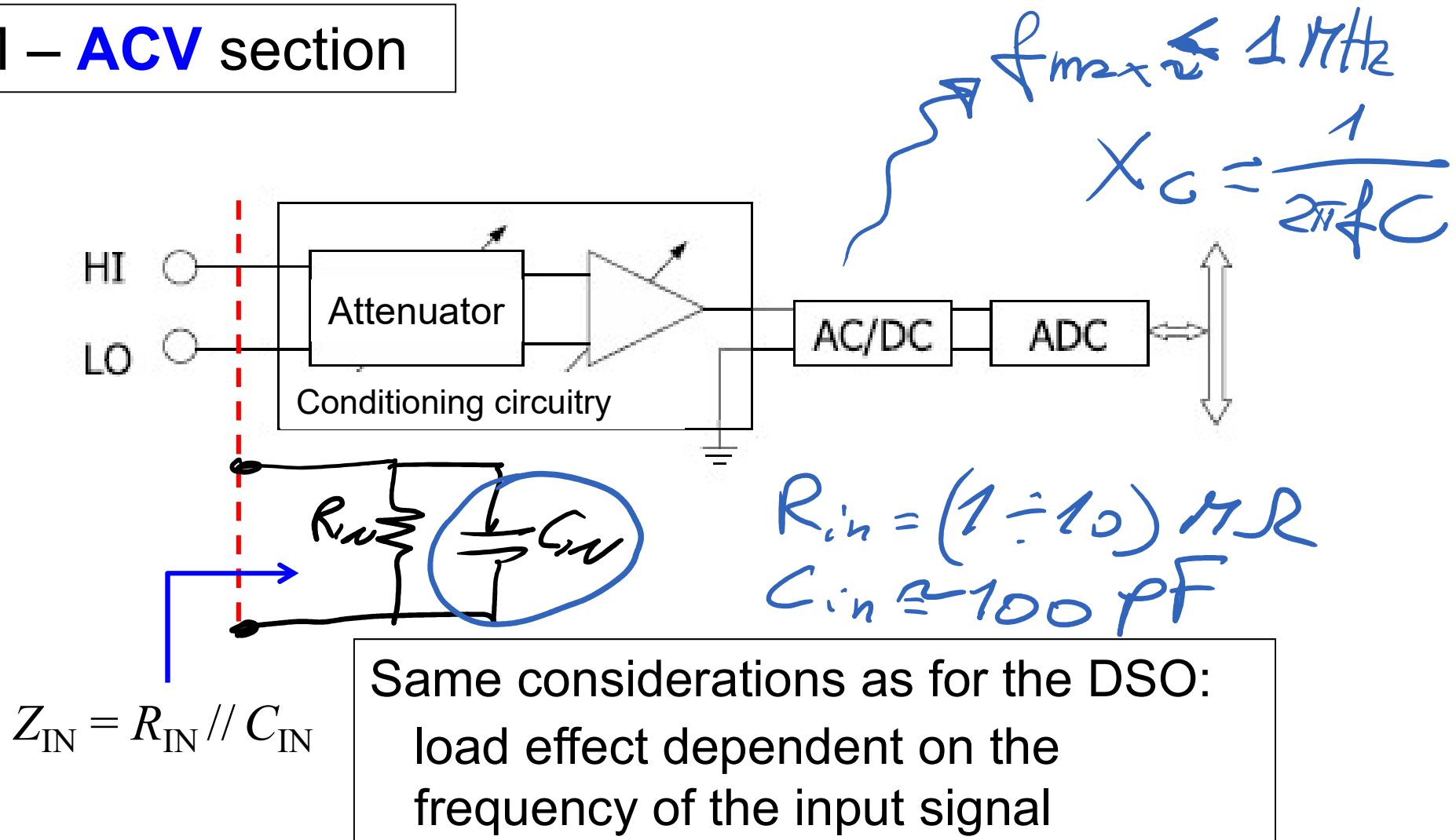

## DMM – **ACV** section

r.m.s : root mean square

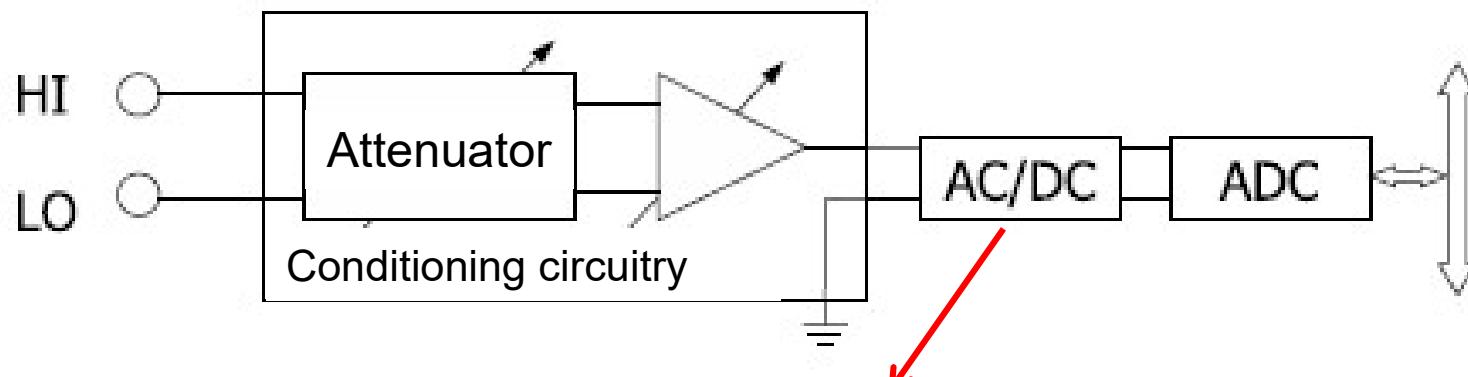


### True rms AC/DC converter

- It converts the input signal into a DC voltage that is equal to the rms value of the input signal, **regardless of its waveform**

Influence quantity: **crest factor of the input signal**

$$\frac{V_{\text{pk}}}{V_{\text{rms}}}$$

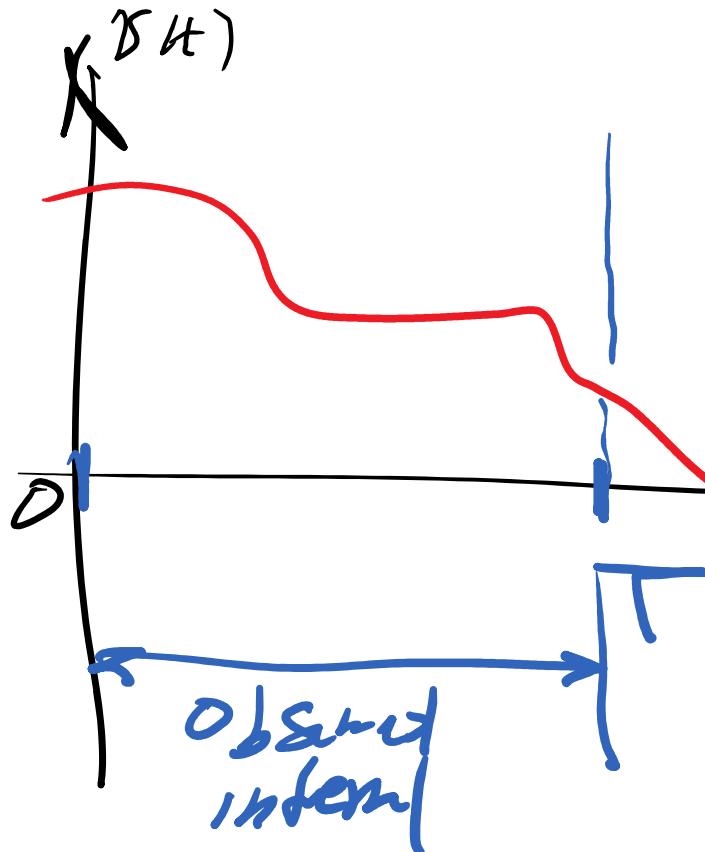


$$V_{DC} = \frac{1}{T} \int_0^T v(t) dt$$

$$V_{rms} = \sqrt{\frac{1}{T} \cdot \int_0^T v^2(t) dt}$$

The term  $\int_0^T v^2(t) dt$  is circled in green.

# Digital Multi Meter

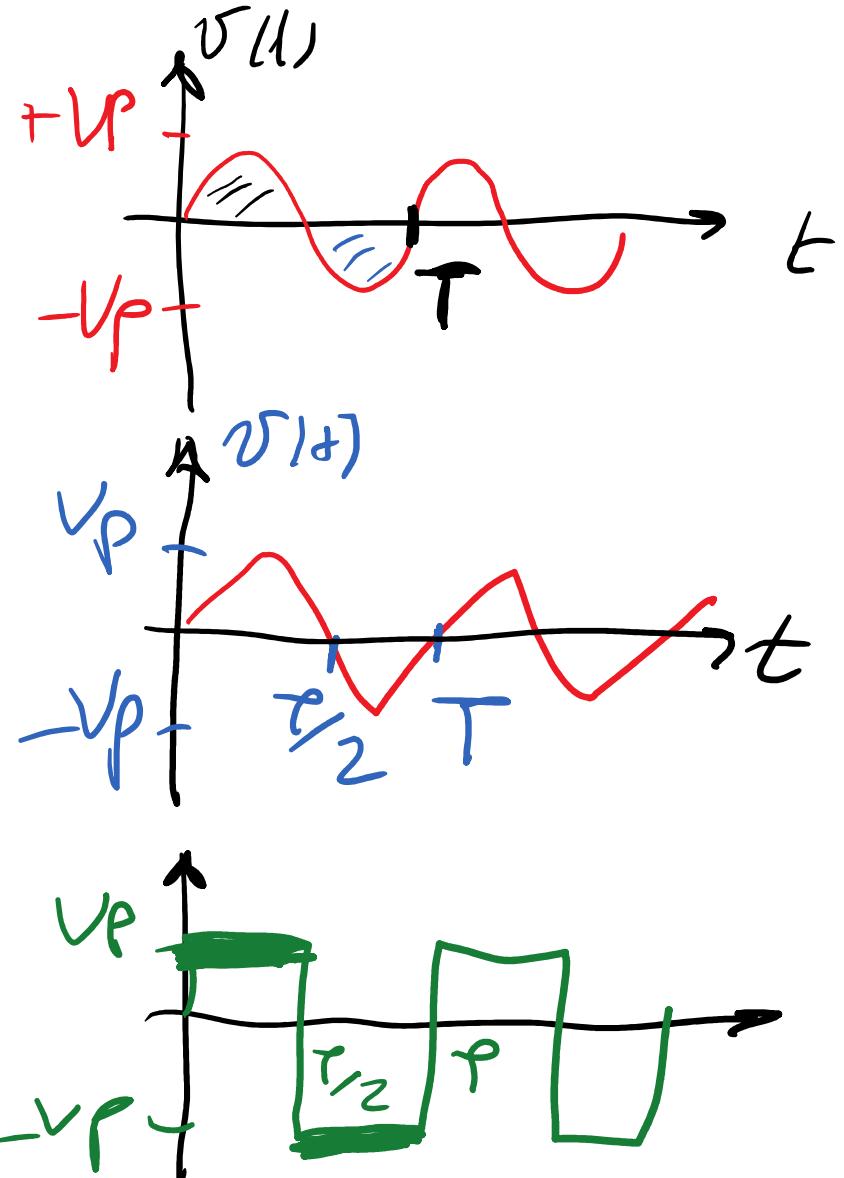

$$V_{DC} = 0$$

$$V_{rms} = \frac{V_P}{\sqrt{2}}$$

$$C.F. = \sqrt{2}$$

$$V_{DC} = 0$$

$$V_{rms} = \frac{V_P}{\sqrt{3}}$$


$$C.F. = \sqrt{3}$$

$$V_{DC} = 0$$


$$V_{rms} = V_P$$

$$C.F. = 1$$

# Digital Multi Meter

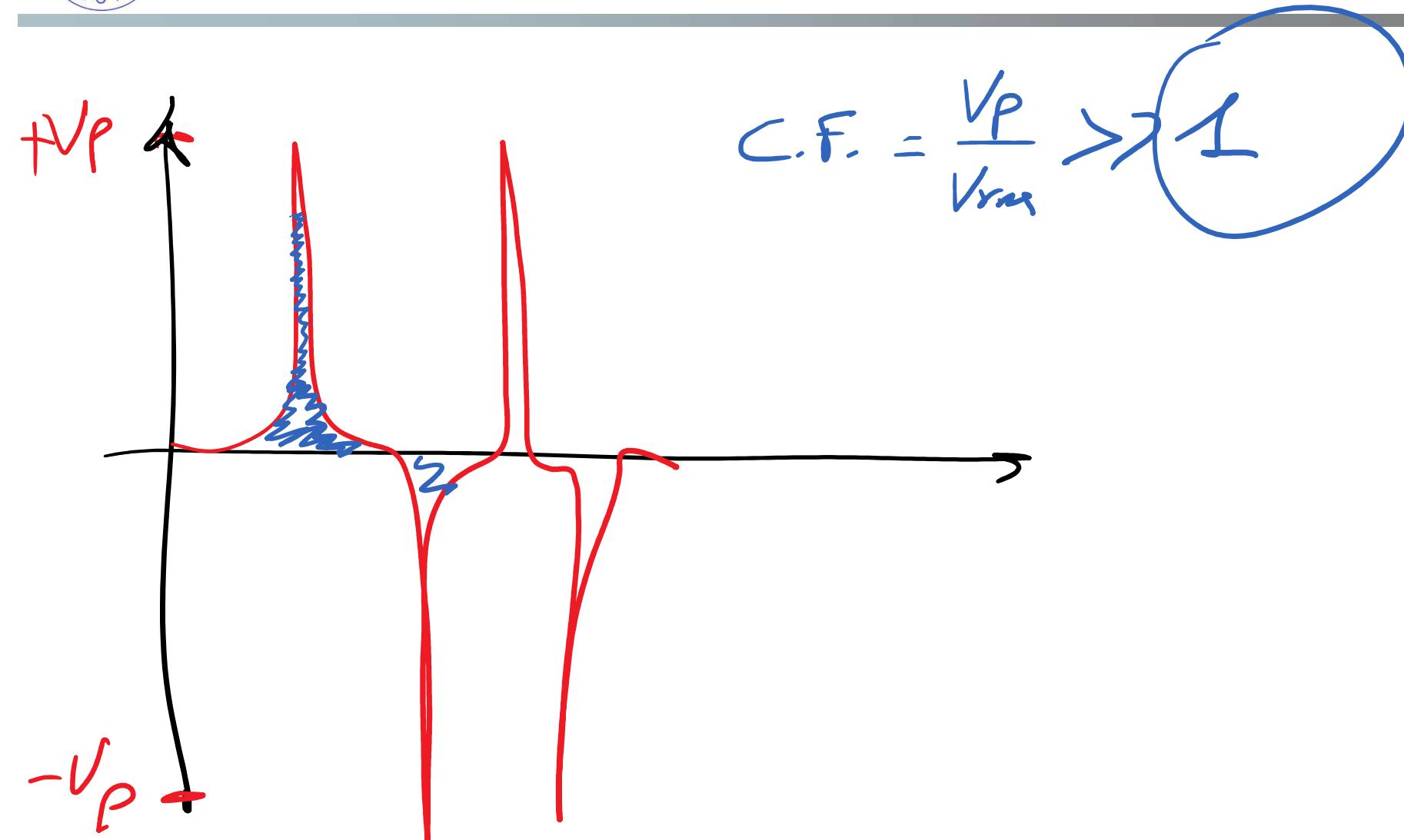

## DMM – **ACV** section

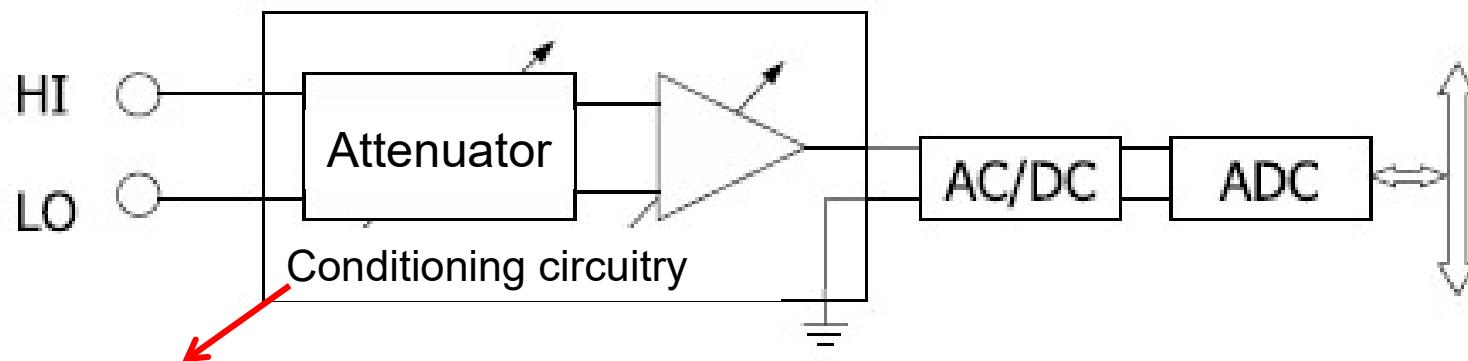

Usually AC coupled


If  $v_{in}(t) = V_{DC} + v_{AC}(t)$  → only the rms value of the AC component is measured

Remember that  $V_{rms} = \sqrt{V_{DC}^2 + V_{rms,AC}^2}$

CMRR for AC signal worse than the CMRR for DC signal


# Digital Multi Meter

17

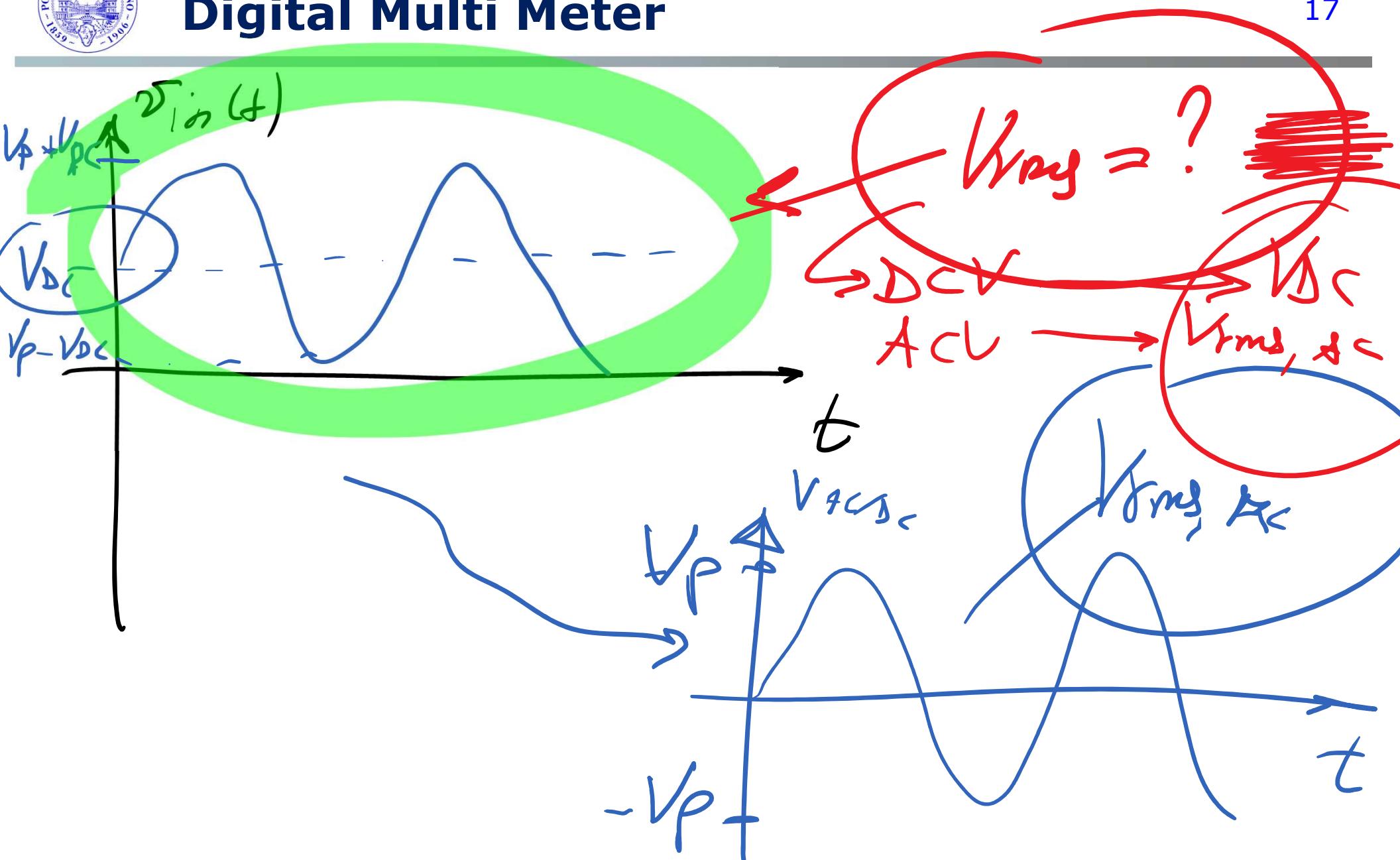
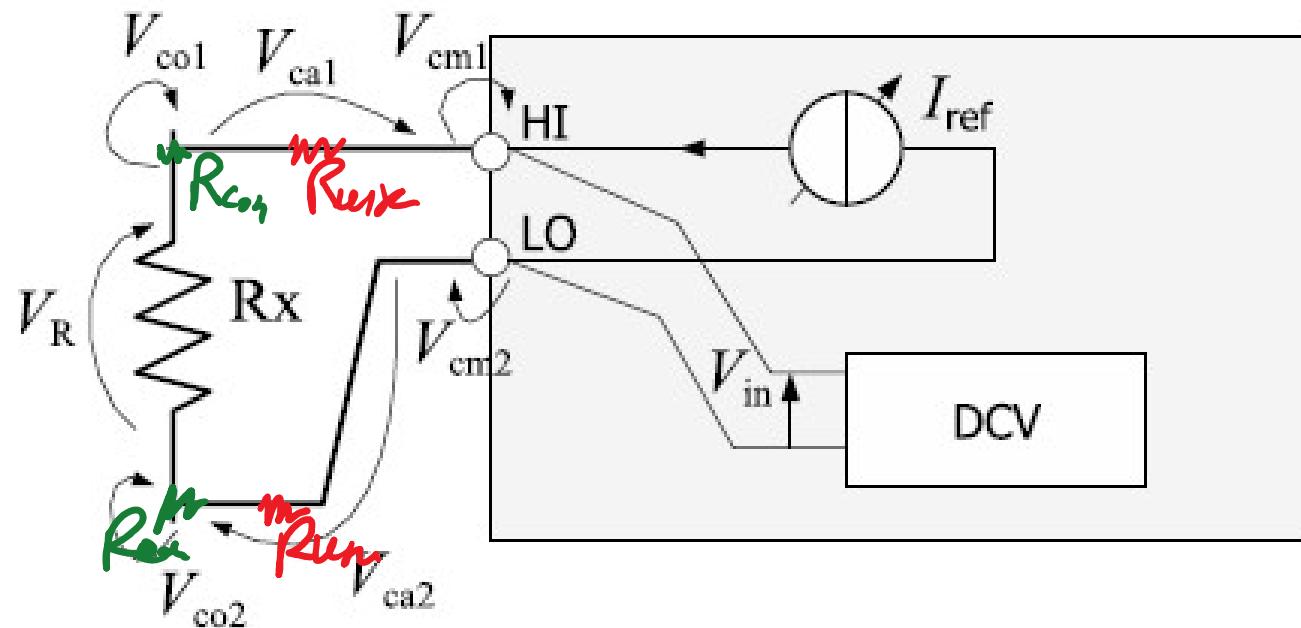
## DMM – OHM (2 wire) section

Measurement based on the volt-ammeter method



$$R_m = \frac{V_{in}}{I_{ref}} = R_x + R_{con} + R_{wire}$$


Systematic error due to cable  
and contact resistances

# Digital Multi Meter

## DMM – OHM (4 wire) section

Not always available

not available in  
all common  
DMM

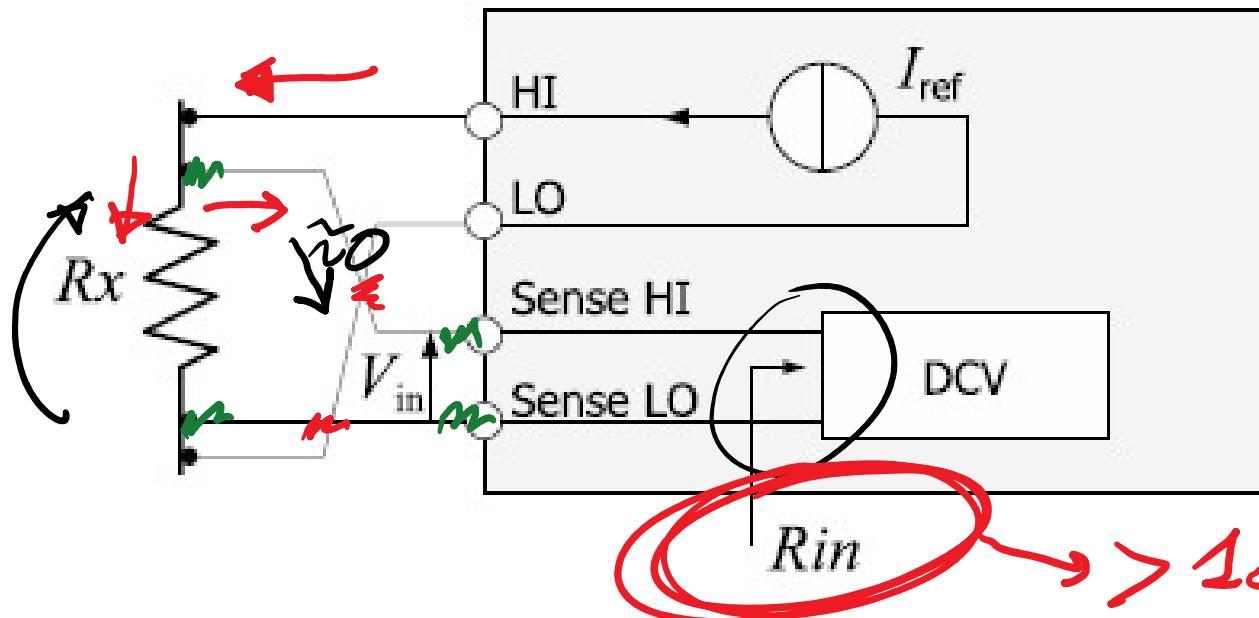

$$R_m = \frac{V_{\text{in}}}{I_{\text{ref}}}$$


$R_{\text{in}}$   $> 10^6 \Omega$

$$\varepsilon_{R_m} = -\frac{R_x}{R_x + R_{\text{in}}}$$


Relative systematic error due to the input resistance of the DCV section
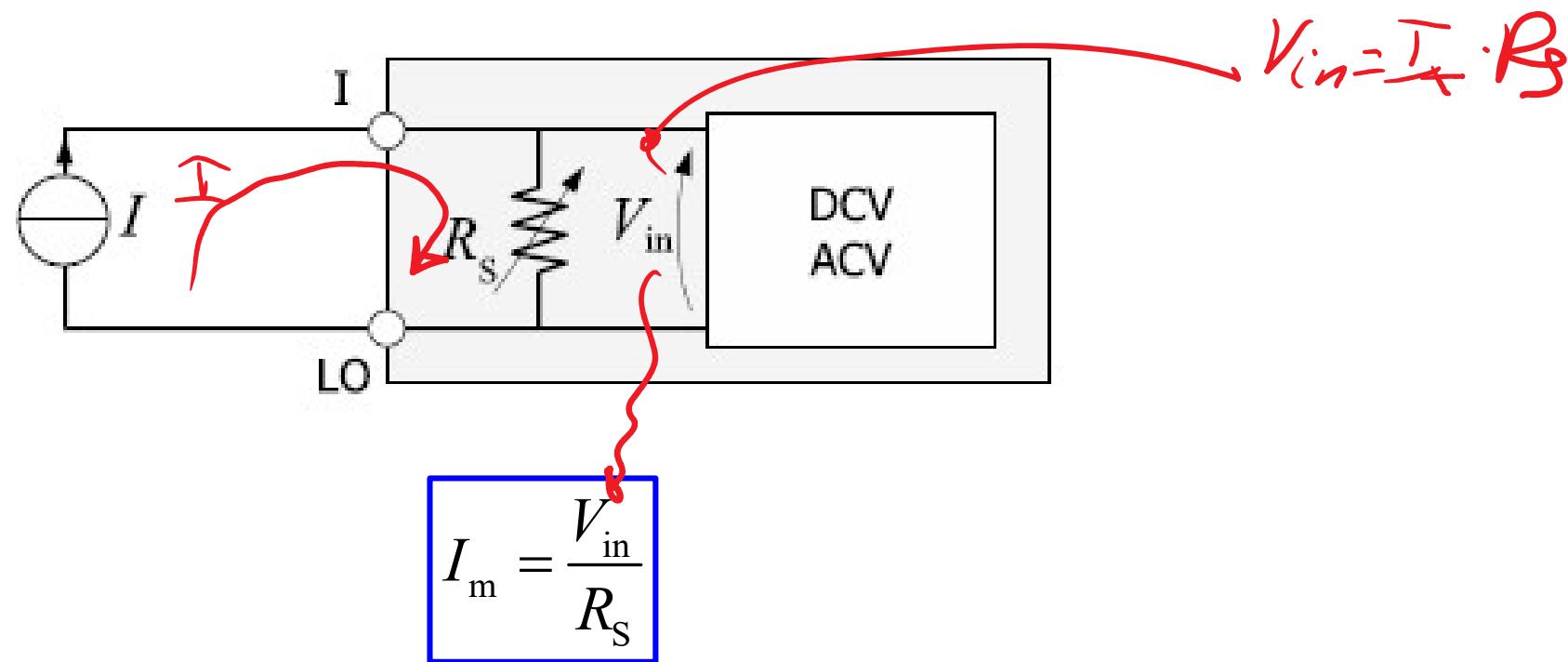
## DMM – DCI and ACI sections

Current under measurement converted into voltage by means of internal shunts  $R_s$



# Digital Multi Meter

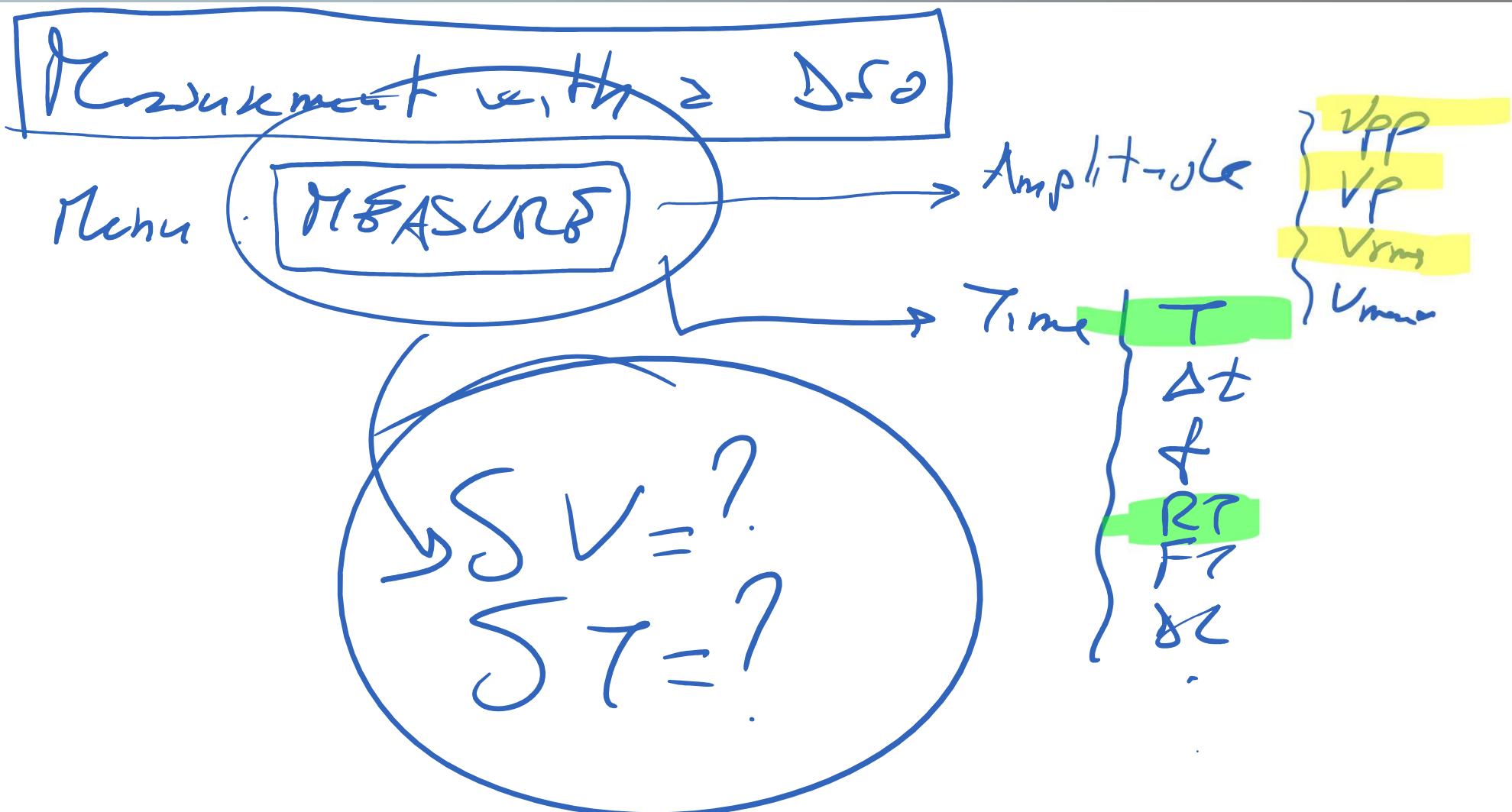


# Digital Multi Meter

22

DSO

$$E_{ky} = 2 \frac{1}{2}$$

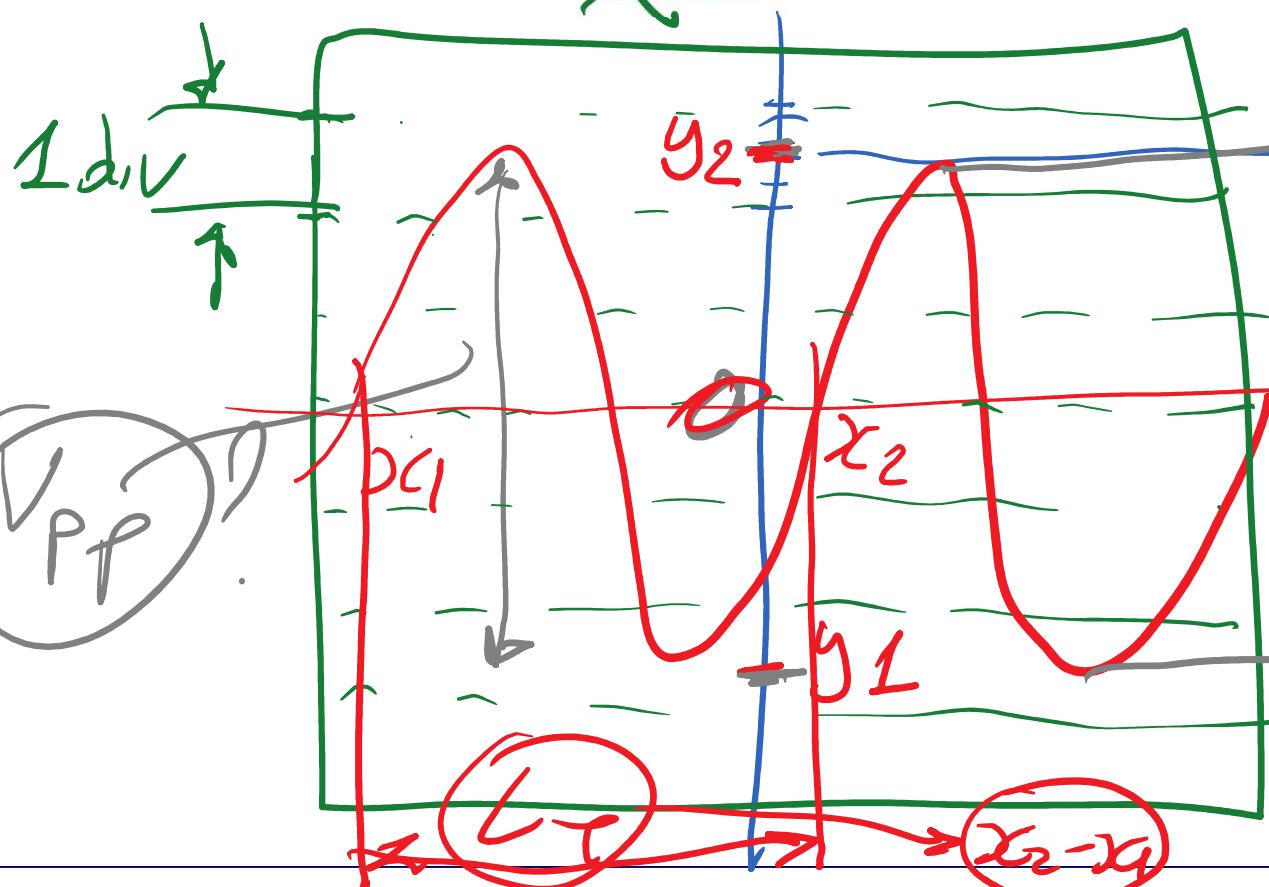

$$K_V : V/\text{div} \quad \begin{matrix} \text{vertical} \\ \text{calibration} \\ \text{constant} \end{matrix}$$

$$K_O : \text{s}/\text{div} \quad \begin{matrix} \text{time} \\ \text{c.c.} \end{matrix}$$

$$k_y = 1 V/\text{div}$$

$$y_2 = 2. - \text{div}$$

$$y_1 = -2.5 V$$

# Digital Multi Meter

$$L_{pp} = 5 \text{ div}$$

$$K_y = 1V/div$$

$$V_{pp} = L_{pp} \cdot K_y$$

$$V_{pp} = (y_2 - y_1) \cdot K_y$$

$$V_{pp_0} = L_{pp_0} \cdot K_{y_0} = \\ = 5 \cdot 1 = 5V$$


$$V_{pp_0} = 5V$$

$$\epsilon_{V_{pp}} = \epsilon_{L_{pp}} + \epsilon_{K_y} = \epsilon_{L_{pp}} + 0.02$$

$$L_{pp} = y_2 - y_1 \Rightarrow \epsilon_{L_{pp}} =$$

$$\frac{\delta L_{pp}}{L_{pp}} = \frac{\delta y_1 + \delta y_2}{y_2 - y_1}$$

# Digital Multi Meter

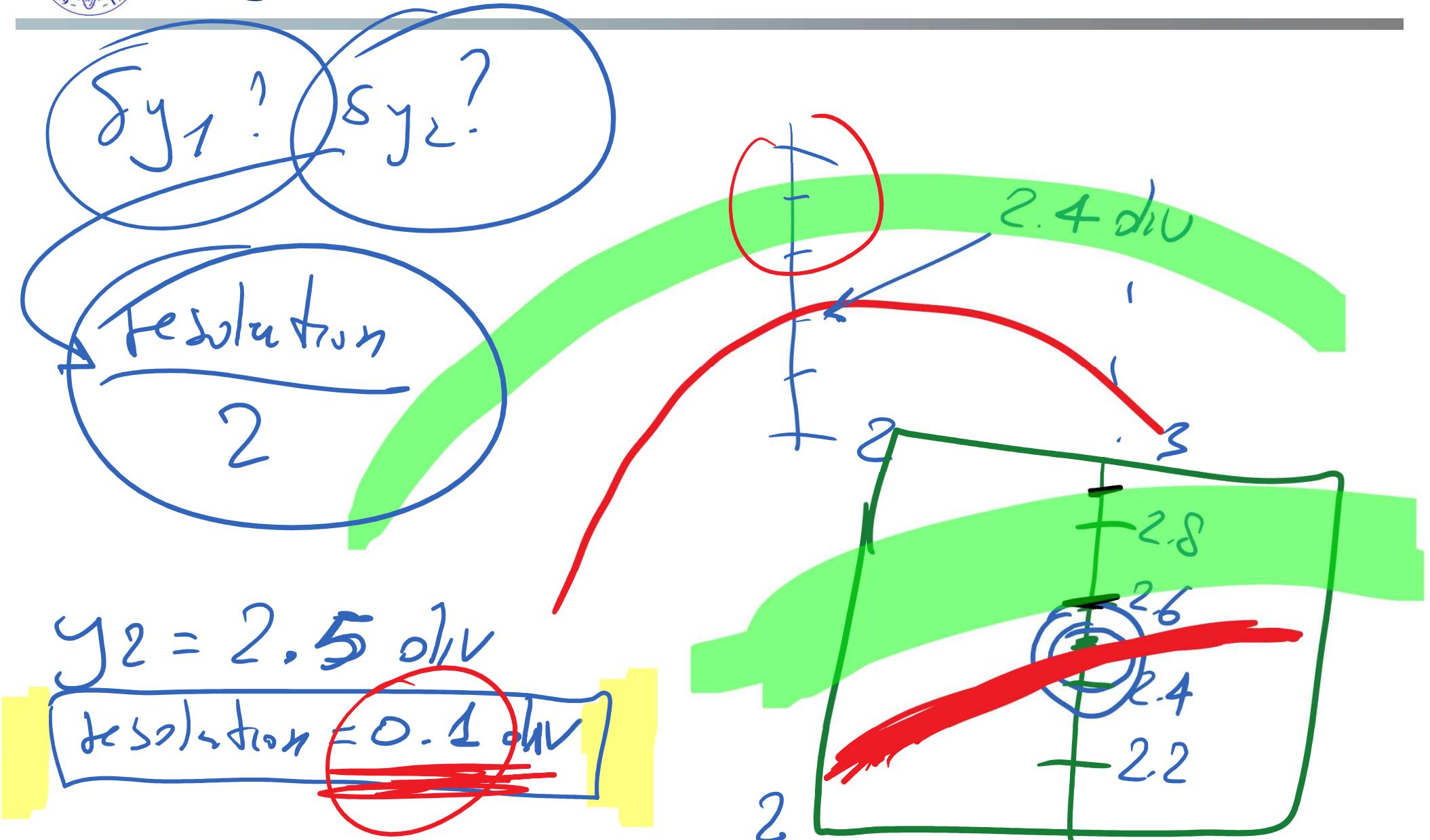

# Digital Multi Meter

$$\mathcal{E}_{V_{pp}} = \frac{\delta y_1 + \delta y_2}{y_2 - y_1} + \mathcal{E}_{Rg} = \frac{0.05 + 0.05}{5} + 0.02$$

$\mathcal{E}_{V_{pp}} = \cancel{0.1} + 0.02 = 0.02 + 0.02 = 0.04$

$V_{pp\%} = +4\%$

$$\delta V_{pp} = V_{pp} \cdot \mathcal{E}_{V_{pp}} = 5 \cdot 0.04 = 0.2 \text{ V}$$

$$V_{pp} = (5.0 \pm 0.2) \text{ V}$$

~~NOT  
SUITABLE  
CONFIGURATION~~

$$K_V = 5V/2m$$

$$L_{PP} = 1$$

$$\frac{\delta y_1 + \delta y_2}{y_2 - y_1} = \frac{0.1 - 0.1}{1}$$

10%

# Digital Multi Meter

$$\delta V = 2\% \text{ of FULL SCALE}$$

$$\delta V = 0.02 \cdot \text{FULL SCALE}$$

8 divisions  $\cdot K_g = \text{Full Scale}$

$$K_g = 1V/div \Rightarrow F.S. = 8V$$

$$\delta V = 0.02 \cdot 8 = 2 \cdot 10^{-2} \cdot 8 = 0.16V$$

$$V_{PP} = 5V \Rightarrow \Sigma V_{PP} = \frac{5V}{V_{PP}} \cdot 0.16V = 0.16V$$

$$T = L_T \cdot K_X = (x_2 - x_1) \cdot K_X$$

$$E_{K_X} = (50 \div 100) \cdot 10^{-6} = (50 \div 100) \times ppm$$

Part per million

$$E_{K_{X_{10}}} = 100 \cdot 10^{-4} = 0.01$$

# Digital Multi Meter

$V_{PP} = (5.0 \pm 0.2) V$        $\sim V_{rms} = ?$

Sim wave →  $V_{rms} \rightarrow \frac{V_{PP}}{2\sqrt{2}} = \frac{5}{2\sqrt{2}} = \dots V$

$E_{V_{rms}} = E_{V_{PP}} = 0.04$

$\rightarrow S_{V_{rms}} = V_{rms} \cdot E_{V_{rms}} = \dots 0.04 = \dots V$



# Digital Multi Meter

DCV

1

$$SV = (A\% \text{ reading} + B\% \text{ range}) \checkmark \times$$


2

$$SV = (A\% \text{ reading})V + BV$$

3

$$SV = (A\% \text{ reading})V + n \text{ digits}$$

~~n times the resolution~~

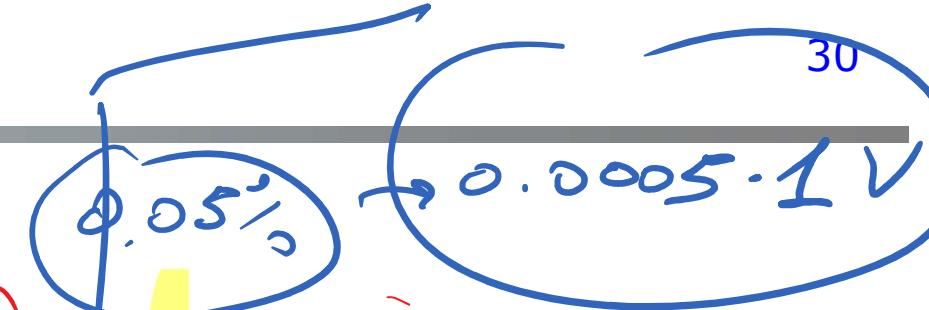

**DC V**

range 1 V

$0 \div 1$

$0 \div 9$

DMM 4 e  $\frac{1}{2}$  digits

$\boxed{\times.\text{XXXXXX}}$  ✓

reading = 0.5 V

0-1 mV

$$\delta V = 0.1\% \text{ reading} + 3 \text{ digits} =$$

$$= 0.001 \cdot 0.5 + 3 \cdot 0.1 \cdot 10^{-3} =$$

$$= 0.0005 + 0.0003 = 0.0008 =$$

$$= 0.8 \text{ mV}$$

$$\delta V = (A \text{ ppm} \cdot \text{Hz}^{-1} + B \text{ ppm} \text{ range}) V$$

$$\text{ppm} = 10^{-6}$$

$$A = 5$$

$$B = 2$$

$$\text{range} = 10V$$

$$\text{reading} = 5V$$

$$\begin{aligned} \delta V &= 5 \cdot 10^{-6} \cdot 5 + 2 \cdot 10^{-6} \cdot 10 = \\ &= 25 \cdot 10^{-6} + 20 \cdot 10^{-6} = \\ &= 4.5 \cdot 10^{-5} \approx 4.5 \mu V \end{aligned}$$

# Digital Multi Meter

$\boxed{DCV}$

$$CMRR = \underline{100 \text{ dB}}$$

$$V_{H1} = 10V$$

$$V_{L0} = 9V$$

$$V_{in} = V_{H1} - V_{L0} = \underline{1V}$$

$$V_{CH} = \frac{V_{H1} + V_{L0}}{2} = 9.5V$$

$$\cancel{\sigma_{error} = V_{CH} \cdot \frac{1}{A_d} \cdot 10^{-\frac{cm}{20}} = 9.5 \cdot 10^{-5} \approx 95 \mu V}$$

$$\cancel{\sigma_V = 0.2\% \text{ reading} + 1mV = 0.002 \cdot 1 + 1 \cdot 10^{-3} = 3mV}$$



# Digital Multi Meter

34

$$CMRR = 80 \text{ dB} \rightarrow E_{d\omega r} = 0.95 \text{ mV}$$

$$\delta V = 3 \text{ mV}$$

OHM

DMR  $\rightarrow \delta R = (0.1\% \text{ reading} + 0.05\% \text{ temp}) \sqrt{R}$

Range = 100Ω  $\rightarrow$  reading = 74 Ω

$R_w + R_{out} \approx 0.02 \Omega$   $R = 20 \text{ m}\Omega$  ~~(20 mΩ)~~

$\delta R = 0.001 \cdot 74 + 0.0005 \cdot 100 \approx 0.12 \Omega$  ↑

# Digital Multi Meter

**ΩHM**

$$\delta R = (0.01 / \text{reading} + 0.005\% \cdot \text{kNz}) \Omega$$

$$\text{reading} = 74 \Omega$$

$$R_w + R_{out} \approx 0.02 \Omega$$

$$\delta R = 0.0001 \cdot 74 + 0.00005 \cdot 100 = 0.012 \Omega$$

$$\delta R = 12 m\Omega$$

$$R_w + R_{out} < 20 m\Omega$$


$$(R_w + R_{out}) > \delta R$$

SOLUTIONS?

# Digital Multi Meter


**ΩHM**

ZW : 2 wire measurement circuit

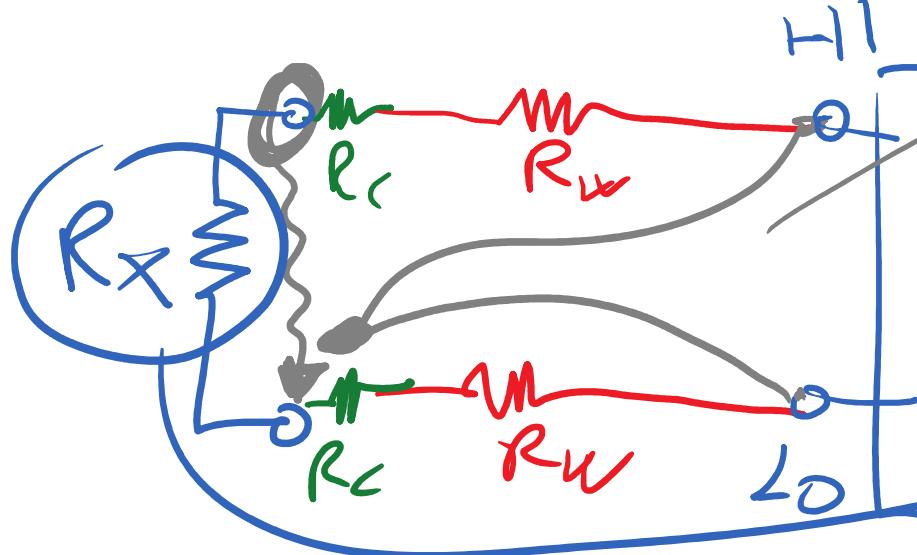


$$R_m = R_x + (R_v + R_f)$$

~~20mΩ~~

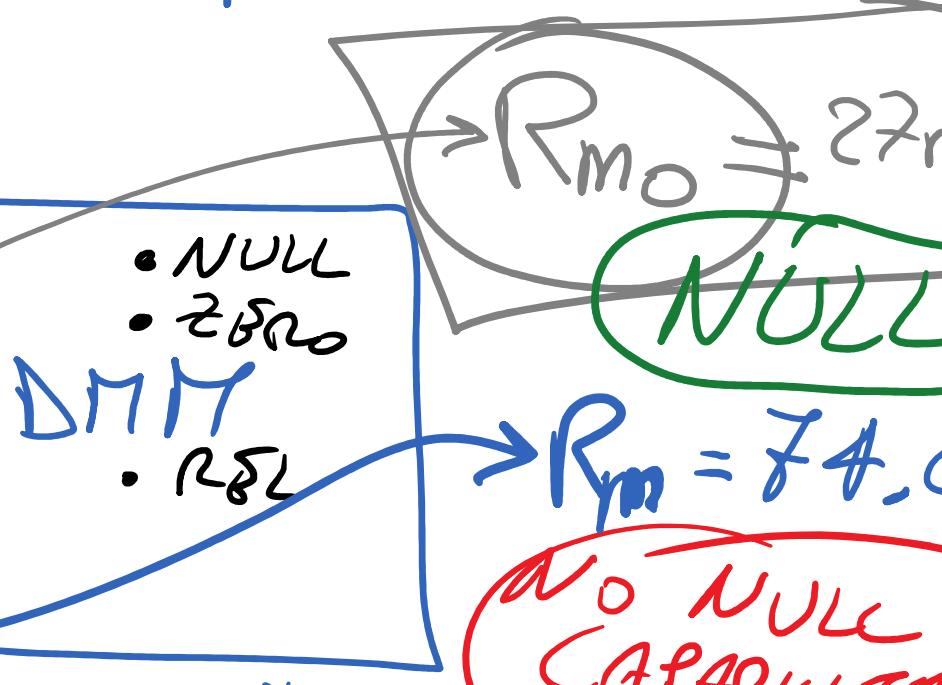
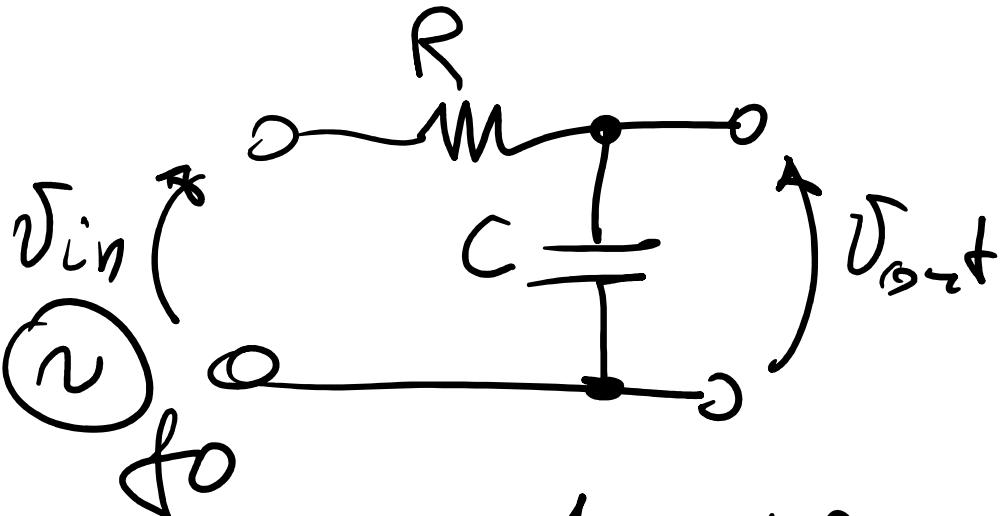
$$R_m^* = R_m - R_{m0} = \\ = (24.035 - 0.027,$$




$$Att(\omega) = \frac{V_{out}(\omega)}{V_{in}(\omega)}$$

$$Att_{dB}(\omega) = 20 \log_{10} \left[ \frac{V_{out}(\omega)}{V_{in}(\omega)} \right]$$
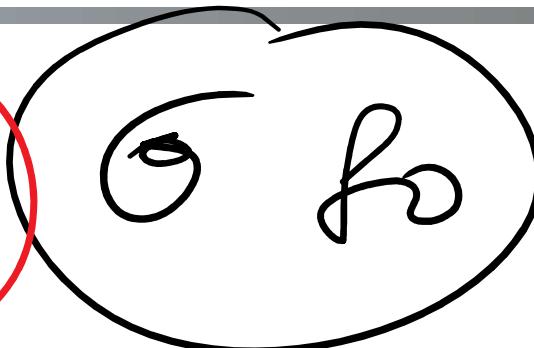
# Digital Multi Meter

$$A_{HdB} = 20 \cdot \log_{10} \left( \frac{V_{out}}{V_{in}} \right)$$



$$V_{in} = (V_{in_0} \pm \Delta V_{in}) V$$

$$f(V_{in}, V_{out})$$

$$V_{out} = (V_{out_0} \pm \Delta V_{out}) V$$

$$SA_{HdB} = \left[ \frac{\partial A_{HdB}}{\partial V_{in}} \right] \cdot \Delta V_{in} + \left[ \frac{\partial A_{HdB}}{\partial V_{out}} \right] \cdot \Delta V_{out}$$



# Digital Multi Meter

40