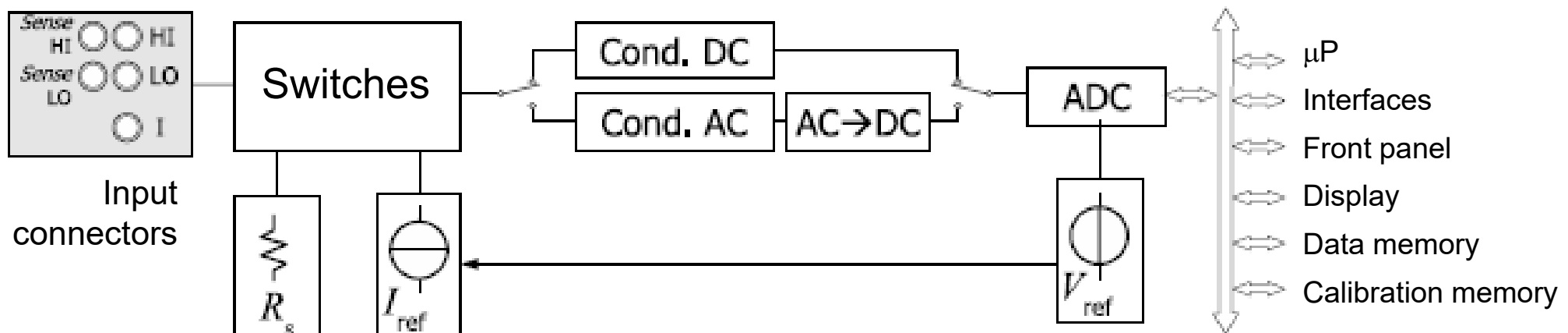




Digital Multi Meter (DMM)

DMM – Block scheme






Digital Multi Meter

3

DMM – **DCV** section

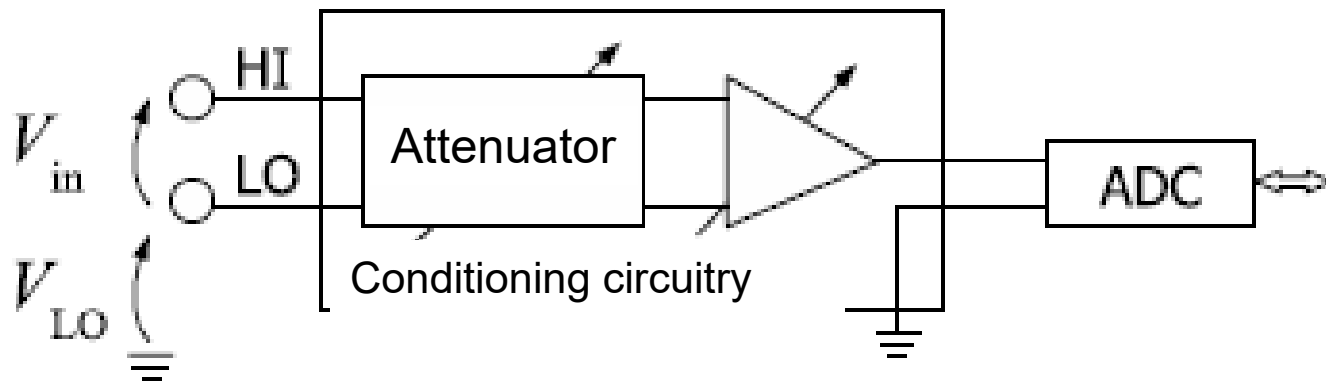




Digital Multi Meter

4

DMM – **DCV** section

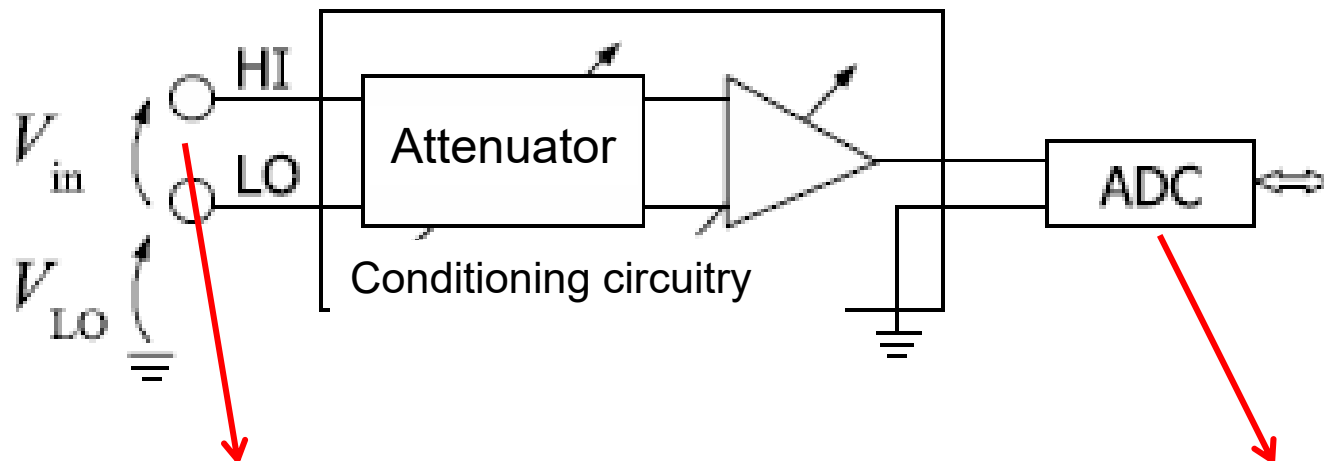

Measurement range up to 1 kV

Multi-range capability

Example:

$\pm 50 \text{ mV}$, $\pm 500 \text{ mV}$, $\pm 5 \text{ V}$, $\pm 50 \text{ V}$,
 $\pm 500 \text{ V}$, $\pm 1000 \text{ V}$

Bipolar measurement range
not greater than 10 V


Example: $\pm 5 \text{ V}$




Digital Multi Meter

5


DMM – DCV section

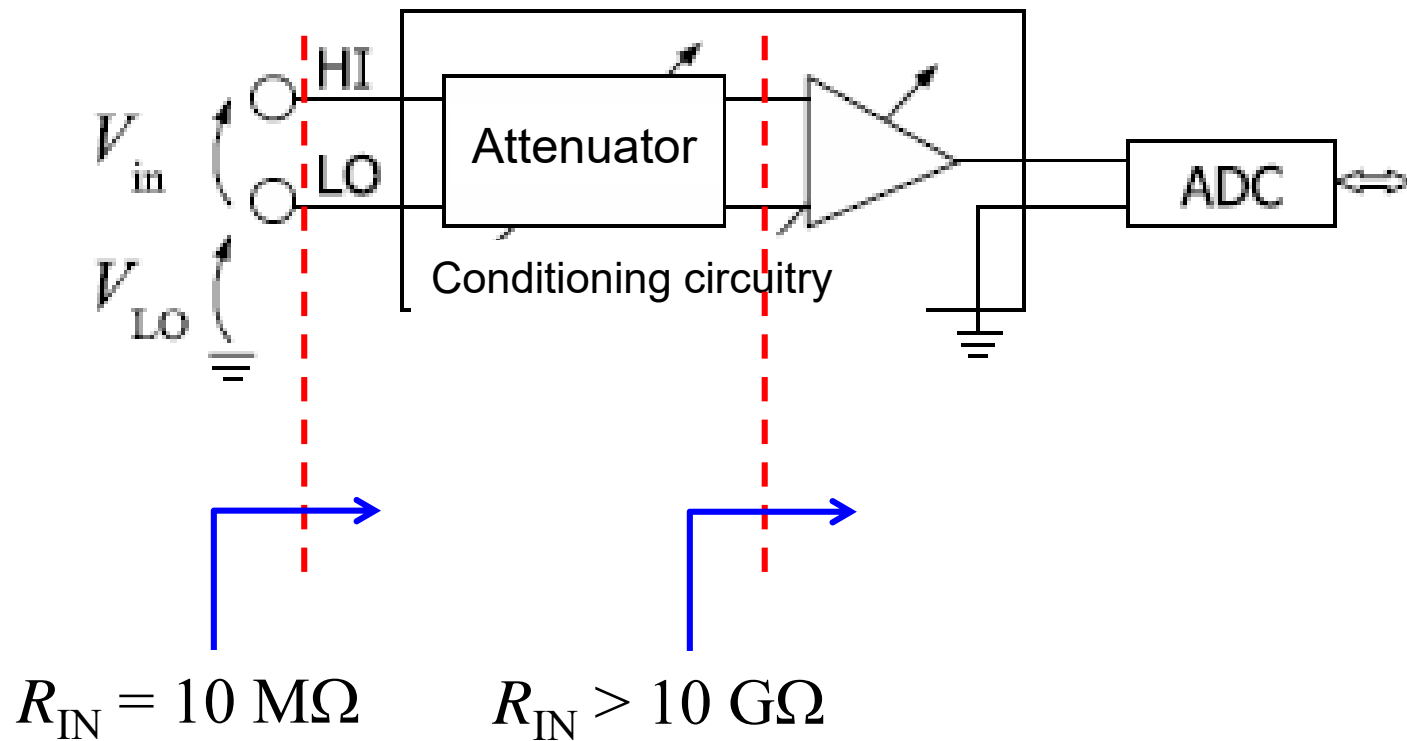

DMM – **DCV** section

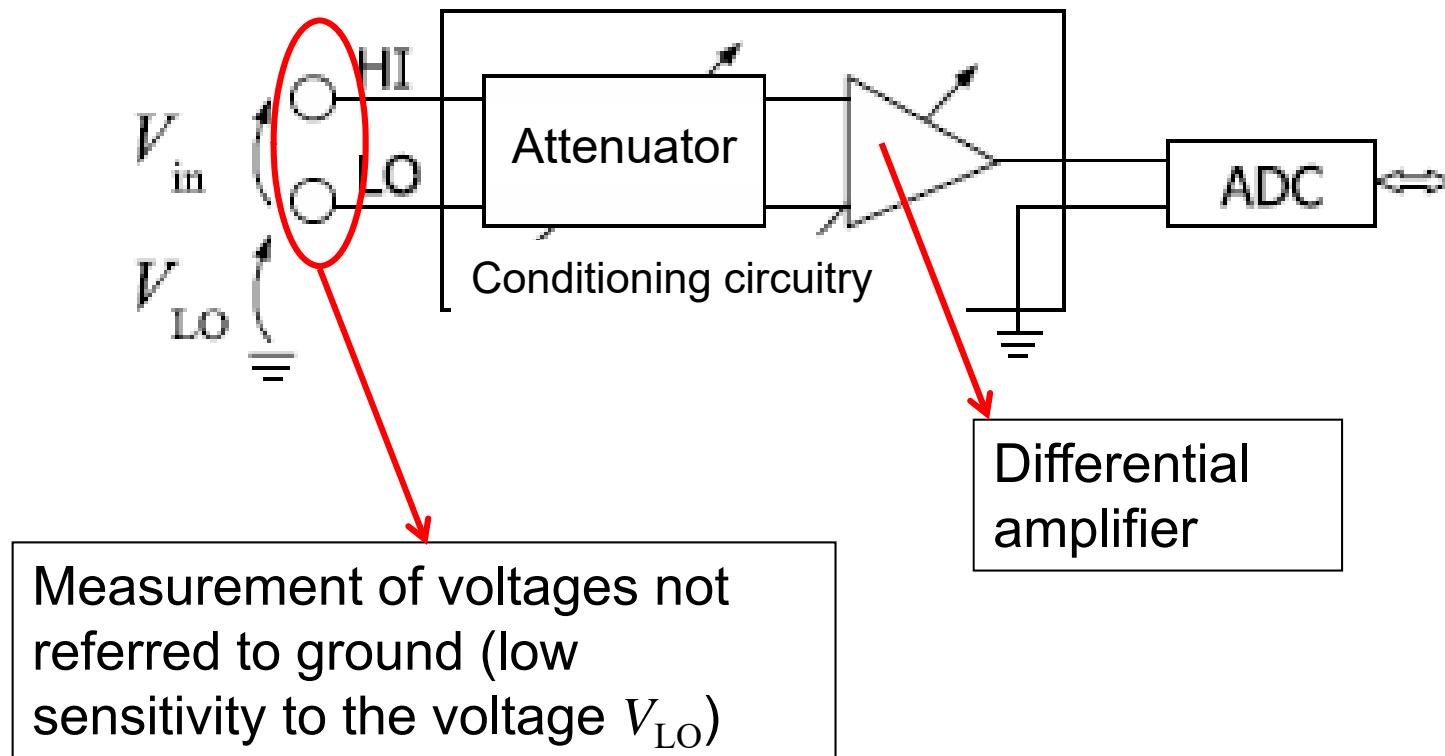

DMM – DCV section

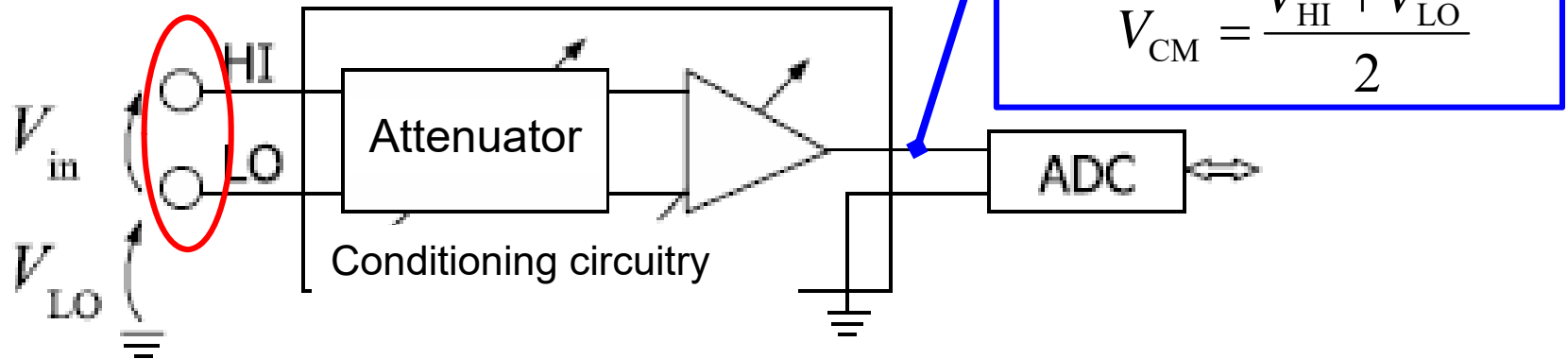

**Common-Mode
Rejection
Ratio**


$$CMRR = 20 \cdot \log_{10} \left(\frac{A_D}{A_{\text{CM}}} \right)$$

A_D : Differential gain

A_{CM} : Common-mode gain

Ideal amplifier $A_{\text{CM}} = 0 \Rightarrow CMRR = \infty$

DMM – **DCV** section

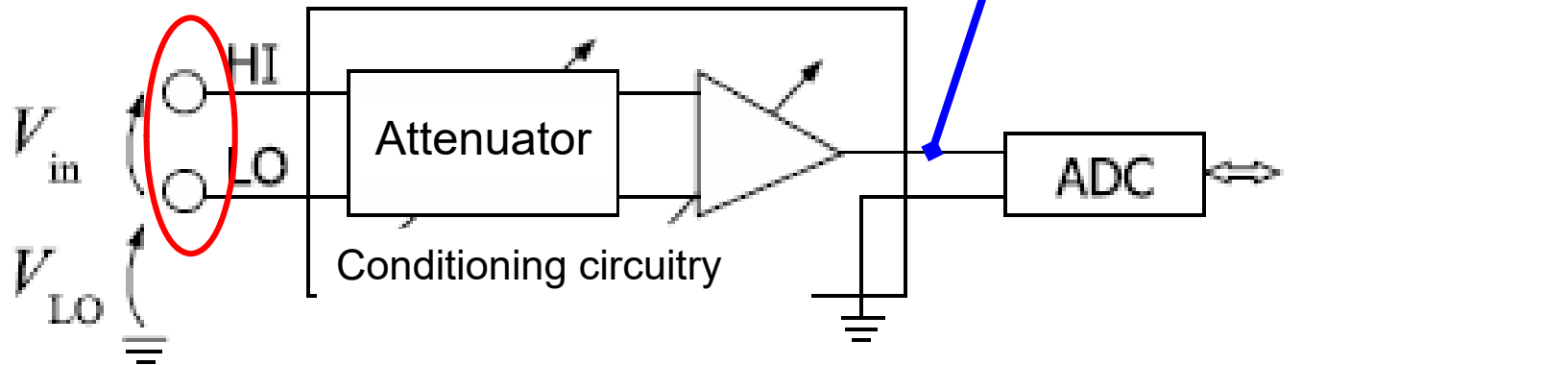


$$CMRR = 20 \cdot \log_{10} \left(\frac{A_D}{A_{CM}} \right)$$

For a real amplifier $A_{CM} > 0$, then the DMM provides an indication $L_{CM} \neq 0$ even though $V_{IN} = 0$

Example: $CMRR = 100$ dB; $V_{HI} = 100$ V; $V_{LO} = 99$ V; $A_d = 1$


$$\Rightarrow V_{out, V_{in}} = 1 \text{ V}; \quad V_{out, V_{CM}} = V_{CM} \cdot 10^{\left(\frac{-CMRR}{20} \right)} = 0.995 \text{ mV}$$

DMM – **ACV** section

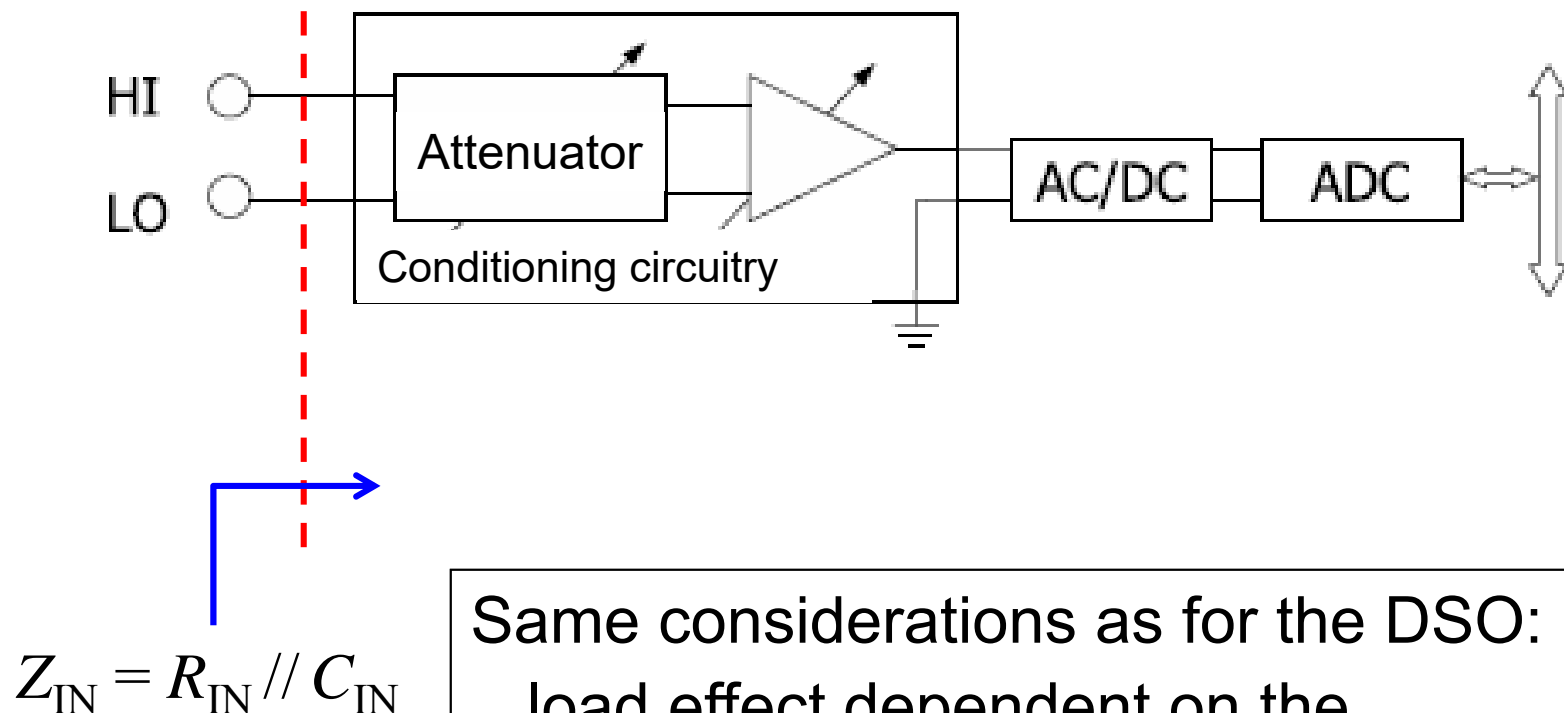

Same considerations as for the DSO:
load effect dependent on the
frequency of the input signal

DMM – **ACV** section

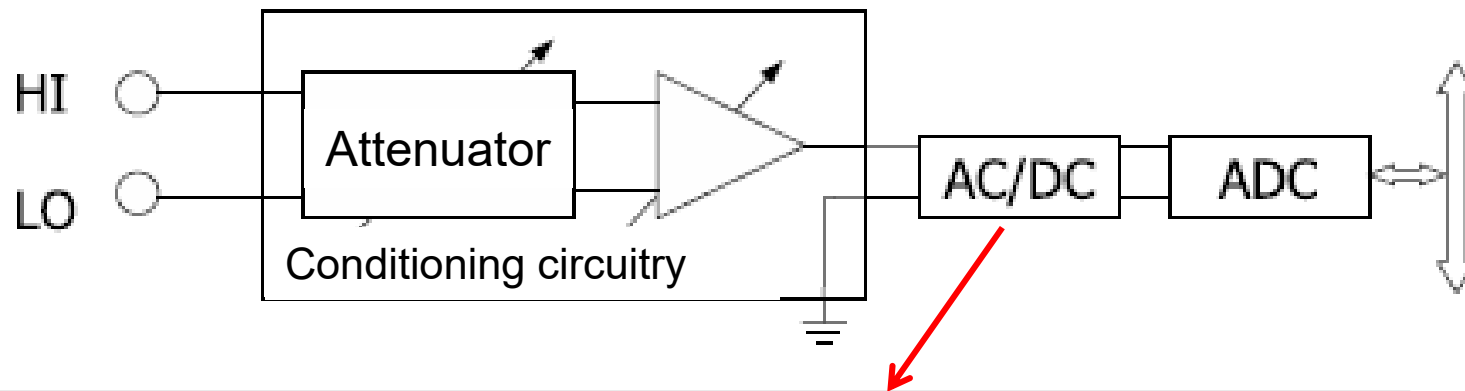


True rms AC/DC converter

↳ It converts the input signal into a DC voltage that is equal to the rms value of the input signal, **regardless of its waveform**

Influence quantity: crest factor of the input signal

$$\hookrightarrow \frac{V_{pk}}{V_{rms}}$$

DMM – ACV section

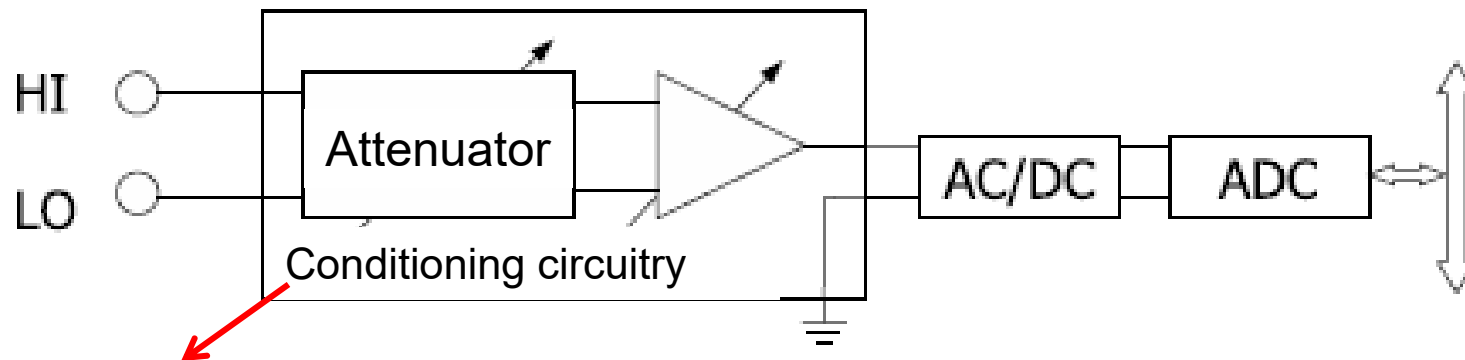

Usually AC coupled


If $v_{in}(t) = V_{DC} + v_{AC}(t) \rightarrow$ only the rms value of the AC component is measured

Remember that $V_{rms} = \sqrt{V_{DC}^2 + V_{rms,AC}^2}$

CMRR for AC signal worse than the CMRR for DC signal

DMM – OHM (2 wire) section

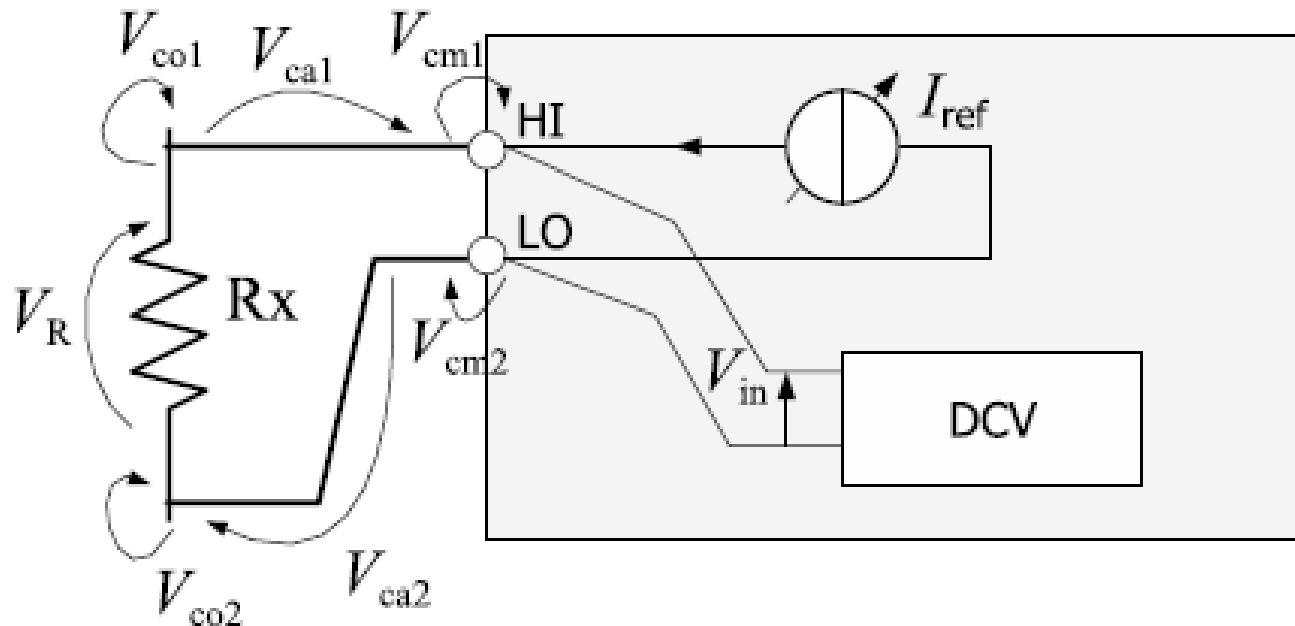Measurement based on the volt-ammeter method




$$R_m = \frac{V_{in}}{I_{ref}} = R_x + R_{con} + R_{wire}$$

Systematic error due to cable and contact resistances

DMM – OHM (4 wire) section

Not always available

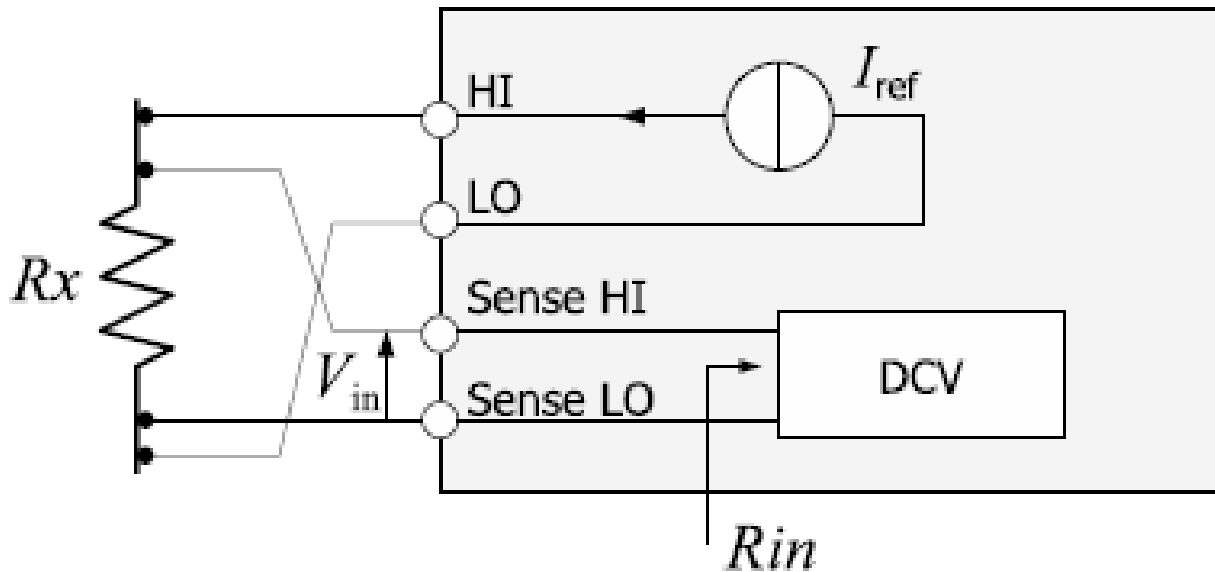

$$R_m = \frac{V_{in}}{I_{ref}}$$

$$\varepsilon_{R_m} = -\frac{R_x}{R_x + R_{in}}$$

Relative systematic error due to the input resistance of the DCV section




Digital Multi Meter

14

DMM – DCI and ACI sections

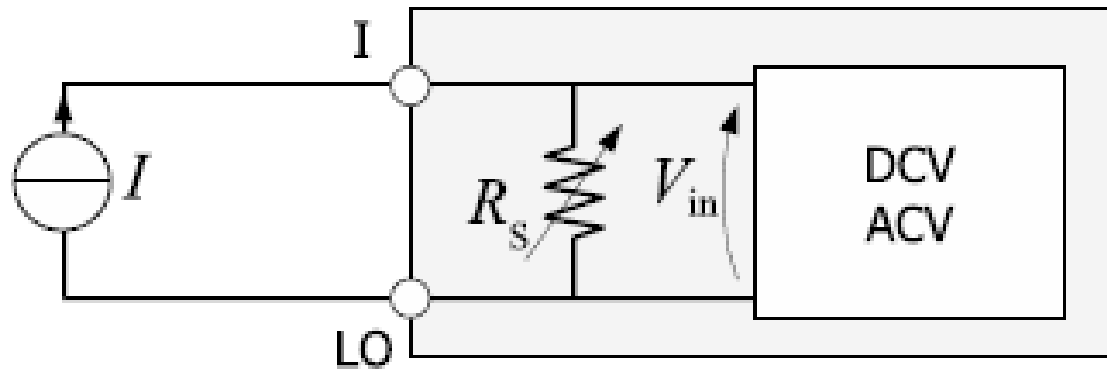Current under measurement converted into voltage by means of internal shunts R_S



$$I_m = \frac{V_{in}}{R_S}$$