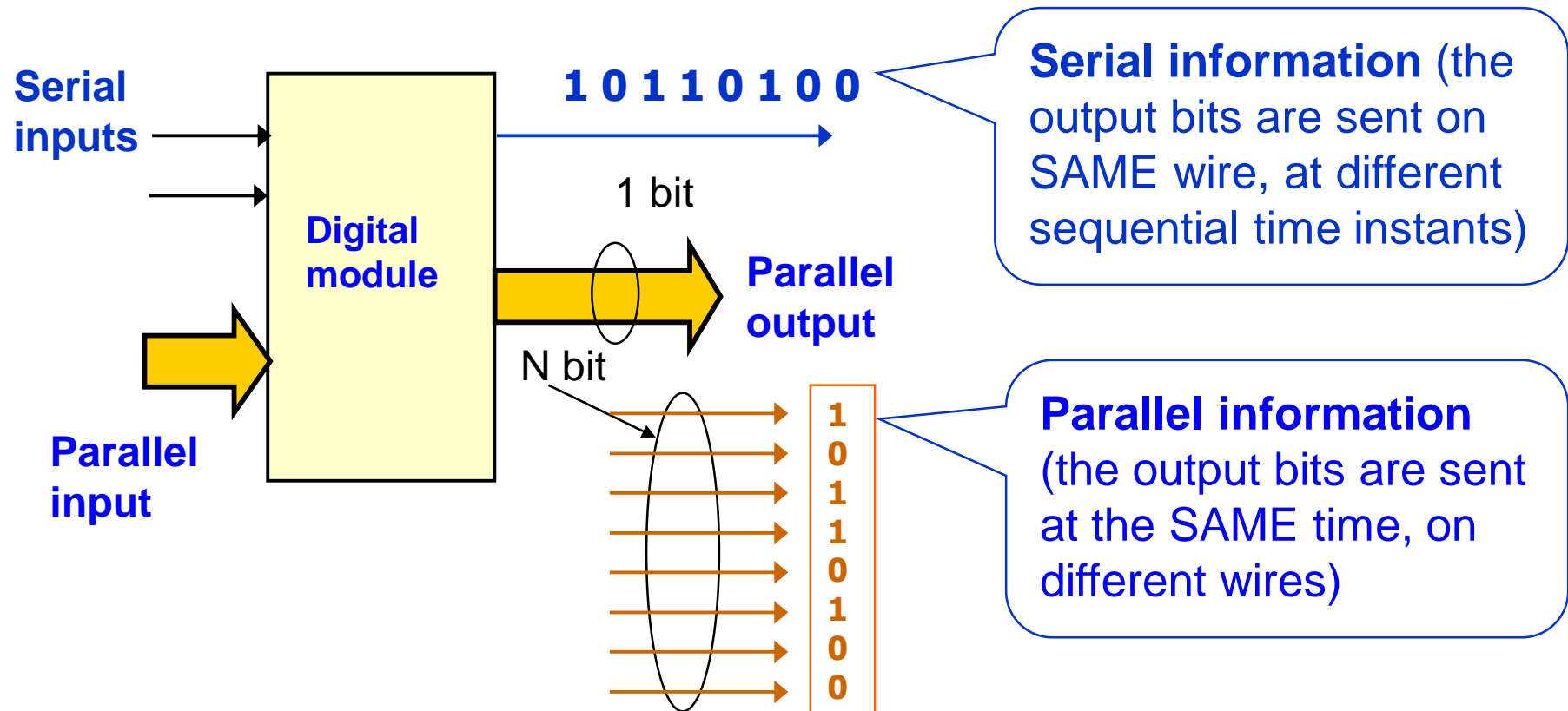


Applied Electronics

Sequential Circuits


Serial and Parallel Signals

- Digital signals can be represented and transferred in **serial** or **parallel** mode



Parallel Data Transfer

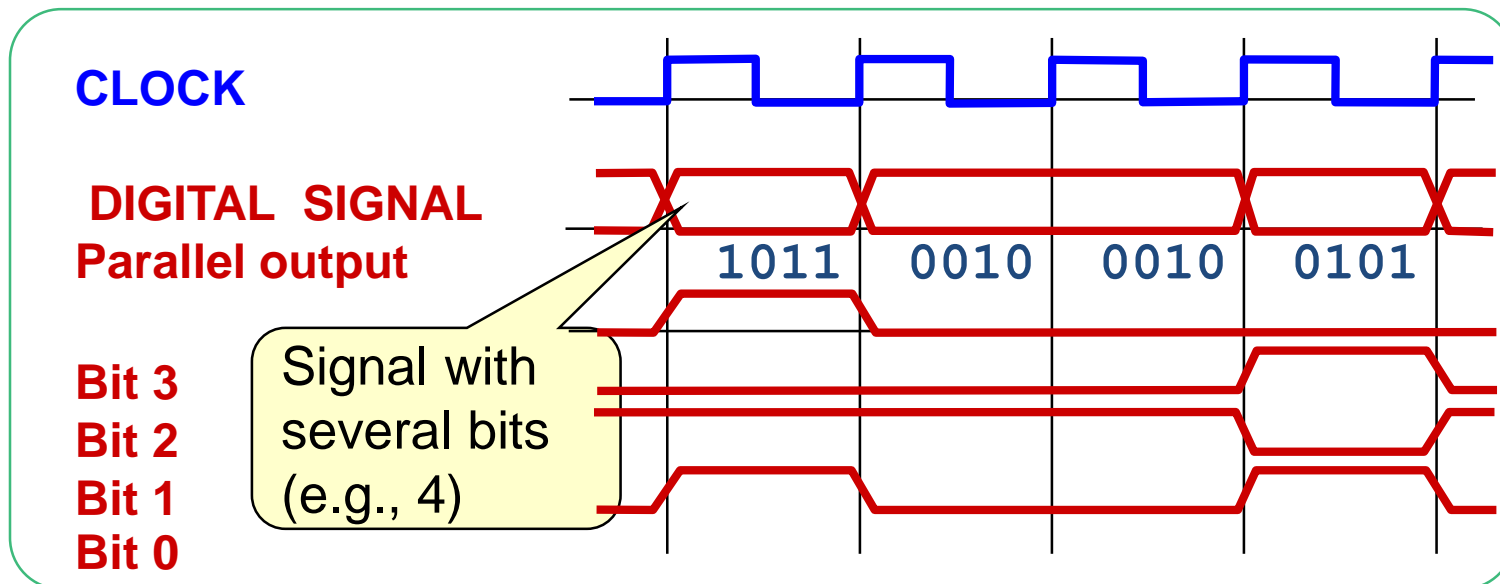- The clock determines the signal rate and ensures synchronization




- Parallel transfer: N bits in one clock cycle
 - ◆ N bits at the same time \Rightarrow total time T_{ck}



Serial Data Transfer

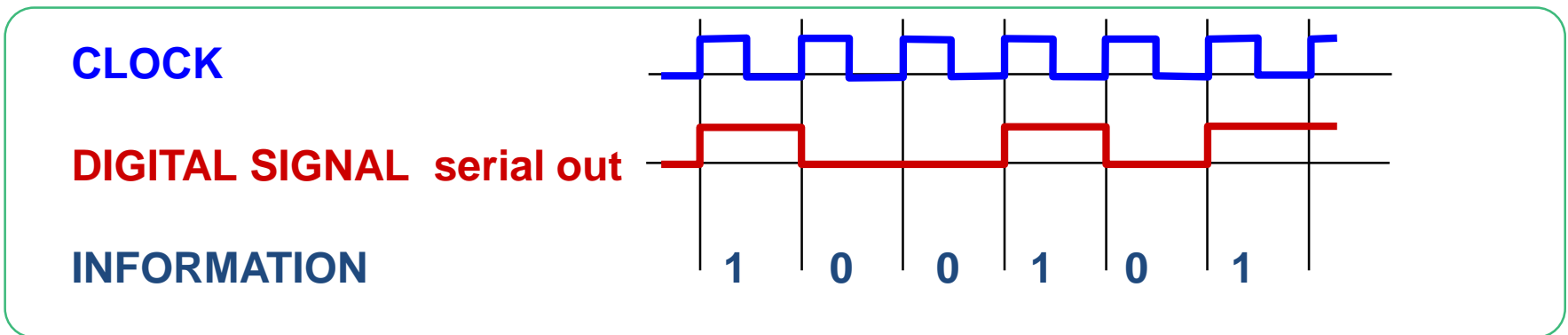- The clock determines the signal rate and ensures synchronization



- Serial transfer rate: N bits need N clock cycles
 - ◆ 1 bit per CK cycle
 - => total time for data transfer: $N T_{ck}$



Benefits and Drawbacks

- Parallel connection
 - ◆ Fast, sends several bits at the same time
 - ◆ Many lines: higher power consumption and cost
 - ◆ Used mainly for short distances
 - Inside ICs, on PCBs among ICs
 - Buses: PCI, ATA, ...
- Serial connection
 - ◆ Slow, one bit at a time (but “time” can be very short)
 - ◆ A single line: reduced power consumption and cost
 - ◆ Used mainly for long distances and “channels”
 - Ethernet, SATA, USB
 - Radio channels



Review of FF Synchronization

- Level-sensitive (LE command)
 - ◆ Latch registers
 - ◆ Transparent when enabled ($LE = 1$)
 - ◆ Memory when blocked ($LE = 0$)
- Edge-sensitive (CK command)
 - ◆ Master-slave registers
 - ◆ Store input state on the active transition of the CK
 - ◆ No transparent mode
- LE and CK
 - ◆ Active Low / High
 - ◆ $H \rightarrow L$ / $L \rightarrow H$




FF and Latch Synchronization Symbols


Four basic synchronization types:

LATCH

POSITIVE

 

NEGATIVE

 


LATCH

(LEVEL sensitive)


Output can change at any time in the transparent phase ($LE = 1$)

EDGE-TRIGGERED

POSITIVE

 

NEGATIVE

 


EDGE-TRIGGERED

(EDGE sensitive)

Output can change **only** on the (active) clock edge



Registers

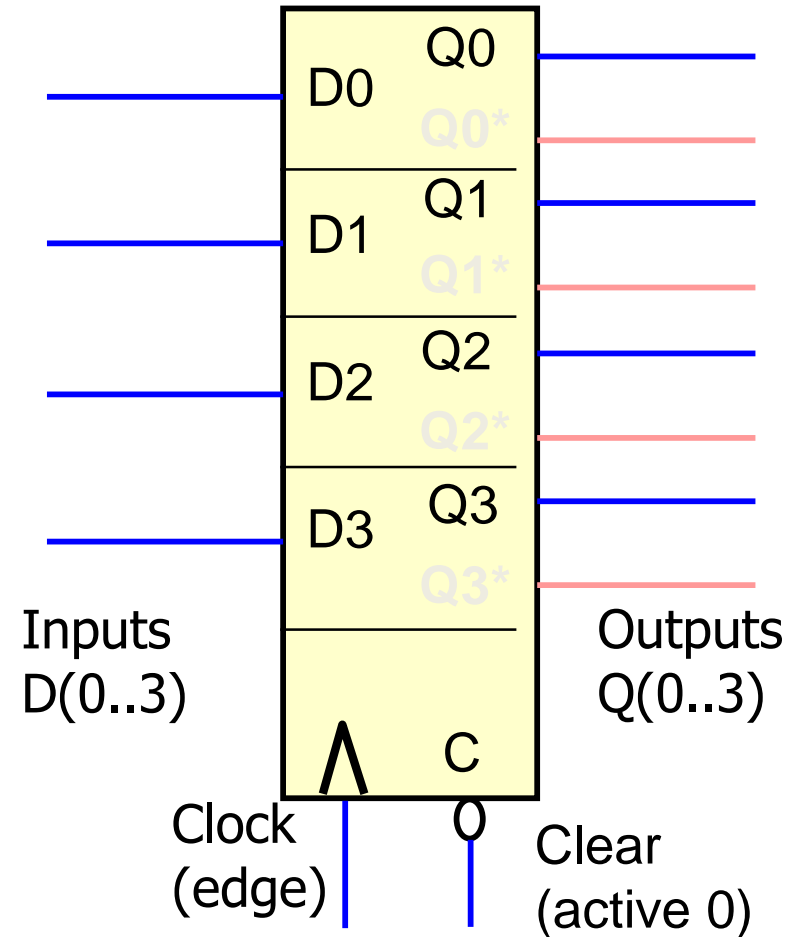- A group of FF with shared commands
 - ◆ Clock
 - ◆ Reset/Clear
 - ◆ ...
- Register type given by the FF clocking
 - ◆ Latch
 - ◆ Edge-Triggered





Parallel Register

  - Parallel input
- Parallel output
- PIPO Register
 - ◆ Parallel In/Parallel Out
- **Parameters:**
 - ◆ Bit number N
 - ◆ Sync (clock) type
 - Level (latch)
 - Edge (D-FF, master-slave)
 - ◆ Other commands
 - Clear, OE, ...





Synchronization Signals

- Level enabled

  


- Edge triggered

  





Example: PIPO With D-FF

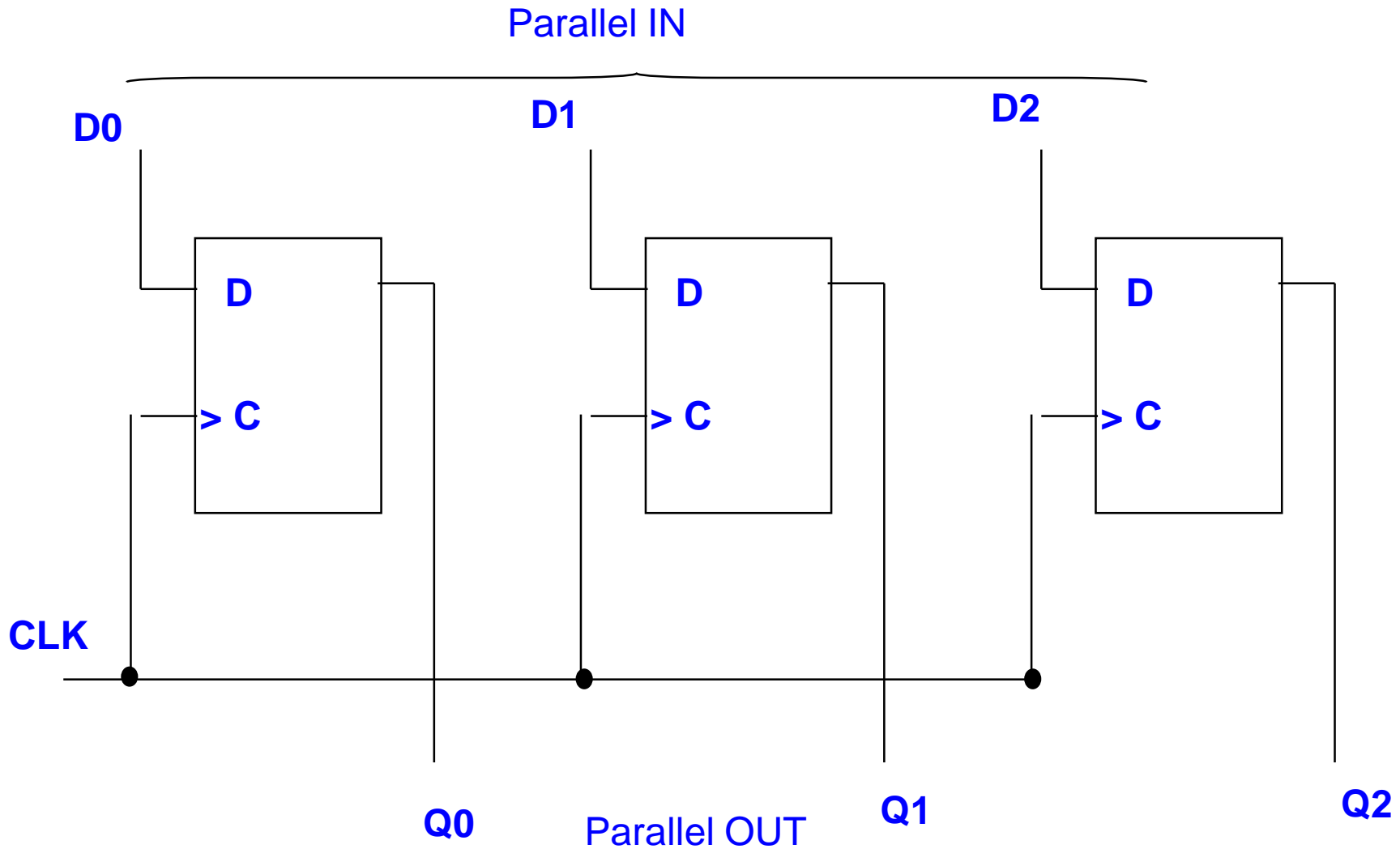

PIPO Register Timing

  
- Latch and master-slave with the same inputs






SISO Shift Register

 - A set of D-FFs with chain connection ($Q_n \rightarrow Q_{n+1}$)
 - ◆ Common Clock CK (common Reset, if any)
- The input Data is moved through the chain
 - ◆ Serial In $\rightarrow Q_1 \rightarrow Q_2 \rightarrow$ Serial Out
- Shift Register: Serial In – Serial Out: SISO



SISO Register Timing

 

Only the Q_3 output is available outside the device.
(or Q_n for a N-stage register).

The SERIN is available in Q_3 after 3 clock cycles





Shift Register SIPO

- Serial data transmission is widely used by peripherals to exchange with a computer
 - ◆ USB (universal serial bus) connects peripherals
- The computer processes data in parallel
 - ◆ We need serial-to-parallel conversion

Shift Register SIPO

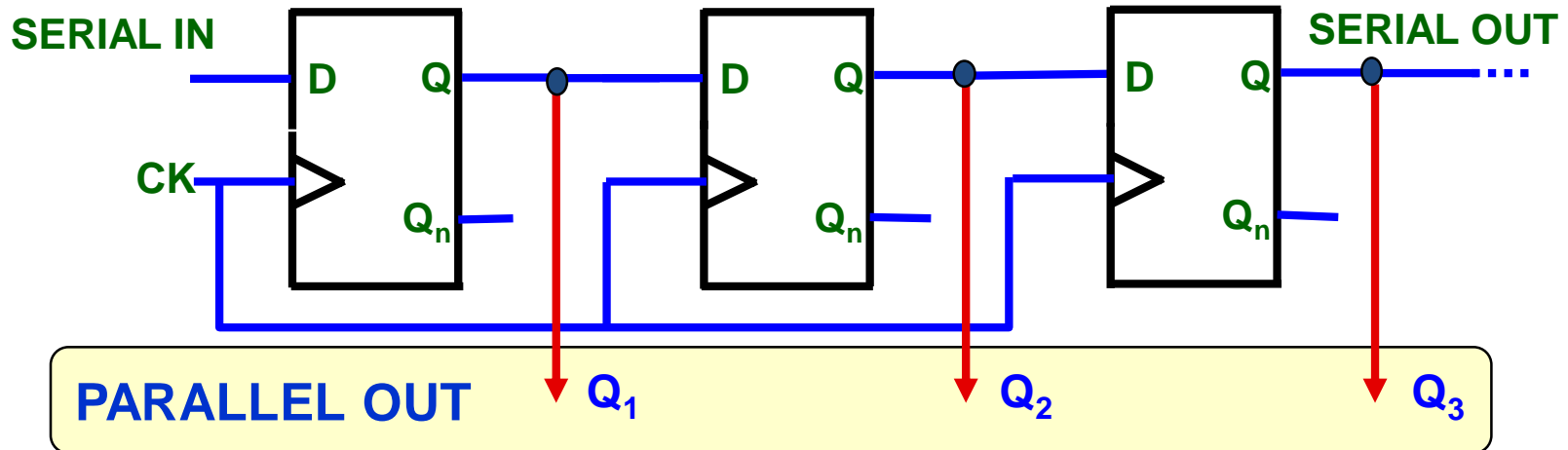
- A set of D-FF with chain connection ($Q_n \rightarrow D_{n+1}$)
 - ◆ Common clock CK (common Reset, if any)
- Can convert serial data into parallel
 - ◆ SIPO register: Serial In \rightarrow Parallel Out



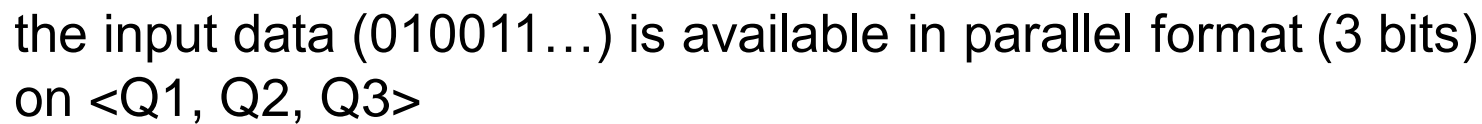

PISO Shift-Register

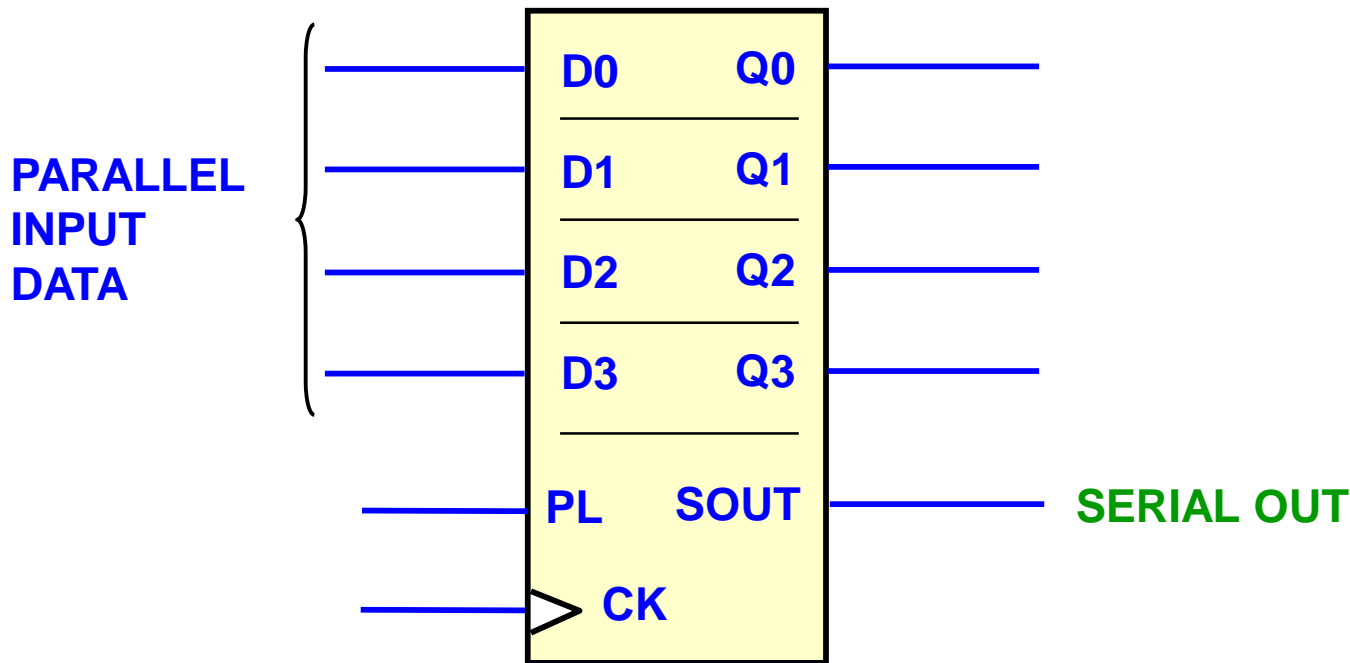- It allows to load all FFs with a single operation
 - ◆ Parallel Load command (PL)
 - ◆ Both parallel and serial outputs are available









Register Summary


- PIPO

 


SIPO

 

- PISO

 


SISO

 

Shift-Register Complete Version

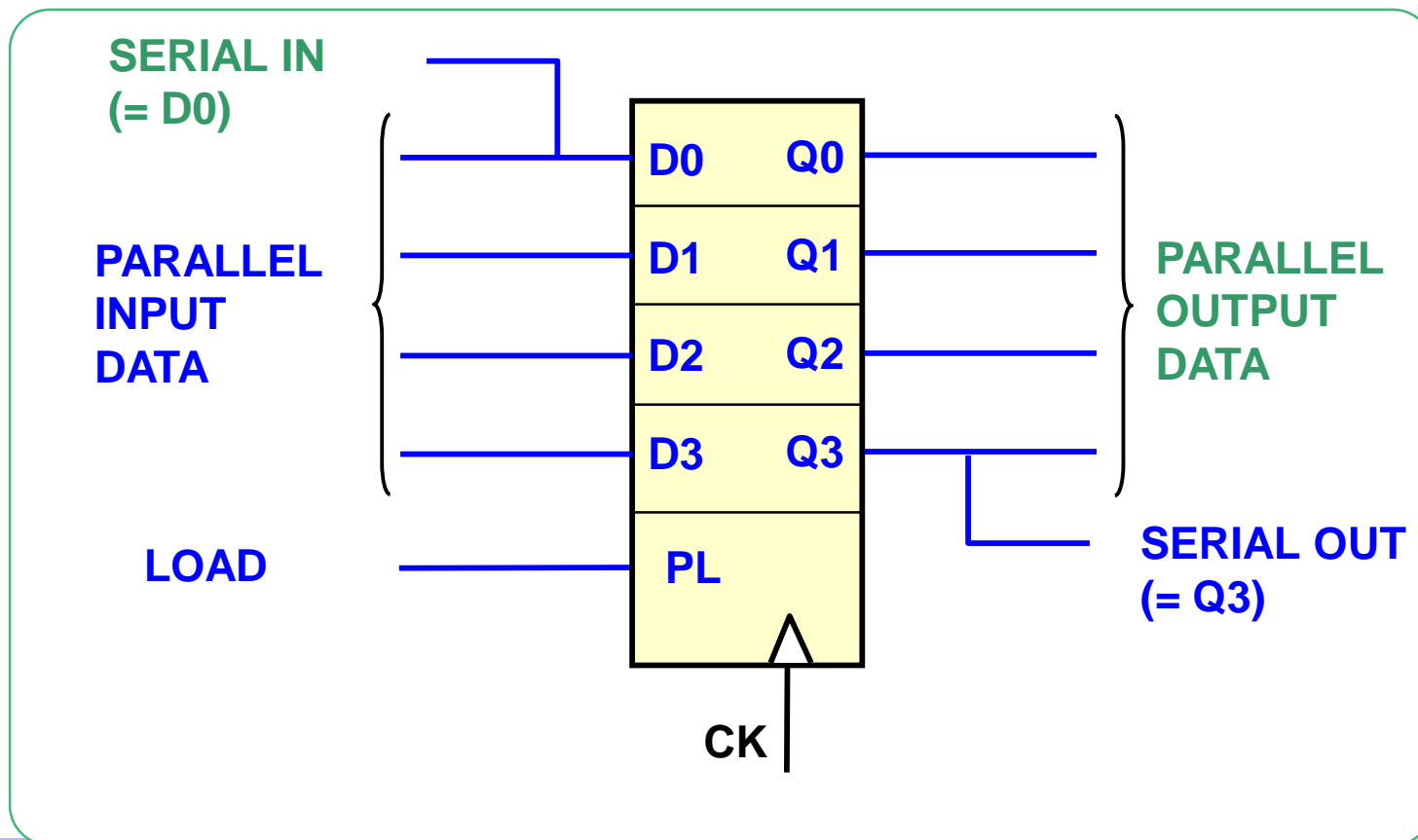
- It can manage both serial and parallel input and output







Application Example: Serial Communication

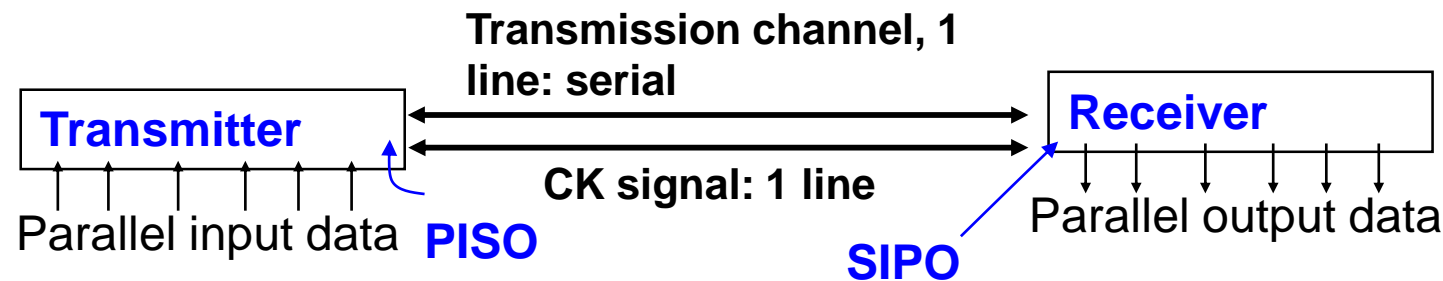- Serial output over channel; just one line needed
- Used in long-distance communication
- Same CK for transmitter and receiver
 - ◆ CK sent over the channel
 - ◆ Or the receiver has a CK recovery circuit
 - Can recover the CK from the data sequence





Divider Modulus 2/4 (Ripple)

  

**Q1 changes
(0,1,0,1...) at
each CK
rising edge**

Count down: the output is 11, 10, 01, 00


Each stage divides the clock rate (CK) by 2

M stages: division modulus 2^M



Counter With JK-FF

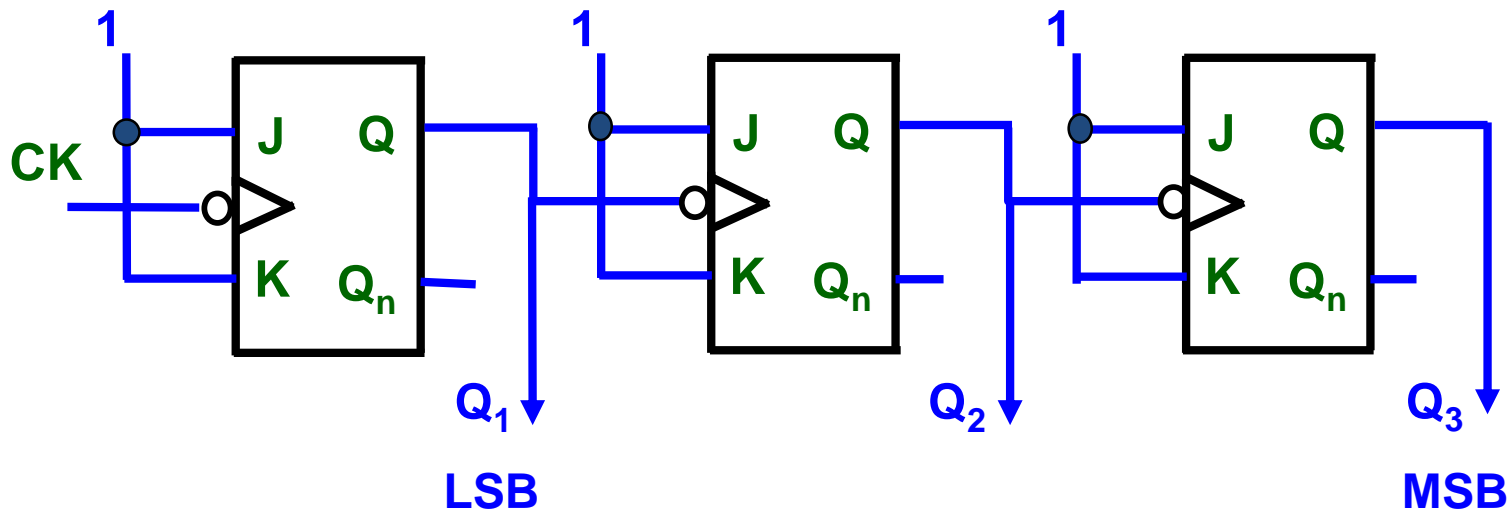- JK-FF toggles on each clock pulse when $J = K = 1$
 - ◆ JK-FF can be used to build counters
- Example: three stage counter (:8)
 - ◆ JK-FF Falling-Edge-Triggered






Asynchronous Counter

- Clocks connected in a chain
- Switching delays add up along the chain
- The circuit is an **asynchronous counter**
 - ◆ The outputs switch with different delays
 - ◆ Single FF: delay T_{pd} (from CK to Q)
 - ◆ Q_M output: delay $T_{pdM} = M T_{pd}$


Asynchronous Counter Timing

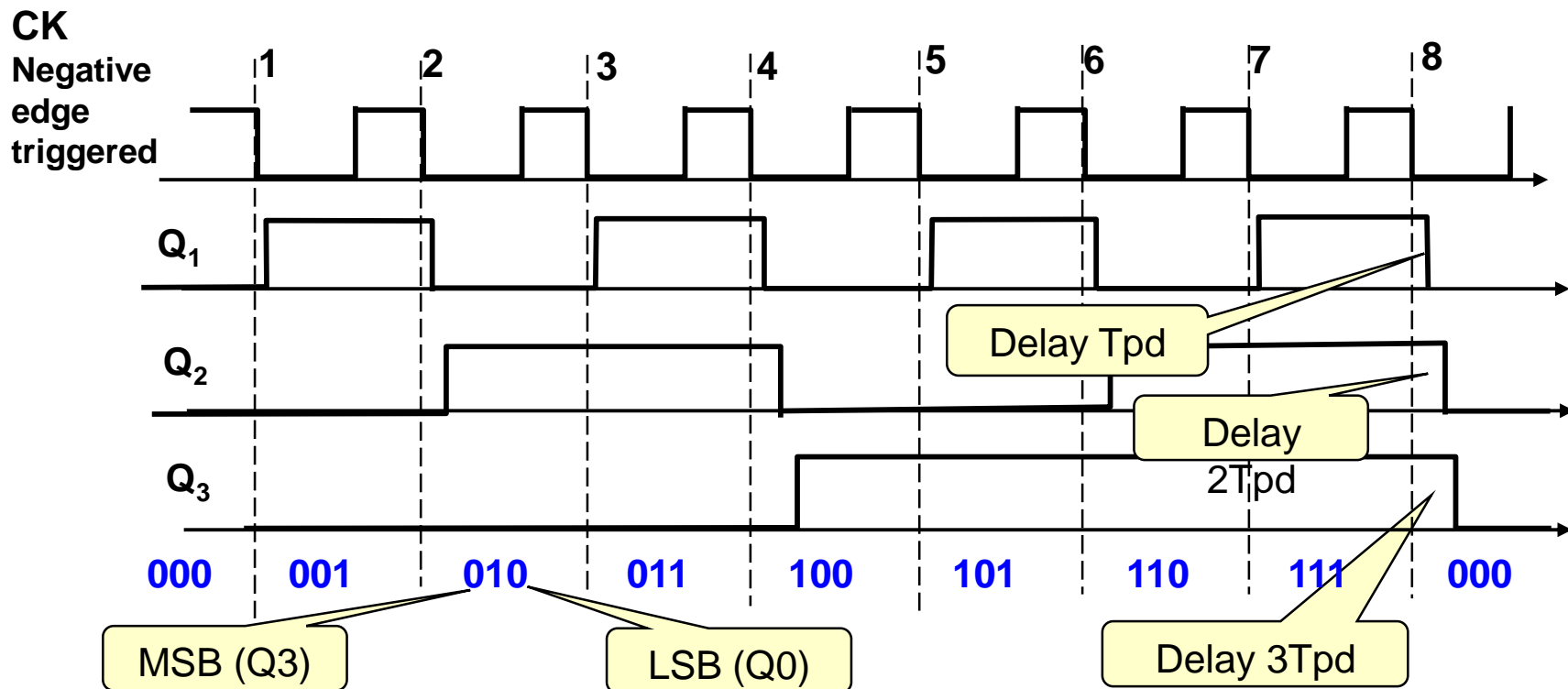- ◆ Each stage toggles at half the rate of the previous one
- ◆ Acts as a frequency divider by 2^n (n is the number of FFs)
- ◆ Generates the sequence of binary numbers




Asynchronous Counter Timing

 - ◆ Each stage toggles at half the rate of the previous one
- ◆ Acts as a frequency divider by 2^n (n is the number of FFs)
- ◆ Generates the sequence of binary numbers




Asynchronous Counter Timing

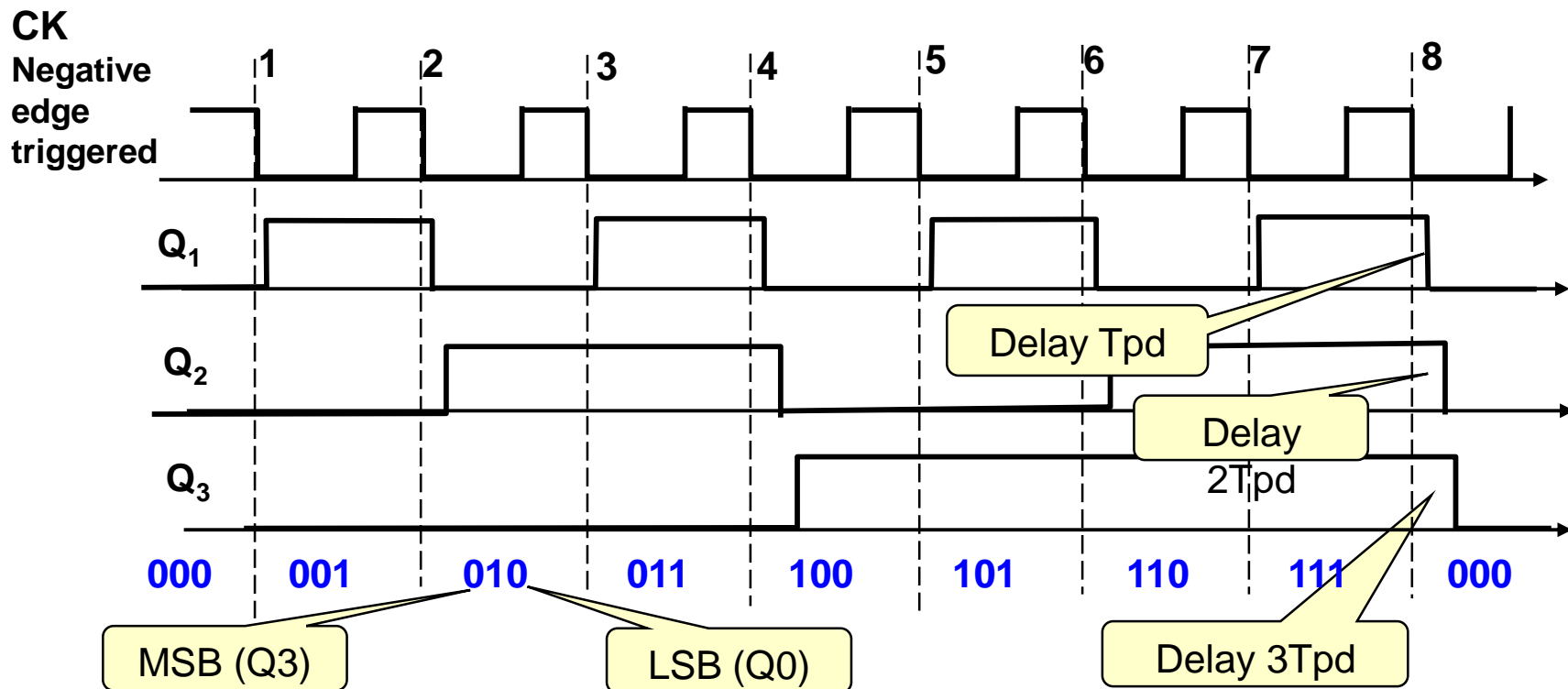- ◆ Each stage toggles at half the rate of the previous one
- ◆ Acts as a frequency divider by 2^n (n is the number of FFs)
- ◆ Generates the sequence of binary numbers



Asynchronous Counter Timing

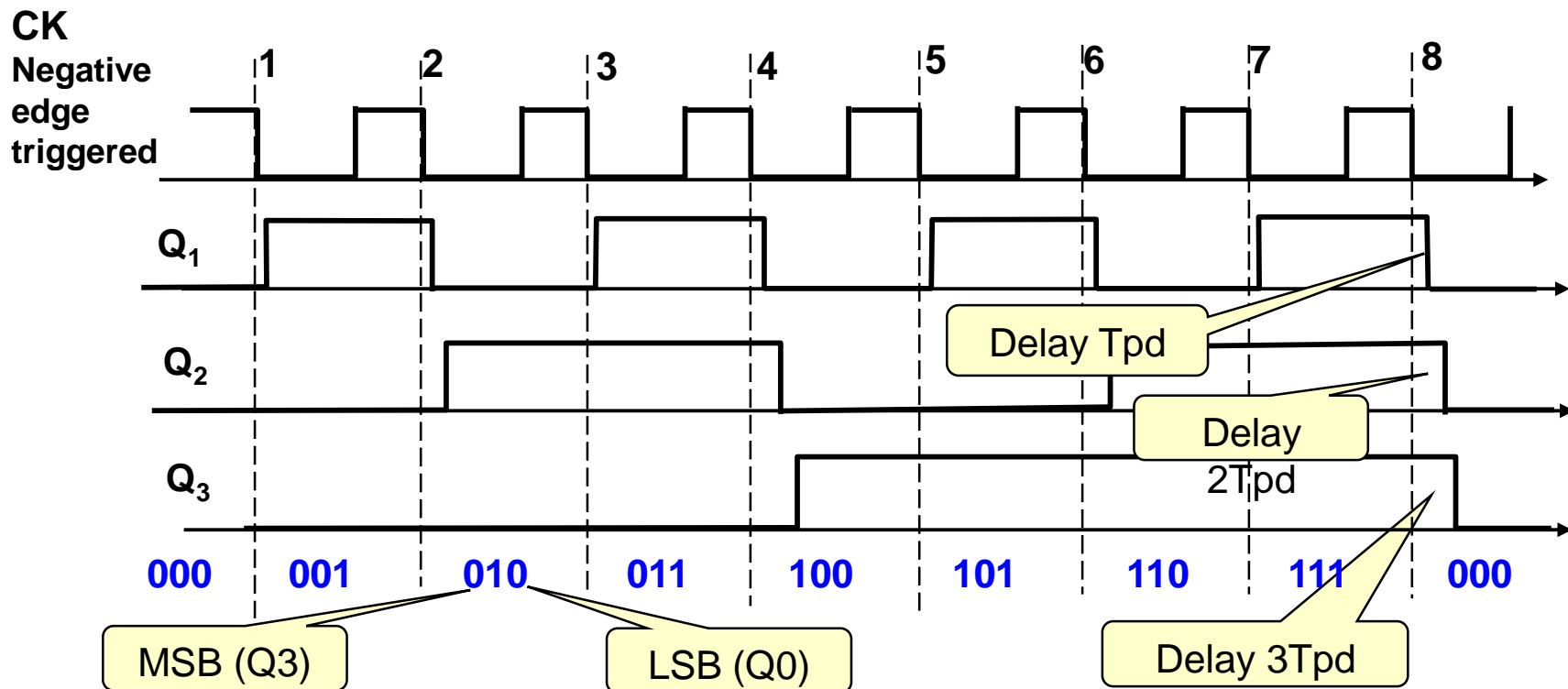- ◆ Each stage toggles at half the rate of the previous one
- ◆ Acts as a frequency divider by 2^n (n is the number of FFs)
- ◆ Generates the sequence of binary numbers







Sync and Async Counters

- Asynchronous counters
 - ◆ The various FFs receive different Clock signals
 - Different delays at various outputs
 - Possible races in transients (transient states)
- Synchronous counters
 - ◆ All FF receive the same Clock signal
 - ◆ All outputs switch with the same delay (**synchronously**)

Example of Synchronous Counter

- Modulus 2^N counter ($N = 4$) - Direct clock to all FFs

Stages 3, 4, ... all the same

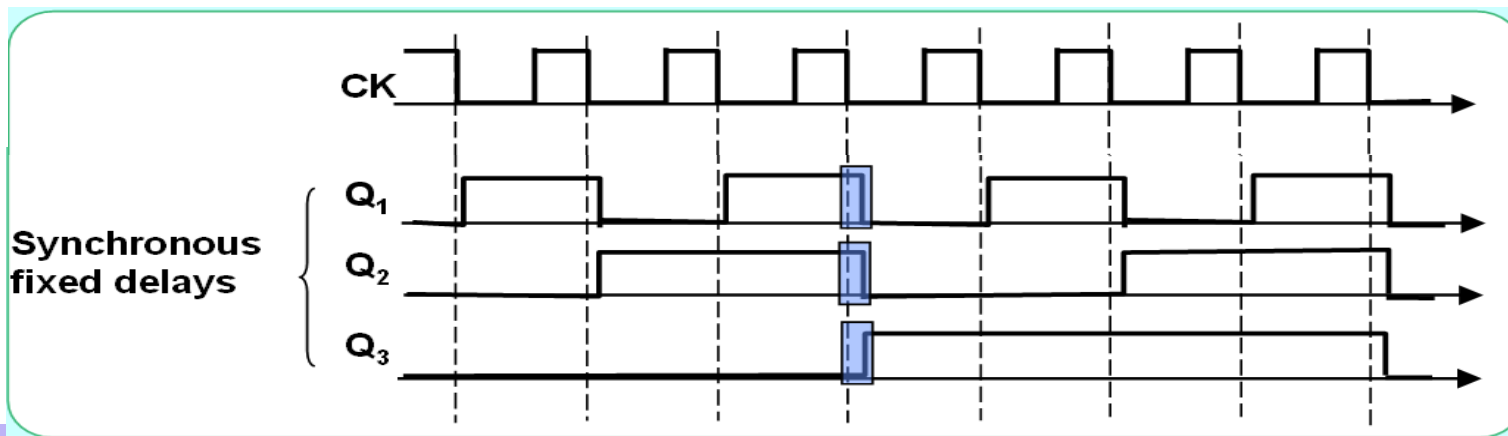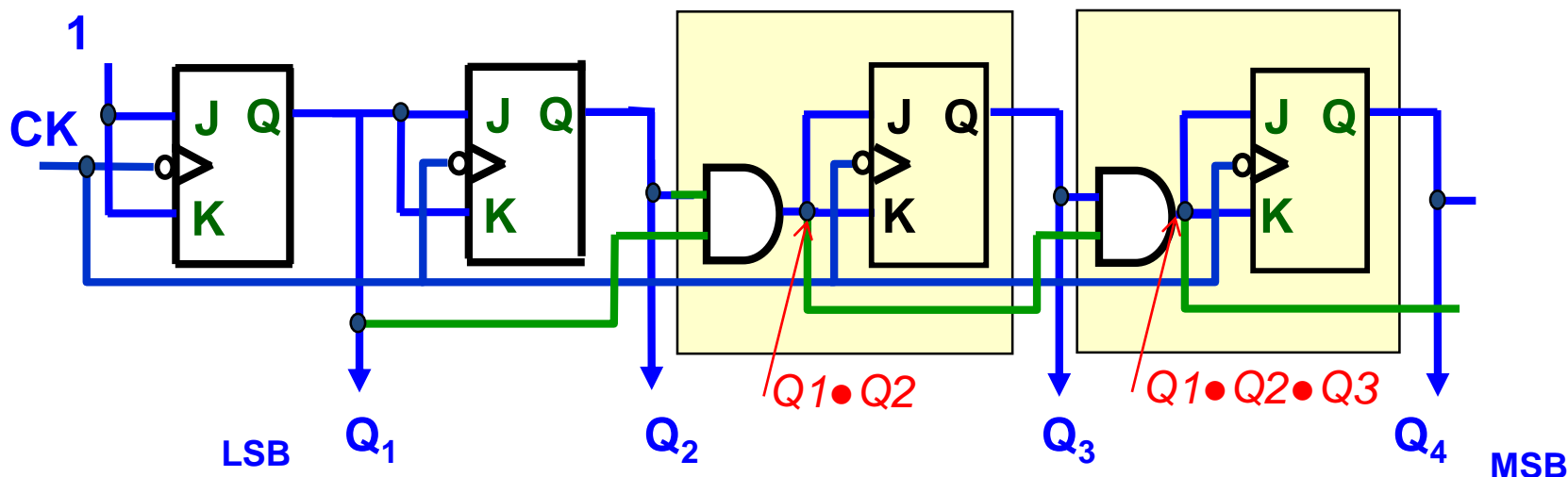




Synchronous Counter Characteristics

- They solve the propagation delay in ripple counters because all flip-flops are connected to the same clock signal
- Thus, each stage changes state at the same time
- Additional circuitry is used to determine which stages must change state on each clock pulse
- Faster than ripple counters, but more complex
- Available in many forms including up, down, up/down, and modulus-N counters




Sync/Async Comparison

 

More General: Any Module Counter

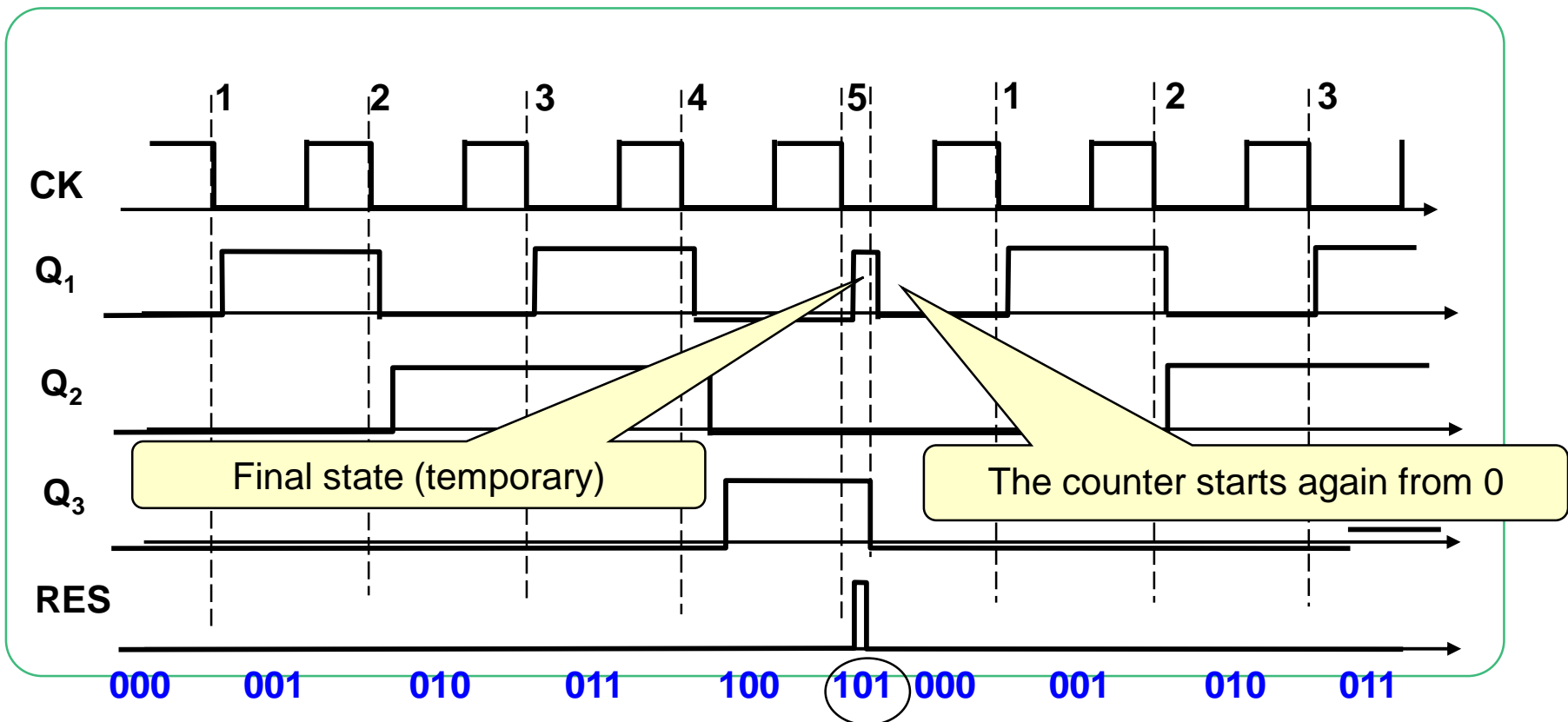- Decodes the module (i.e., 5, 7,)
 - ◆ Issues reset RES to all the FFs (restart from 000...)



A combinational logic circuit decodes this state. The output is the RES signal




Timing Issues

- The signal through combinational logic circuits is delayed by the propagation time: T_P
- For each FF, we must satisfy timing requirements
 - ◆ Set up time
 - ◆ Hold time
- The signal through each FF is delayed by the propagation time $T_{CK \rightarrow Q}$


Maximum Operating Frequency (A)

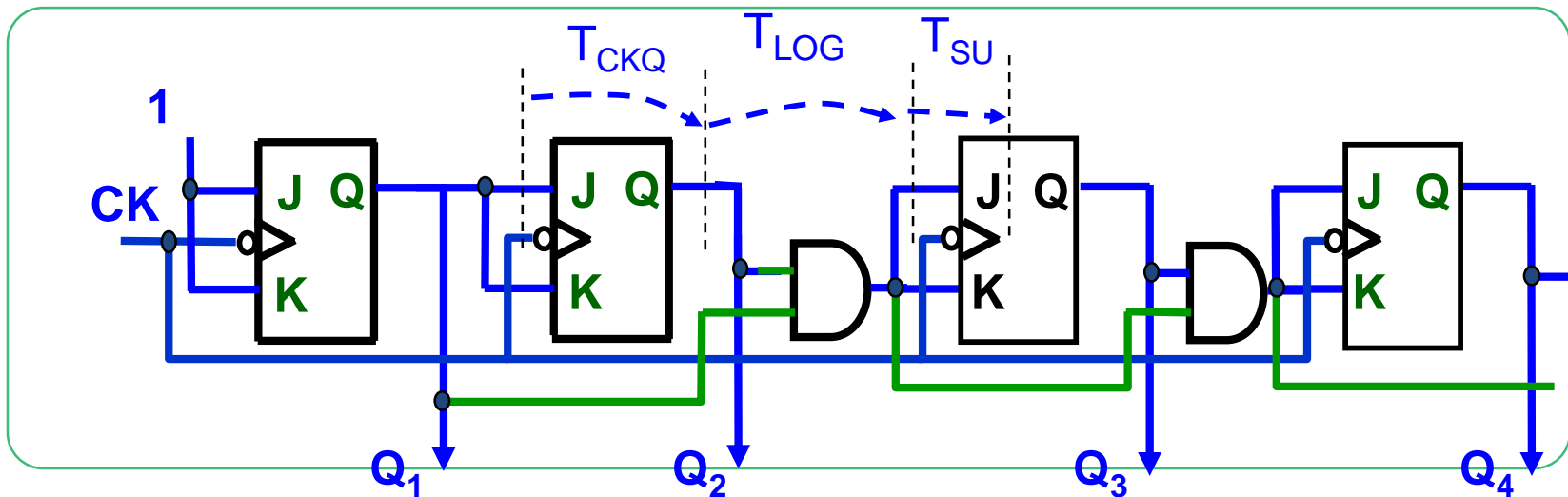- The maximum operating frequency depends on
 - ◆ FF delay $CK \rightarrow Q$: T_{CKQ}
 - ◆ Combinational logic delay (AND gate): T_{LOG}
 - ◆ Setup time required by the FF: T_{SU}




Maximum Operating Frequency (B)

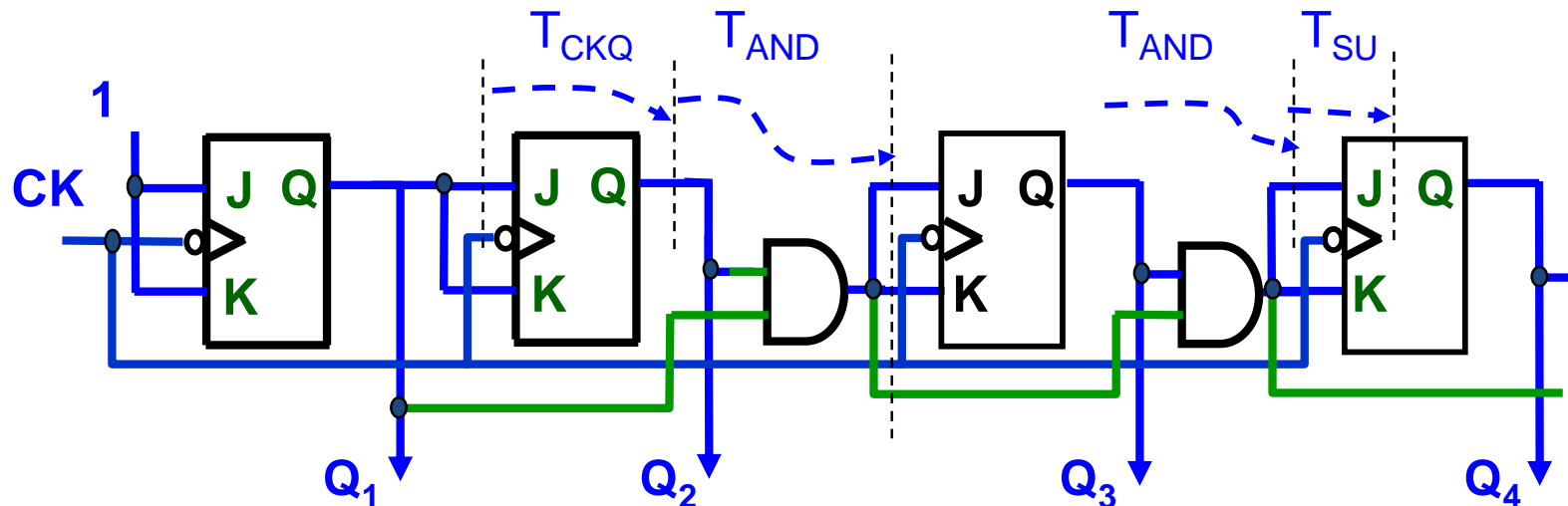- Longest delay path
 - ◆ FF4 combinational input is given by two NAND gates
 - ◆ Total delay: $TD4 = T_{CKQ} + T_{AND} + T_{AND} + T_{SU}$
 - ◆ Each additional stage adds a delay T_{AND}



 Exercise: Synchronous Counter


Draw the timing diagram of the outputs Q_i
(initial condition $Q_i = 0$ at $t = 0$)



Calculate the F_{MAX} given the following parameters:
 $T_{AND} = 10 \text{ ns}$; $T_{CKQ} = 8 \text{ ns}$; $T_{SU} = 3 \text{ ns}$




Synchronous Counter Outputs

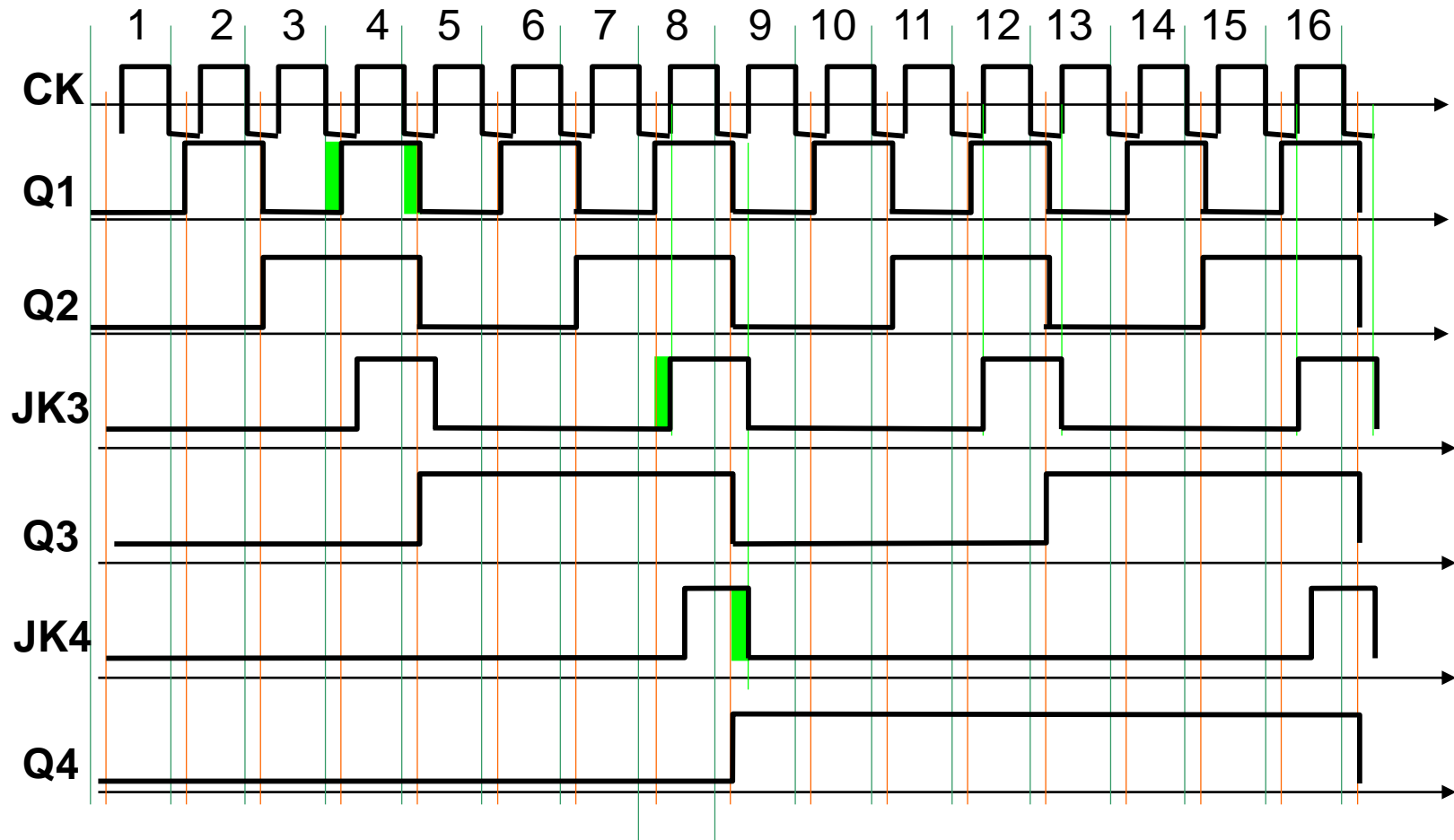




- $$t_{CK_Q} + t_{AND} + t_{AND},$$

 therefore $T_{CK} > t_{CK_Q} + 2t_{AND} + t_{SU}$




Finite States Machines (FSM)

 - The system STATE is defined by the memory elements (FF) state
- State transitions are represented by arcs, conditioned by internal and input variables
- Each internal state has a corresponding OUTPUT state
- This representation is the *State Diagram*



Washing Machine FSM

 
- The control unit for a washing machine is an example of simple sequencer
- Starting state: A; next B, C, D, A, ...



STATE	Q_1	Q_0	
A	0	0	LOAD WATER
B	0	1	WASH
C	1	0	SPIN
D	1	1	DRY

Next State Network

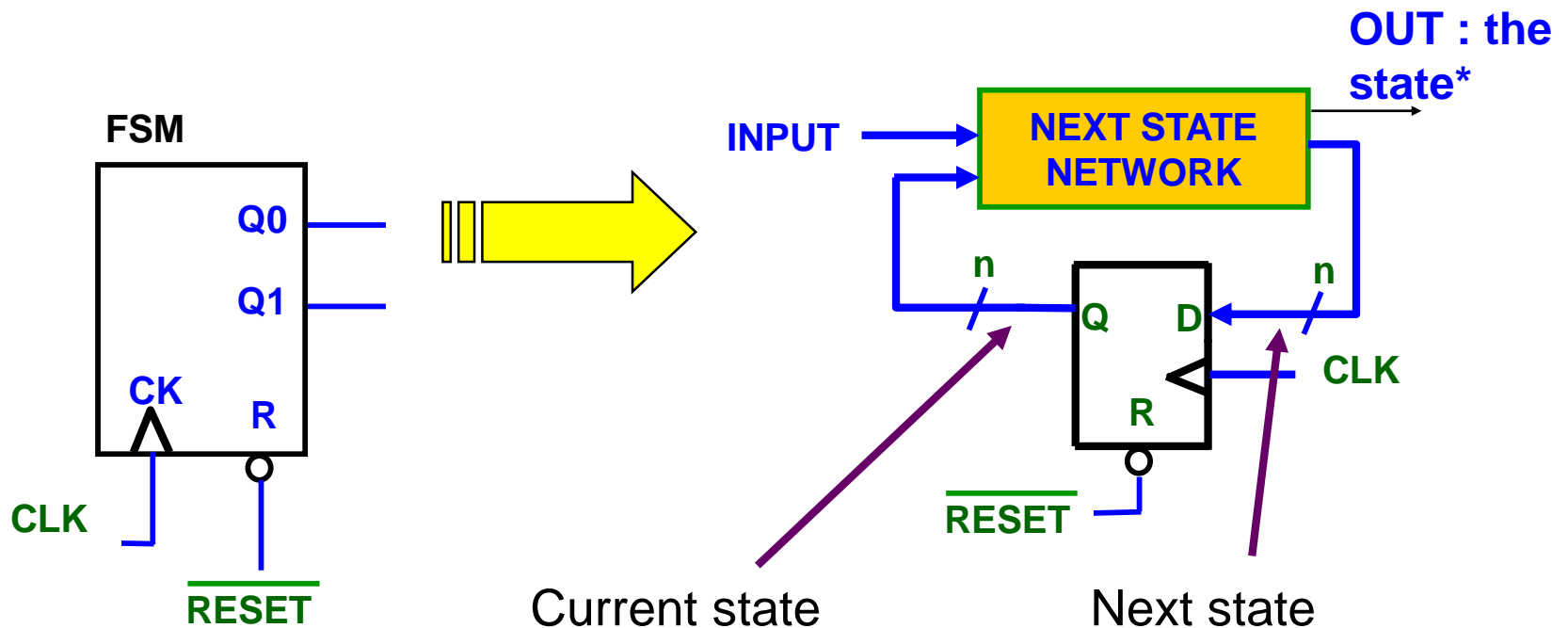
- The FSM advances one step on each clock trigger edge, according to the sequence defined by future state network



*** The new output state is a combinational logic operation between the input and the previous state (Output of the FF, memory element)**

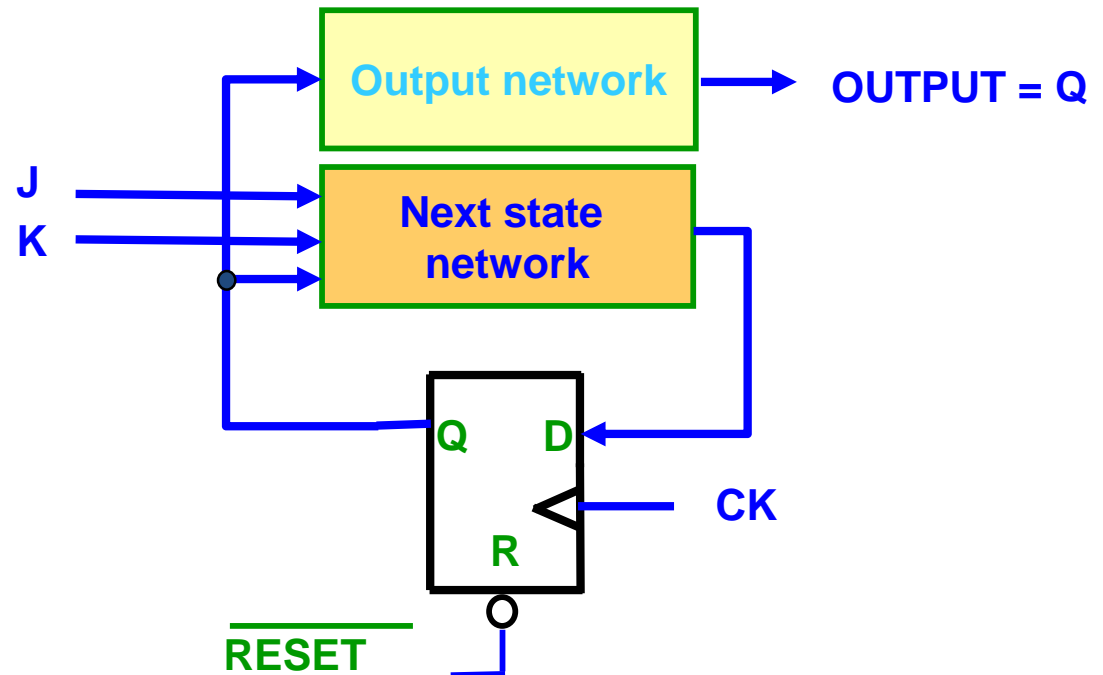Exercise: Design a Simple FSM

- Design an FSM that acts as a flip-flop JK
- It has two inputs (+ RESET): J, K
- It has two states
 - ◆ A (for output $Q = H$)
 - ◆ B (for output $Q = L$)
- The output network is just a wire connecting the FF to the output Q





State Diagram


J K		Current State (Q)	Future State (D)
Memory	L L	L	L
		H	H
K=H sets the output to L	L H	L	L
		H	L
J=H sets the output to H	H L	L	H
		H	H
Toggle	H H	L	H
		H	L

The next step state is determined by the equation:

$$D = Q_{n+1} = \bar{Q} J + Q \bar{K}$$

Combinational logic sets next state; inputs of the combinational logic circuits are: J, K and Q

FSM for JK FF

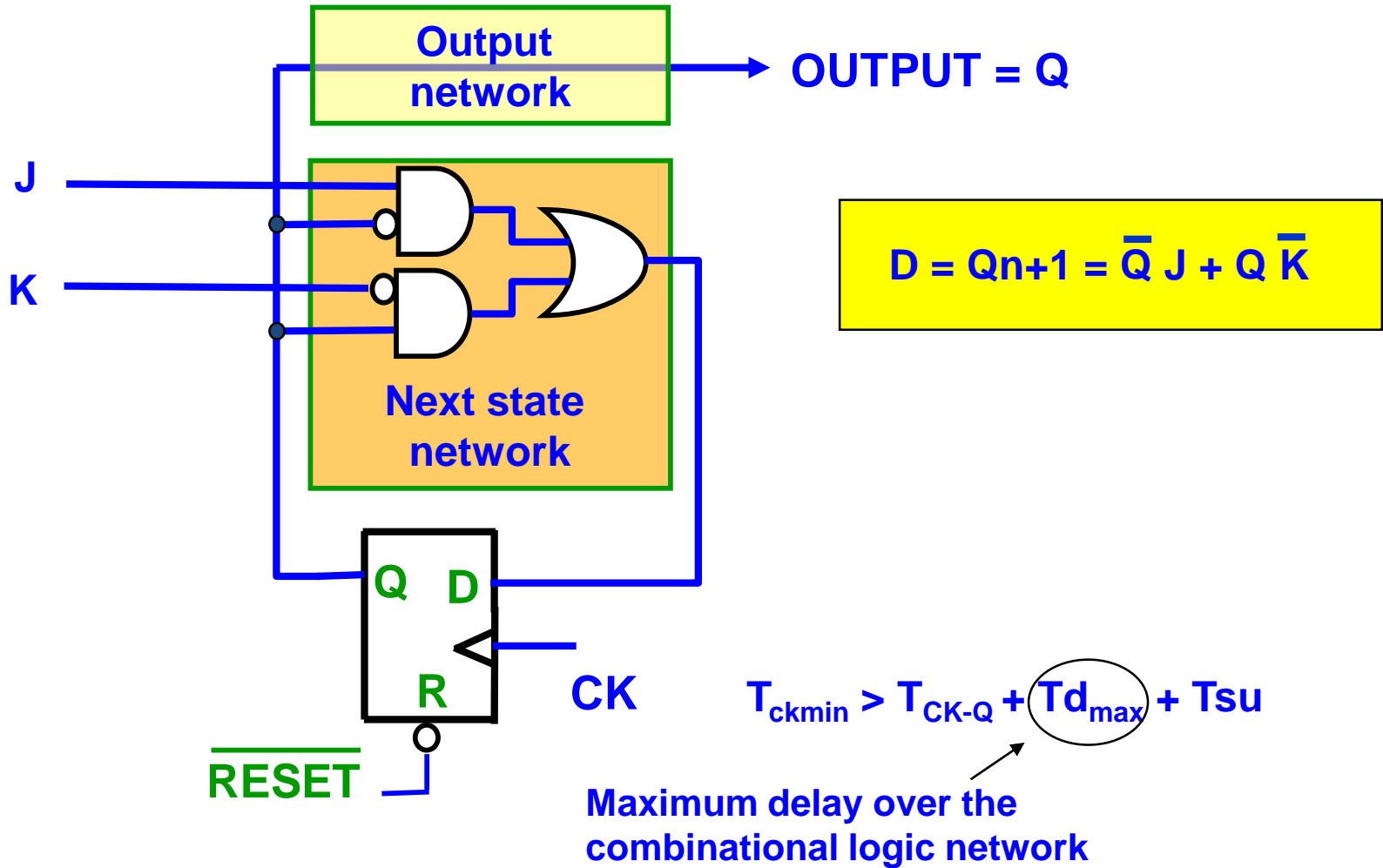



Review Questions

- How many FFs needs a counter modulus 17 (in synchronous and asynchronous implementations)?
- Draw the schematic of an asynchronous divider modulus 32 using D-FFs.
- Draw the schematic (gates and FFs) of a serial-to-parallel converter.
- An FSM has 9 states. How many FFs does it need?
- Do synchronous counters have output delays dependent on the counting modulus?
- Connect two 4-bit SIPO registers to make an 8-bit SIPO.
- Which parameters determine the max clock frequency of an FSM?