



Applied Electronics

E3 – Switching regulators

- Partialization regulators
- Buck and boost regulators
- Parameter evaluation
- Component choice



Lecture E3: switching regulators

- Switching power control
 - ◆ Duty cycle change
- Switching regulators
 - ◆ Buck
 - ◆ Boost
 - ◆ Buck-boost
 - ◆ Flyback
- References
 - ◆ Maloberti: Understanding Microelectronics...: Ch. 13.6



Switching regulators

- Energy is controlled using a switch
 - ◆ ON → full power
 - ◆ OFF → no (zero) power
 - ◆ Low-pass filter towards the load (or the load itself filters)
- Voltage control through duty cycle of the ON/OFF switch
- High performance
 - ◆ Ideal switches → no dissipation, no loss
 - ◆ Real switches → losses from R_{ON} , I_{OFF} , transients, ...
- Applications
 - ◆ Amplifiers: class D, E, ...
 - ◆ Power supplies and switching regulators






Low-pass filter at the output

- Regulator delivers energy to load as a rectangular wave
 - ◆ Average value is related to the duty cycle, **useful output**
 - ◆ Fast edge signal, high harmonic content
 - Noise, lost energy, ...
 - ◆ Low-pass filter required at the regulator output
- The filter can be
 - ◆ Intrinsic to the load (e.g., for a mechanical actuator)
 - Has a much slower response than the ON/OFF command frequency
 - ◆ Added low-pass filter to regulator output
 - RC → cheaper, losses in R, used for low powers
 - LC → more expensive, low losses, used for high power



Switching regulator

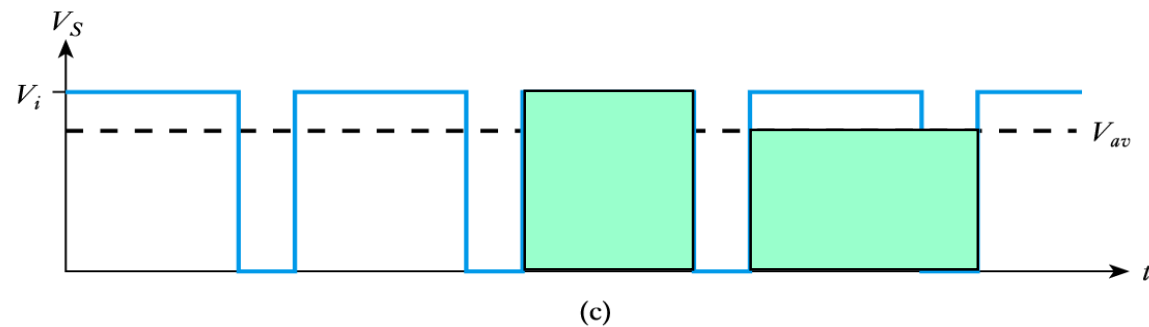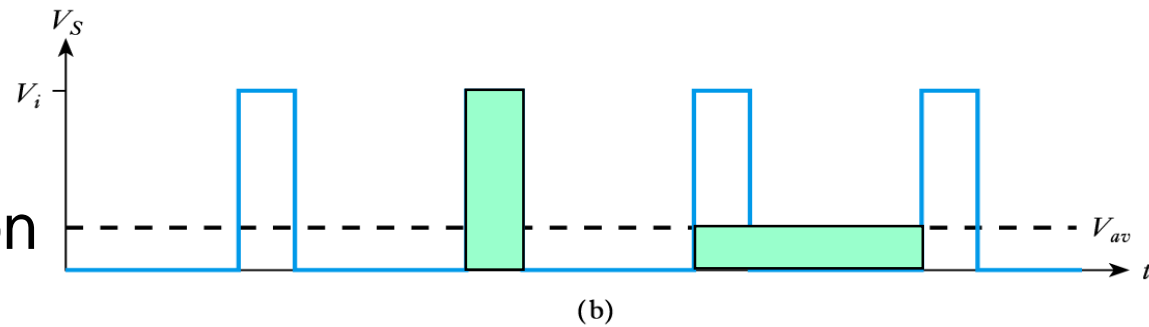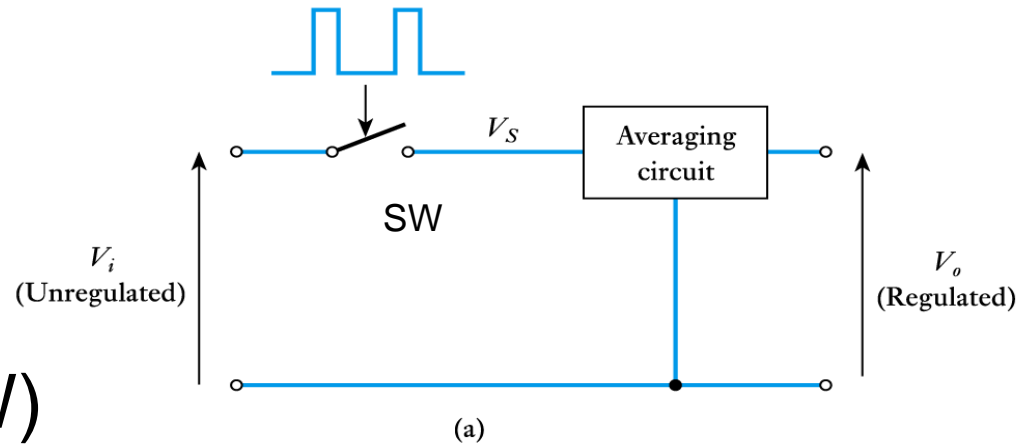- **D-class** amplifier
- Power delivered to the load controlled by the duty cycle of the switch (SW)
- The load “averages” the energy
 - ◆ Low-pass transfer function
- **High efficiency**
 - ◆ Ideal switch, no losses




Accumulation and filtering with LC net.

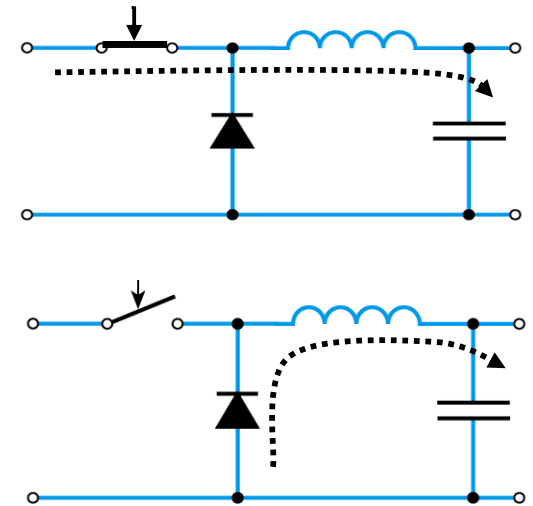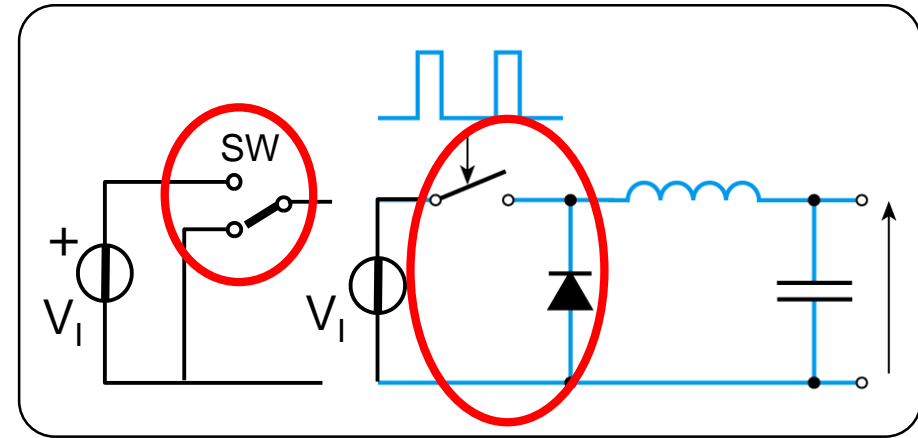- The square wave is generated by a switch, SW
- A branch of the SW is made with a diode (more modern use MOS)
- Inductance L tends to keep the current constant
- When the switch opens, the current flows through the diode



Switching regulator with feedback

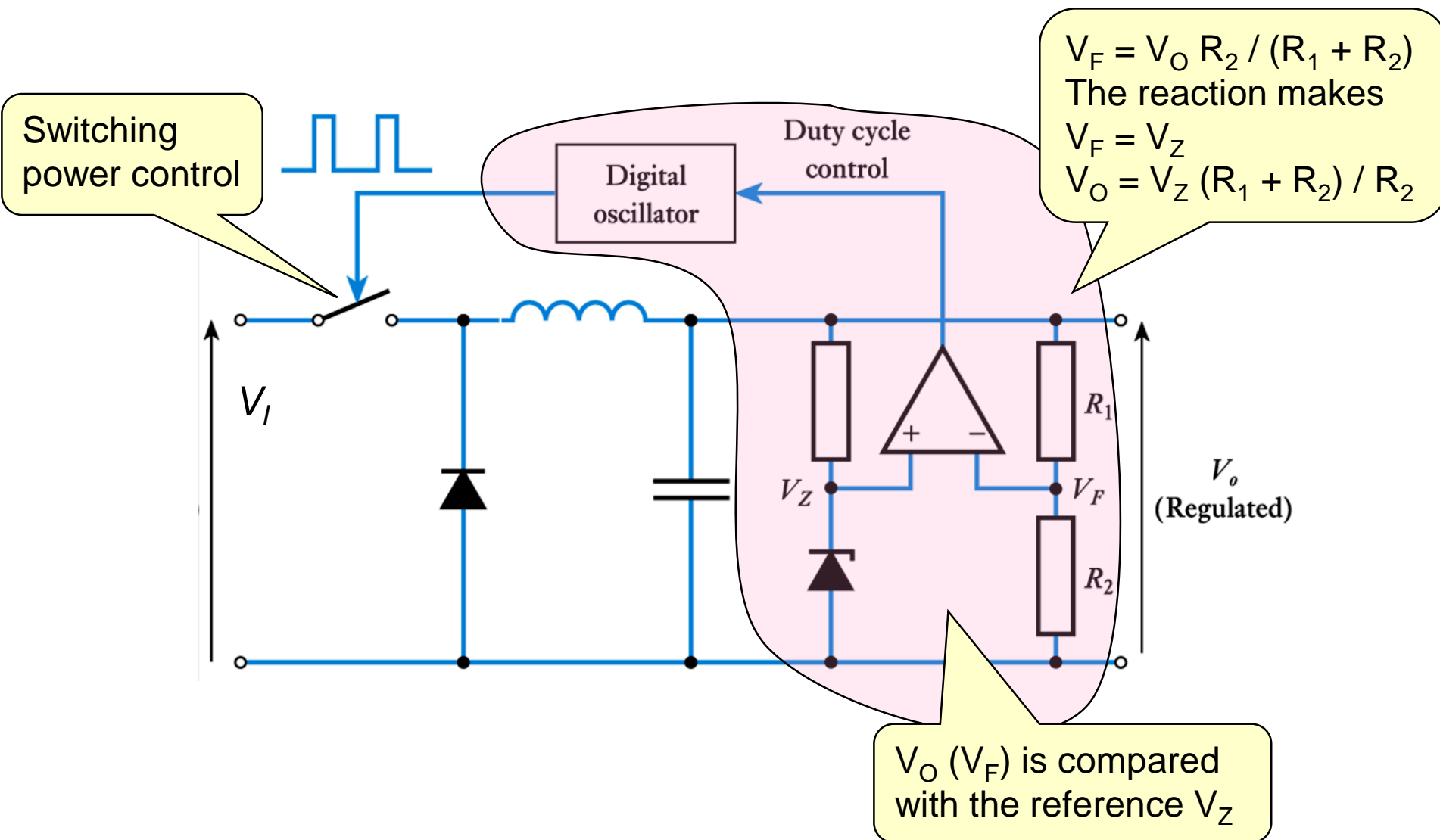




Types of switching regulators

- Converters dc \rightarrow dc, with various topologies
 - ◆ Buck $V_O < V_I$
 - ◆ Boost $V_O > V_I$
 - ◆ Buck-boost $V_O < V_I$ or $V_O > V_I$, reversed polarity
 - ◆ Flyback Buck-boost with galvanic insulation
- Benefit: **high efficiency** (close to 1)
 - ◆ Low power dissipation (unlike linear regulators)
 - ◆ Losses only from parasitic switch components, L, and C
- Disadvantages
 - ◆ Output ripple
 - ◆ Generation of interferences (EMI)

Behavior of an inductance

- Ideal inductance

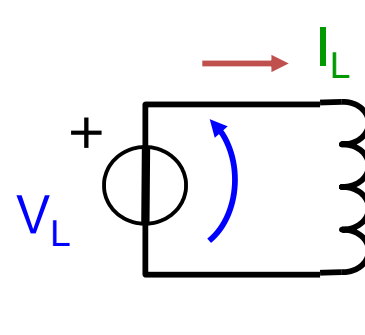- ◆ No current steps!
- ◆ $R_S = 0 \Omega$
- ◆ Applied voltage $V_L(t)$




$$I_L = \frac{1}{L} \int_{-\infty}^t V_L(t) dt$$

$$\Delta I_L = \frac{V_L \Delta T}{L}$$


- Voltage V step response

- ◆ Current ramp (I)

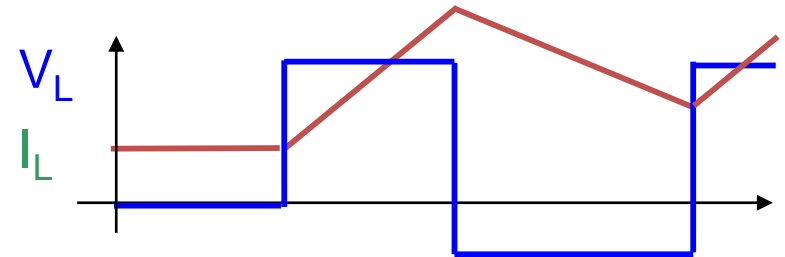

- Driving with square wave $V(t)$

- ◆ Triangular current $I(t)$

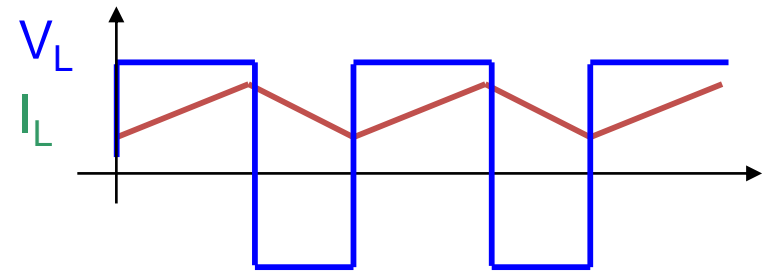




Lecture E3: switching regulators

- Switching power control
 - ◆ Works by varying the duty cycle
- Switching regulators
 - ◆ Buck $V_O < V_I$, presented in detail
 - ◆ Boost $V_O > V_I$
 - ◆ Buck-boost reverse polarity
 - ◆ Flyback isolation transformer


Buck regulator

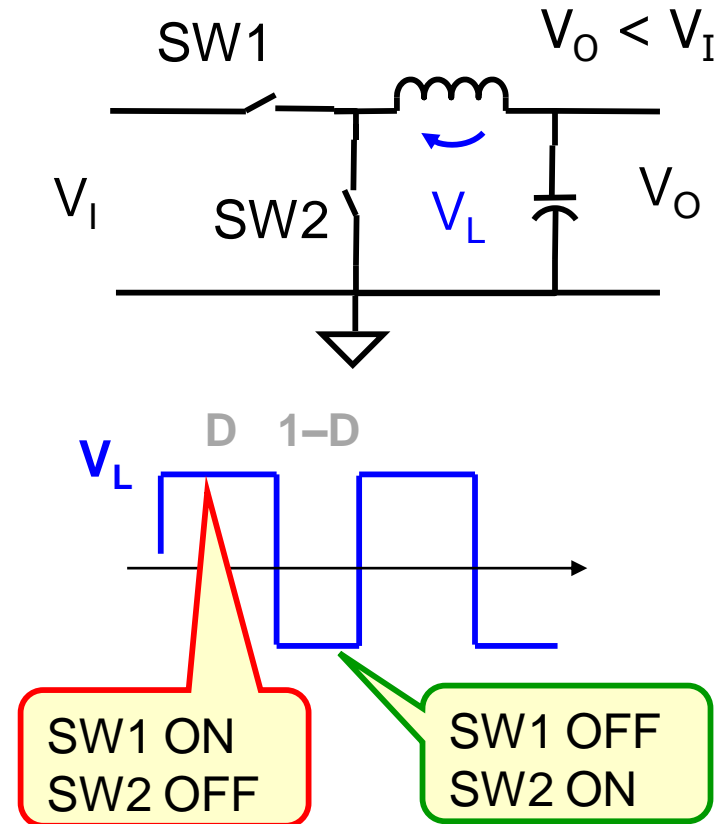- Switches SW1 and SW2
 - ◆ Complemented commands
 - ◆ SW1 is ON with duty cycle D
 $V_L = V_I - V_O > 0$
the current through L increases
 - ◆ SW2 is ON with duty cycle 1-D
 $V_L = -V_O < 0$
the current through L decreases




Buck regulator, ON state

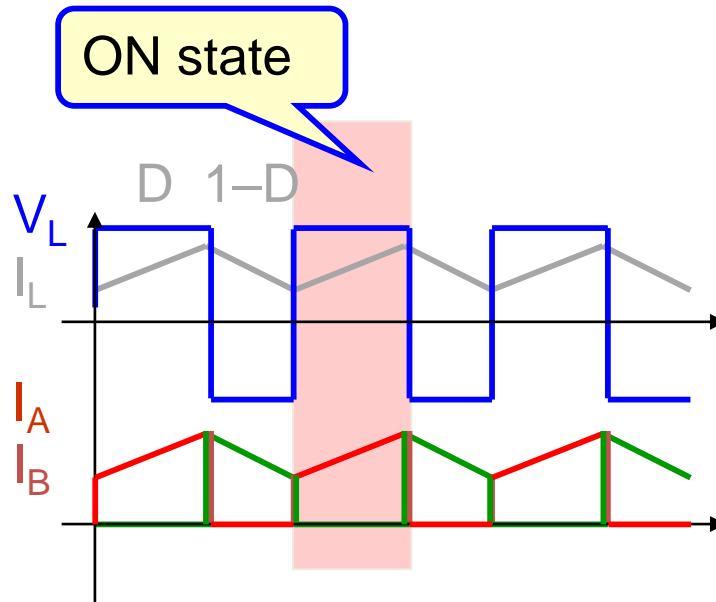- SW1 closed, the current flows from V_I to V_O through L



Current variation in the ON state

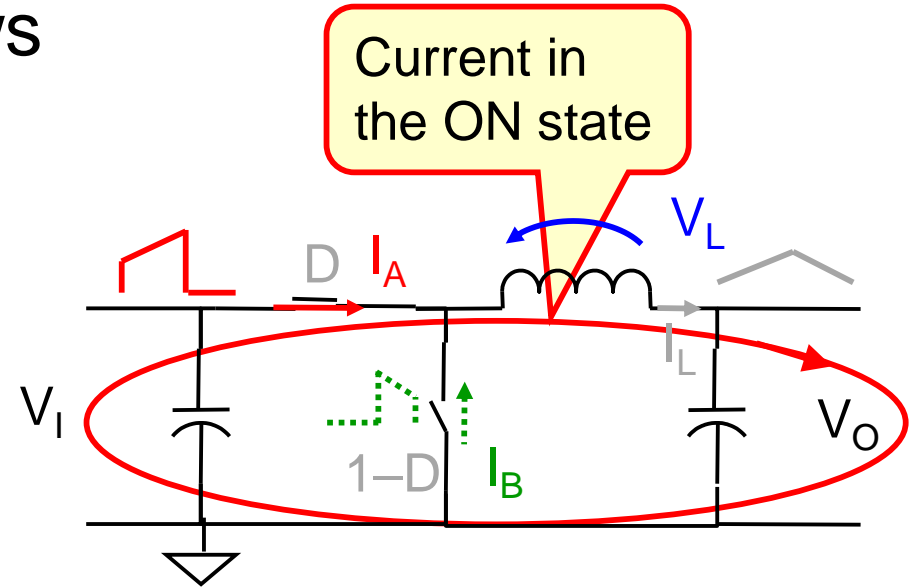

$$I_L = \frac{1}{L} \int_{-\infty}^t V_L(t) dt$$


$$\Delta I = \frac{(V_I - V_O) T_{ON}}{L}$$

Buck regulator, OFF state


Current variation in the OFF state

$$\Delta I = \frac{-V_O T_{OFF}}{L}$$

OFF state

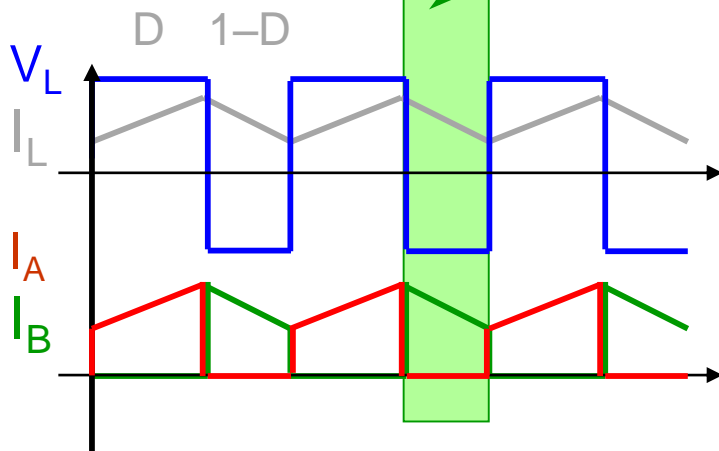

Current in the OFF state

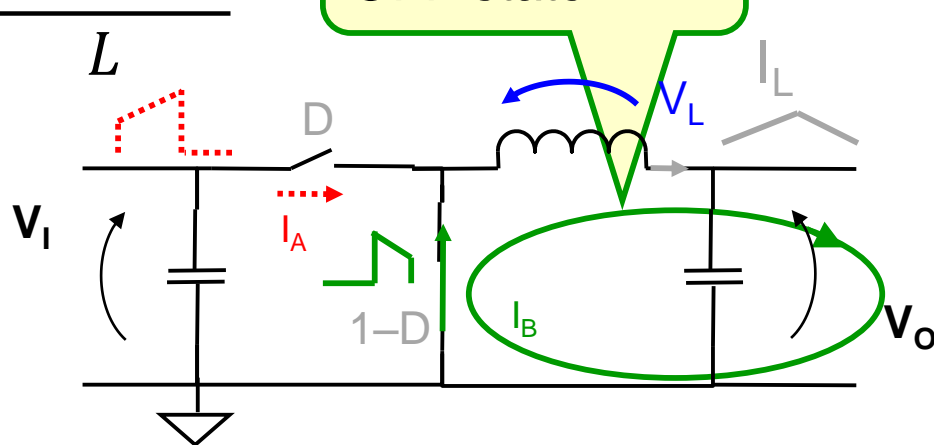

$$\Delta I = \frac{(V_I - V_O) T_{ON}}{L} + \frac{-V_O T_{OFF}}{L} = 0$$


We call: $D = T_{ON} / (T_{ON} + T_{OFF})$

Current variations in the ON and OFF states are balanced; the transfer ratio corresponds to the duty cycle of the ON / OFF command

$$\frac{V_O}{V_I} = D$$

Final schematic of Buck regulator

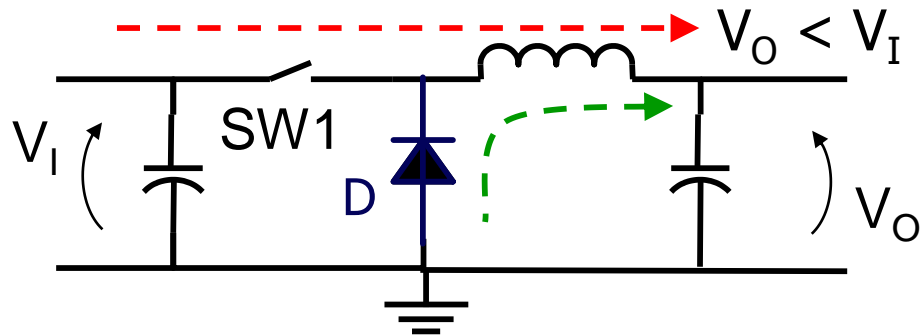- The SW2 switch can also be made with a diode (currently made with a MOS)
 - ♦ **SW1 closed**
 - Reverse biased diode, zero current \rightarrow SW2 OFF
 - ♦ **SW1 open**
 - The inductance tends to keep the current constant
 - Current can only flow through the diode \rightarrow SW2 ON






Efficiency of a Buck regulator



- With ideal switches and diodes
 - ◆ No losses → Efficiency $\eta = 1$
- With real devices we have several losses
 - ◆ Switches: non-zero R_{ON} and non-zero I_{OFF}
 - ◆ Diode (if any): non-zero V_D and non-zero I_S
 - ◆ Transients: MOS operates in the linear zone
 - ◆ L: non-zero series resistance R_L , losses in magnetic core
 - ◆ C: non-zero equivalent series resistance (ESR)
- Efficiency $\eta < 1$ (but close to 1: 0.8... 0.9...), based on the switching frequency
 - ◆ Similar parameters for the efficiency of all switching regulators

Boost regulator

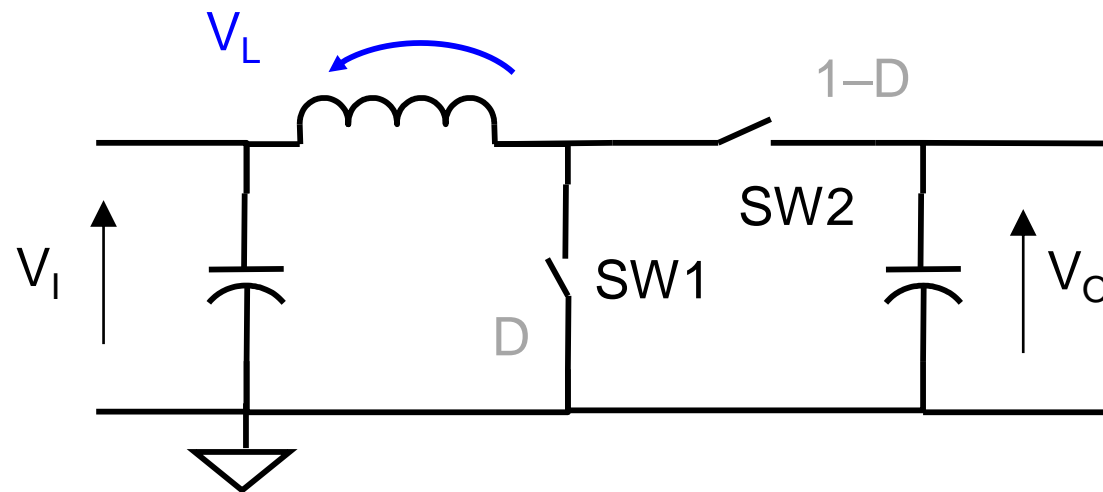- Exchange SW1 \leftrightarrow inductance with respect to the buck
- Similar operation and analysis
- Output voltage $V_{OUT} > V_{IN}$
- SW2 can be implemented with a diode



Boost regulator, ON state

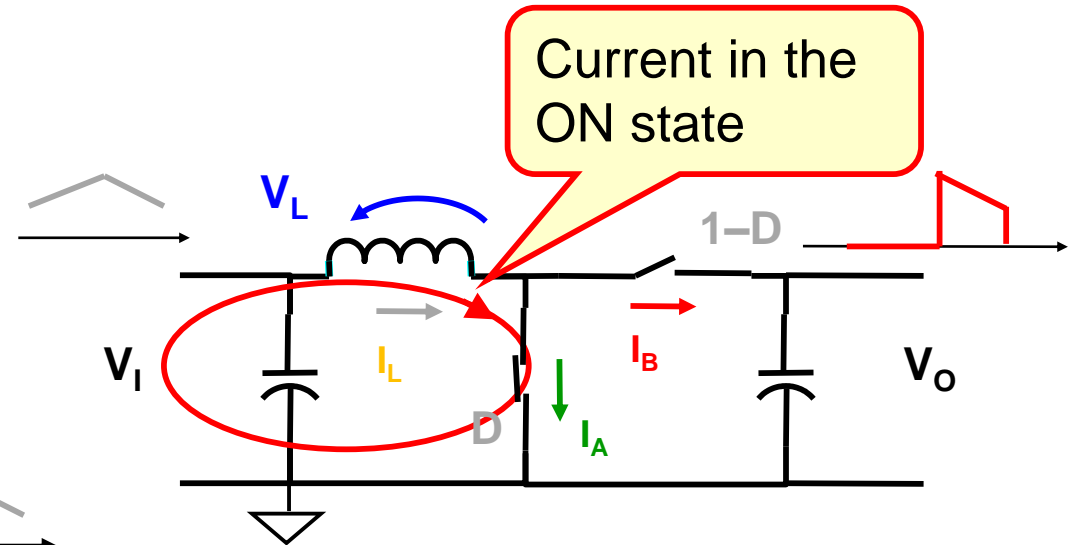
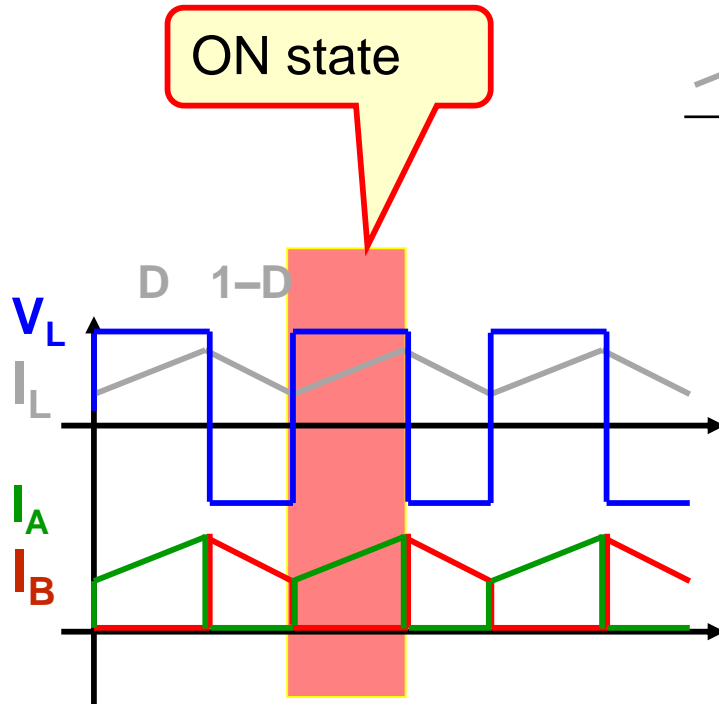


$$\Delta I = \frac{V_I}{L} T_{ON}$$

Inductance current variation in the ON phase

Boost regulator, OFF state

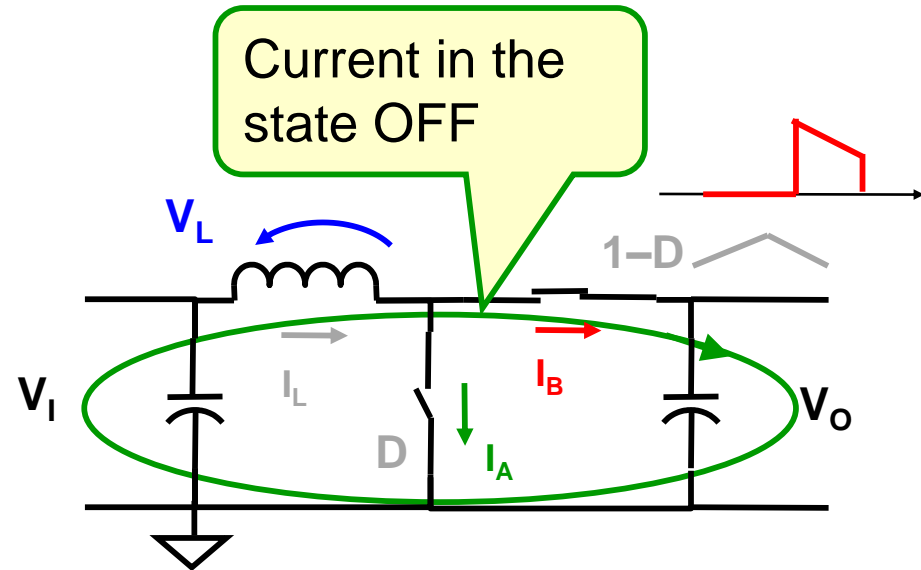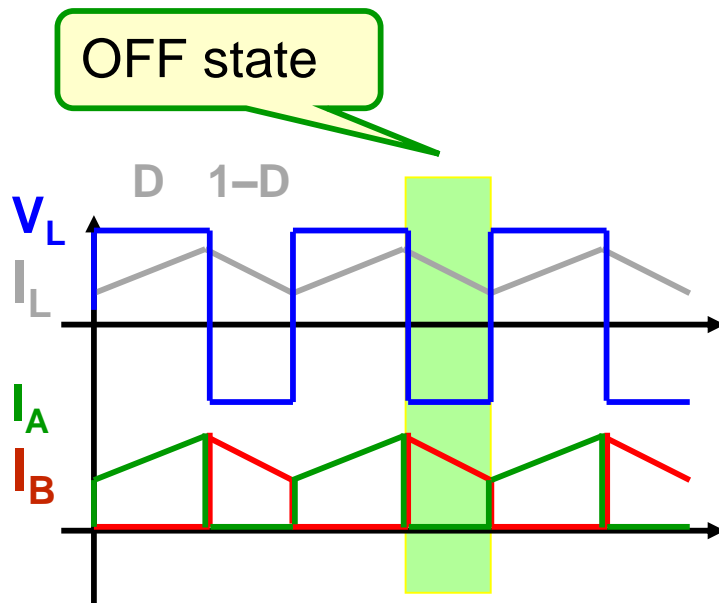- SW open: $V_L = -(V_O - V_I)$
 I_L is a ramp




$$\frac{V_I}{L} T_{ON} = \frac{V_O - V_I}{L} T_{OFF}$$

Transfer ratio defined by the duty cycle D


$$\frac{V_O}{V_I} = \frac{1}{1 - D}$$

Buck-boost regulator

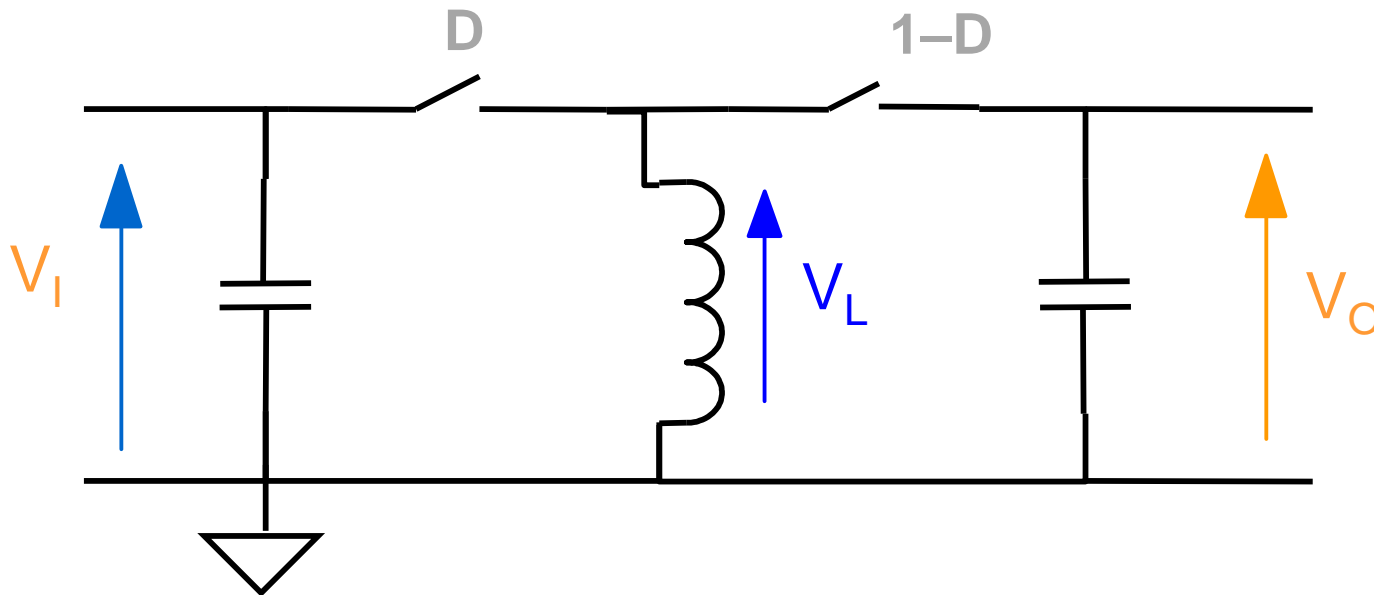- Combines buck and boost topologies
- Inverts the output voltage
 - ◆ $V_O < 0$ for $V_I > 0$



Buck-boost regulator, ON / OFF states

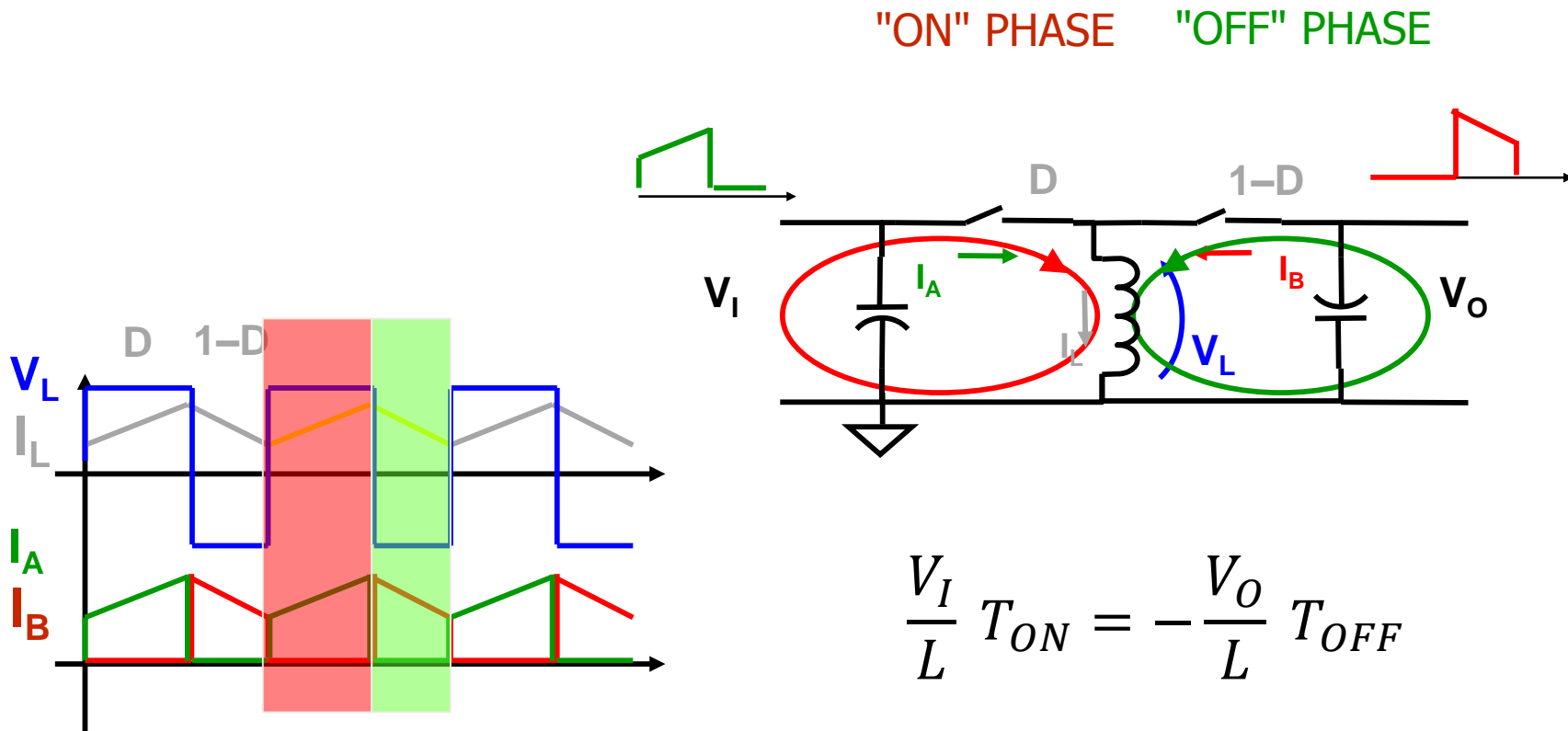


$$\frac{V_I}{L} T_{ON} = -\frac{V_O}{L} T_{OFF}$$

$$\frac{V_O}{V_I} = -\frac{D}{1-D}$$

Negative output voltage,
controlled by the duty cycle


Flyback power supply

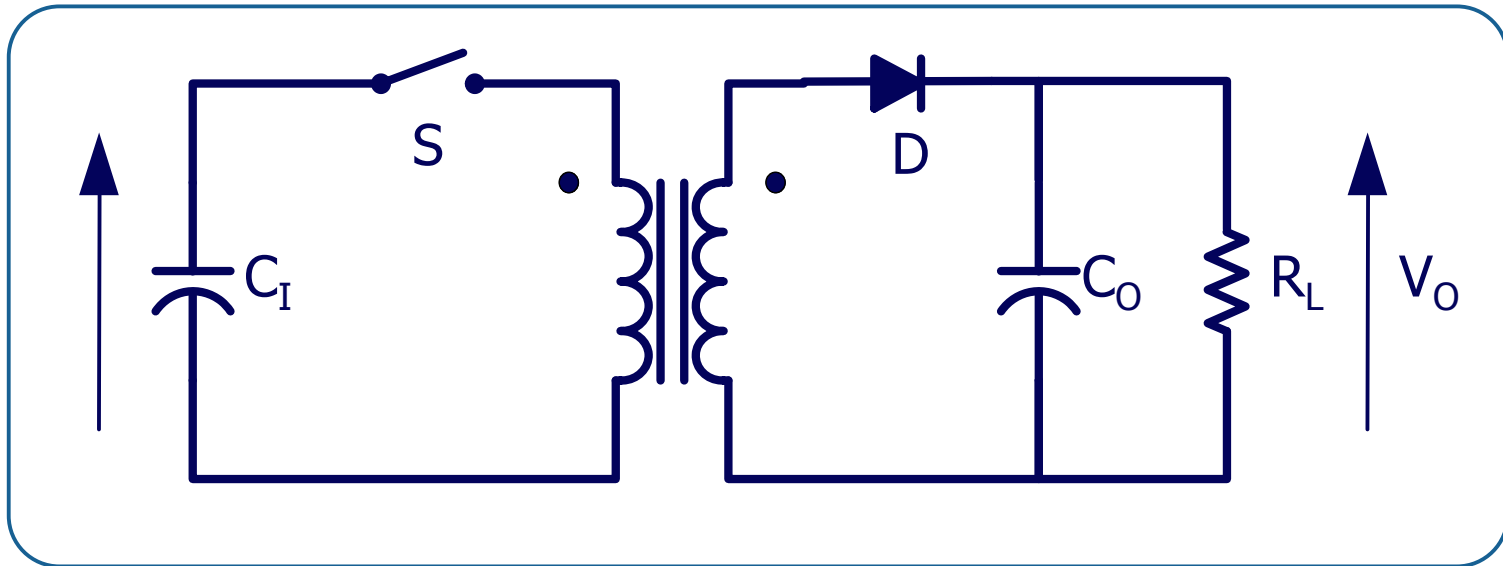- Provides **galvanic isolation**
 - ◆ Is a buck-boost regulator with a transformer instead of the inductance
 - ◆ For control is also used an isolated reaction (optical coupling)



Switching power supply

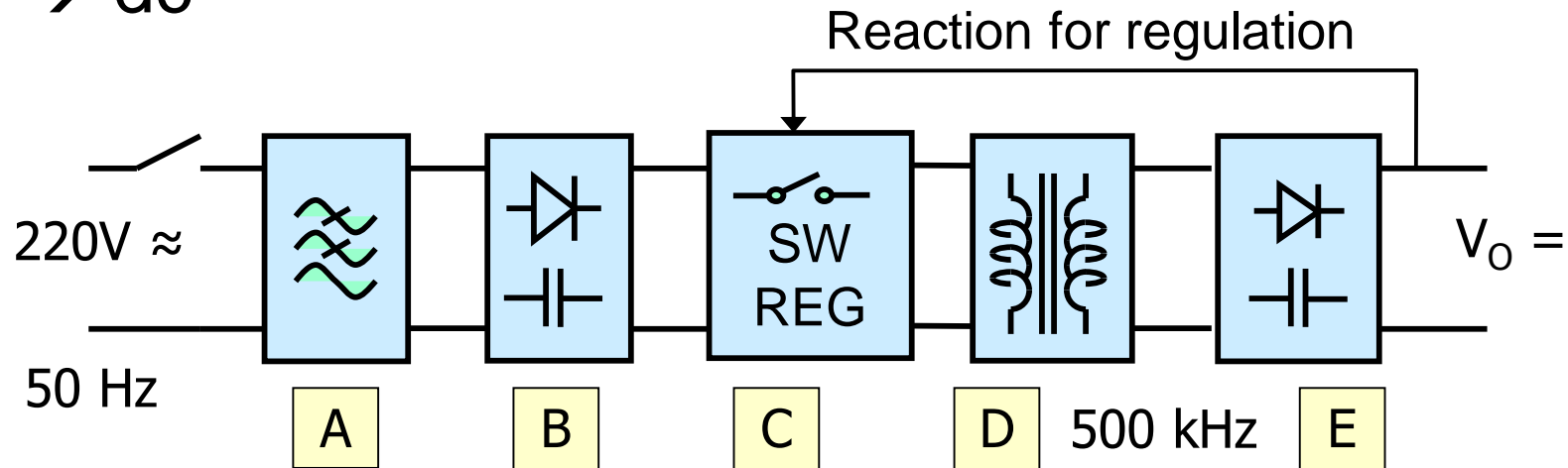- A. EMI filter
- B. From ac (mains) to dc
- C. Switching regulator (dc \rightarrow ac)
- D. Ac \rightarrow ac (high frequency, small transformer)
- E. Ac \rightarrow dc





Lecture E3: final verification

- Describe the PWM regulation technique.
- Draw the block schematic of a switching regulator power supply and describe the function of each block.
- Compare the advantages and disadvantages of linear and switching regulators.
- Draw the block diagram of the two basic switching regulator topologies and describe their operation.
- What parameters affect the output ripple in switching power supplies?
- What parameters affect the efficiency?
- Differences between buck and boost regulators?